

# **Large Signal Modeling of GaN HEMT based Circuits**

Ray Pengelly  
May 2010  
Revision 2

Some examples use latest rev.6 LS models





# Acknowledgement

- None of the material in this tutorial would have been possible without the tremendous work achieved by Bill Pribble who, over many years, has developed large-signal models for Cree's GaN HEMT transistors used within both hybrid and monolithic circuits.
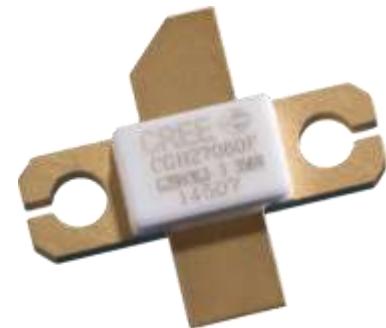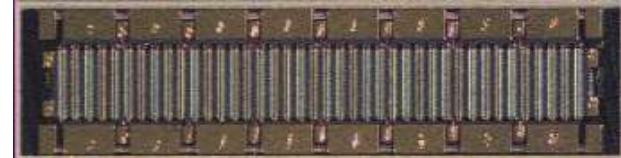
# Contents

- Introduction
- Attributes of GaN HEMTs
- Cree GaN HEMT Models
  - Electrical
  - Thermal
  - Noise
- Design Examples
  1. Basics
  2. 500 to 2700 MHz Amplifier using CGH40010F
  3. Various Broadband Amplifier Design approaches using CGH40090PP
  4. 2 to 6 GHz power amplifier using CGH40010F
  5. Linear WiMAX amplifier using CGH27060F
  6. 6 GHz linear amplifier using CGH55015F
  7. High efficiency waveform engineered PA using CGH40120F
  8. Linear Driver amplifier for DVB-H using CGH27030F
  9. Doherty amplifier using CGH21240F
  10. Comparing Balanced and Doherty amplifier performance with CGH09120F
  11. Noise Figure Analysis of an amplifier using the CGH40006P
- Further Reading



# Introduction

- Large signal models are available for all Cree GaN HEMT transistors
  - Agilent's ADS and AWR's Microwave Office are fully supported
- Highly accurate with excellent history of design pass successes
- Enable complete DC and RF simulations
- Models include self-heating (presently single-pole thermal time constant)
- If customer does not have NDA in place with Cree then a simple DMEA (Device Modeling Evaluation Agreement) needs to be signed prior to model library delivery
- Model library is regularly updated
- Many “starter” designs can be provided

# Attributes of GaN HEMTs


- High Voltage Operation
- High power densities – 4 watts/mm at 28 volt operation
- High Frequency Performance – present Cree process has  $f_T$  of 25 GHz
- High Efficiency
- Low Quiescent Current
- High Native Linearity
- Low capacitance per peak watt (12% of LDMOS and 21% of GaAs MESFET) – supports broad bandwidths
- Enable new amplifier architectures
- Highly correctable under DPD
- Almost constant  $C_{DS}$  as a function of  $V_{DS}$  – great for Drain Modulation

Wide Bandgap

# Models for GaN HEMTs

- Equivalent-circuit based approach
  - Relatively simple extraction
  - Process sensitive based on individual elements
  - Simple implementation using commercial harmonic balance simulators
- Significant historical information for model basis and validation
- Non-linearity introduced as required by element
  - Drain current source is dominant non-linearity
  - Gate current formulation includes breakdown and forward conduction
  - Voltage variations of parasitic capacitances derived from charge formulations
- Model data fit extends over drive, frequency, bias, and temperature
- Many hundreds of successful hybrid and MMIC designs


# Model Schematic

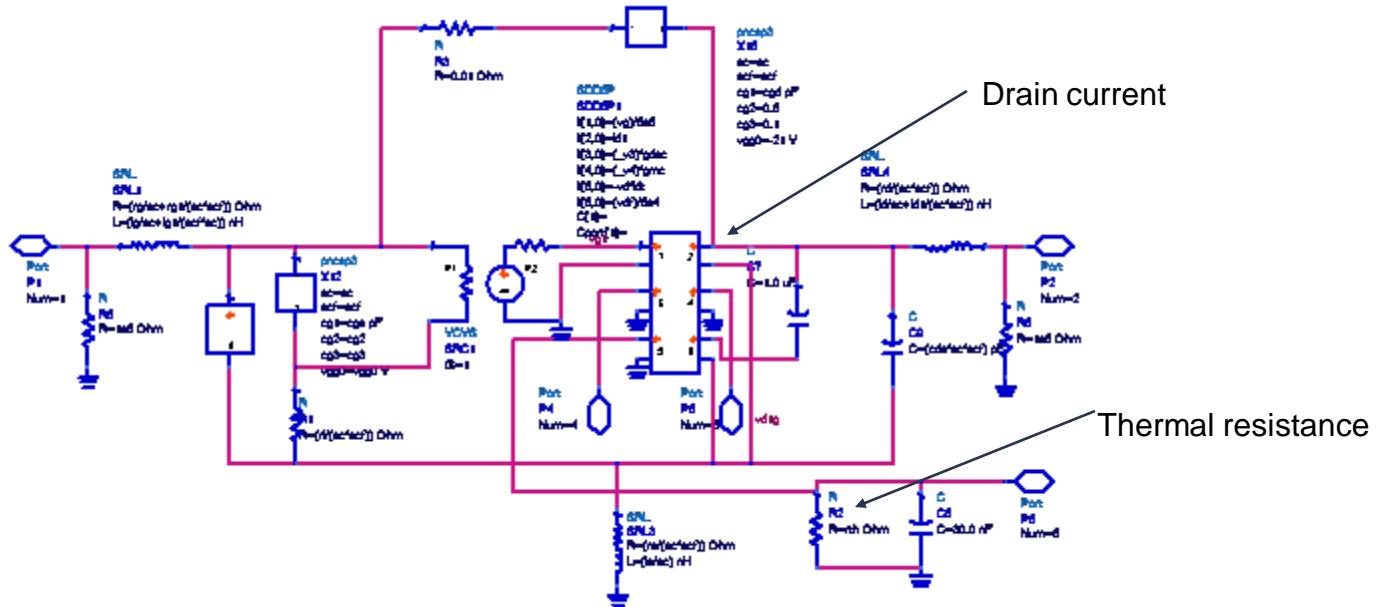

- Based on 13-element MESFET model (Fager-Statz)
  - ADS version shown using non-linear equation-based elements
    - Easily changed during design process
    - Speed comparable to C-coded version
  - AWR version uses C code with “model wizard”

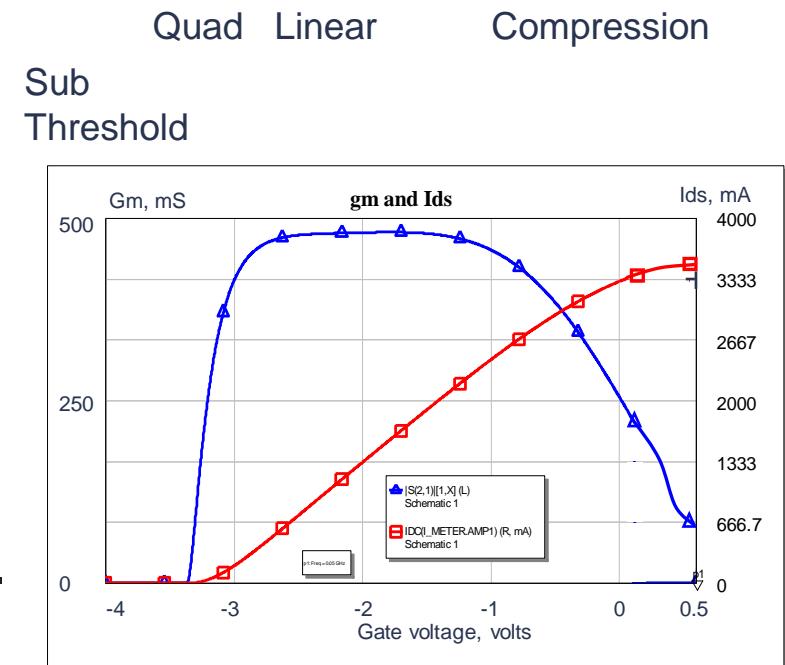
# More details on Cree GaN HEMT Model

- Most FET models implement a gate current-control characteristic that transitions from the sub-threshold region to the linear gate control region directly, without treating the intermediate region, called the quadratic region. Fager et al. implemented an equation and new parameters to fit the quadratic region. This leads to better agreement with measured IMD and other nonlinear characteristics.
- Gate charge is partitioned into gate-source and gate-drain charge. Each charge expression is a function of both  $V_{DS}$  and  $V_{GS}$ . Using charge partitioning, it is possible to fit most GaN HEMT capacitance functions and observed charge conservation.





Blue is DC transconductance  
Red is drain current

# More details on Cree GaN HEMT Model

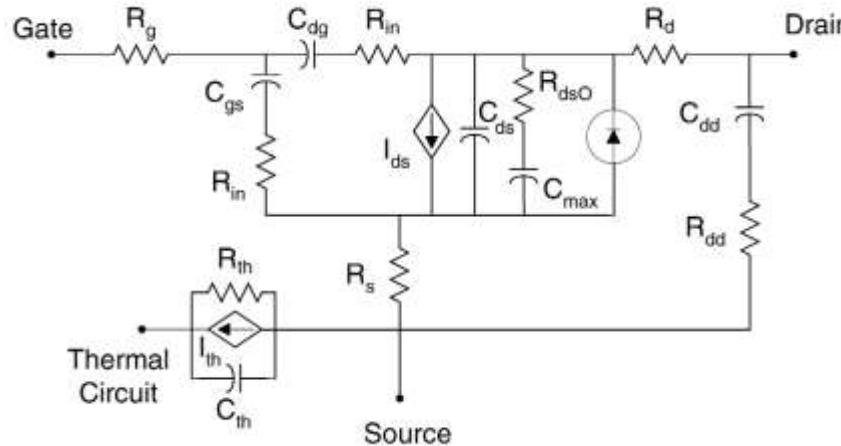


- The model includes new capacitance functions as well as modeling of the drain-source breakdown and self heating.
- The model has four ports, with the extra port providing a measure of the temperature rise. The voltage between the external thermal circuit port and the source node is numerically equal to the junction temperature rise in degrees C. This occurs because the current source in the thermal circuit is numerically equal to the instantaneous power dissipated in the FET and the resistance,  $R_{TH}$  is numerically equal to the thermal resistance. The RC product of the thermal circuit is the thermal time constant.
- The model addresses the sharp turn-on knee in GaN HEMTs leading to the accurate prediction of IMD sweet spots in Class A/B operation.

# Drain Current Model

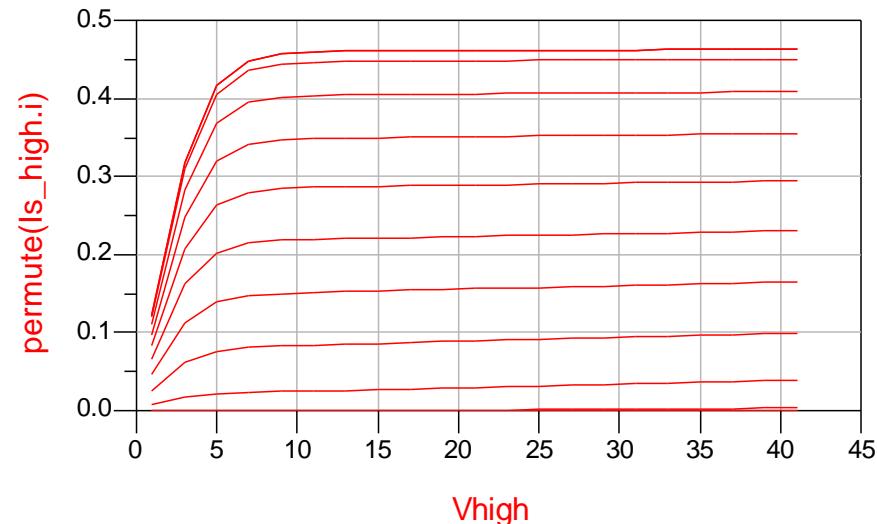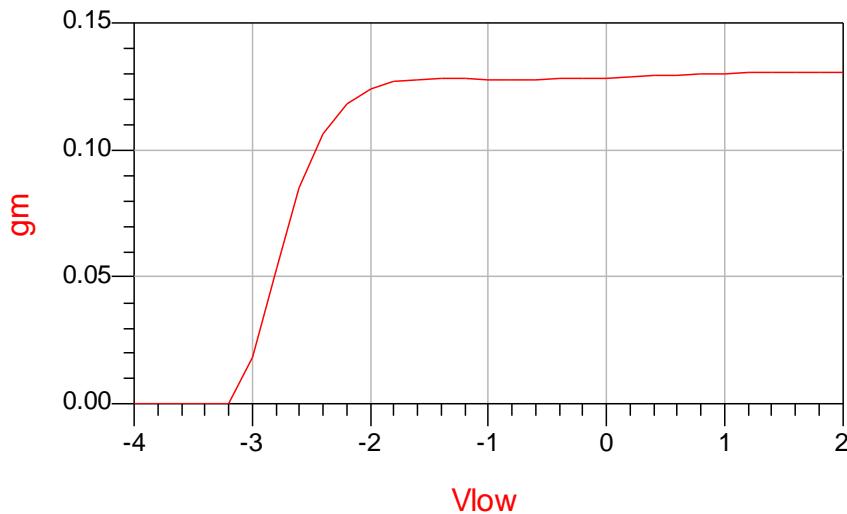


- Transconductance curve fit to  $Gm$  from small-signal model fits over bias range
- Output conductance dispersion model
- Peak current and knee voltage fit from load-pull - includes trap effects
- Pinch-off fit from DC IV-characteristics – gives model of drain current
- IV function similar to Statz formulation – good model of pinch-off needed to accurately predict intermodulation distortion

# Temperature Dependence – Self-heating

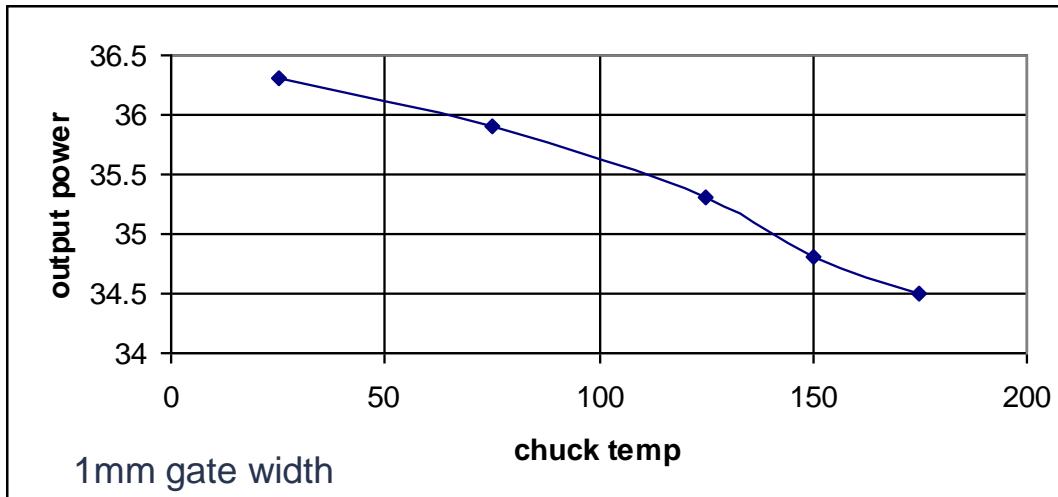


- Drain current is only temperature dependent model element
- Drain current scales to provide  $-0.1 \text{ dB}/10^\circ\text{C}$  reduction in power for current-limited load-line
- Self-heating included using a thermal resistance – calculated from finite element analysis of die and package.
- Thermal performance due to package needs to be included where appropriate

# Feedback Capacitance - $C_{GD}$

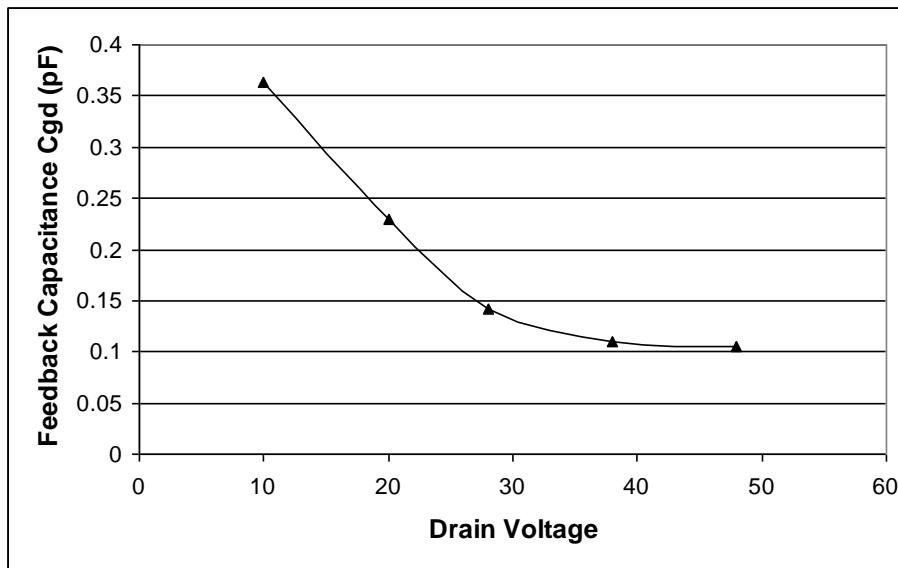

- Feedback capacitance is a strong function of drain voltage
- Inclusion of this effect necessary to fit small-signal data
- Non-linearity changes harmonic generation from the model – effects efficiency and linearity predictions
- Output Capacitance  $C_{DS}$  is linear – no voltage dependence (weak anyway)


# Input Capacitance - $C_{GS}$

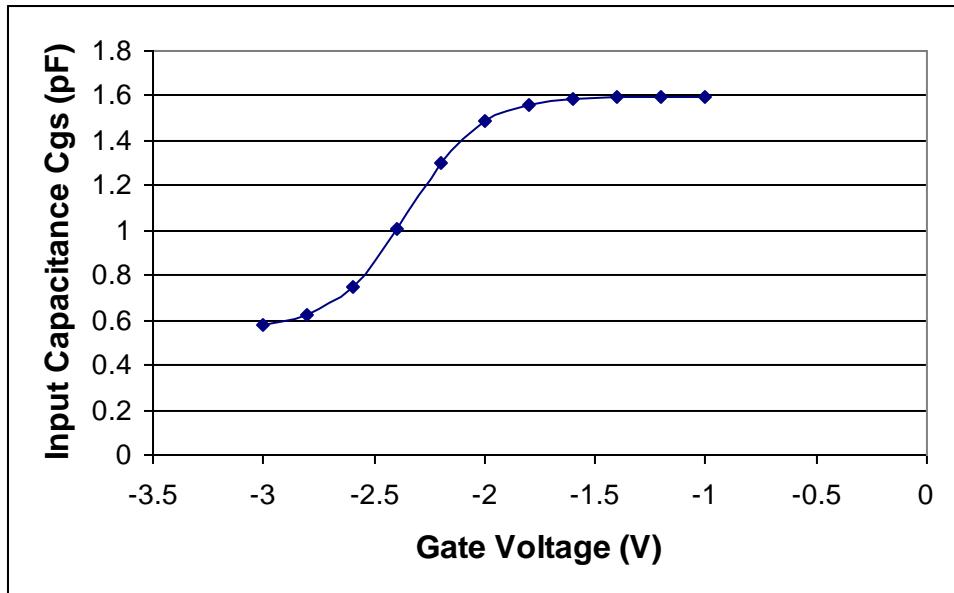

- Input capacitance is a strong function of gate voltage
- $C_{GS}$  is also a function of drain voltage, but this non-linearity is not included at present
- The gate-voltage non-linearity also effects model's harmonic generation

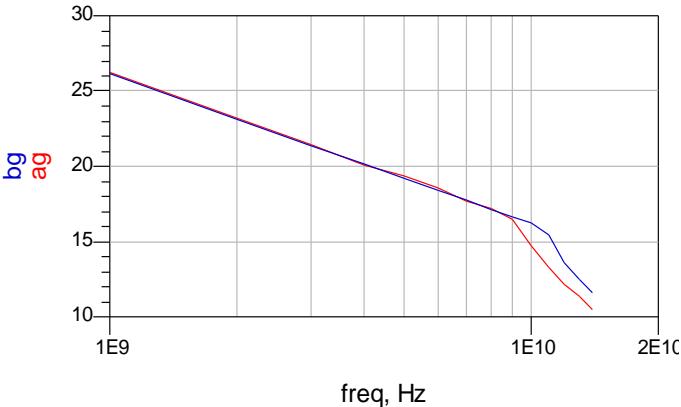
# GaN HEMT Model - Small-Signal

Measured G<sub>max</sub>  
Model G<sub>max</sub>



measured  
model

a(2,2)  
b(2,2)  
a(1,1)

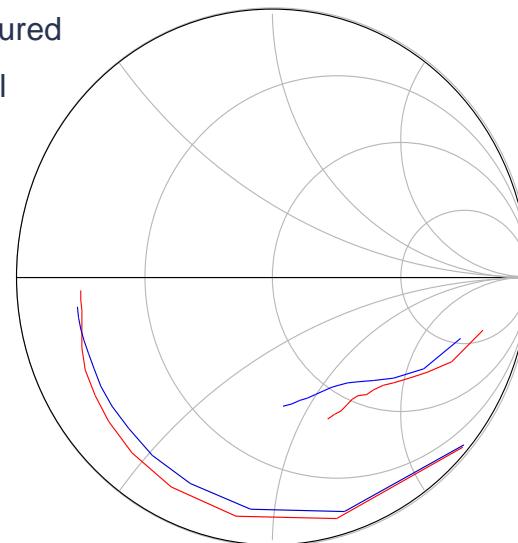

freq (1.000GHz to 14.00GHz)

- On-wafer S-parameters of 0.5 mm HEMT – 25°C baseplate
- Major challenge of modeling for high power circuits – scaling from reasonable test cell to large periphery output stages – successfully implemented for scaling factors >100:1
- Non-linear model fits small-signal parameters over a range of bias voltages
- All measurements performed using 1% duty cycle, 20µs pulsed bias to control thermal effects


# GaN HEMT Model - Large-Signal

Power Contour Levels:

36 dBm

35 dBm


34 dBm

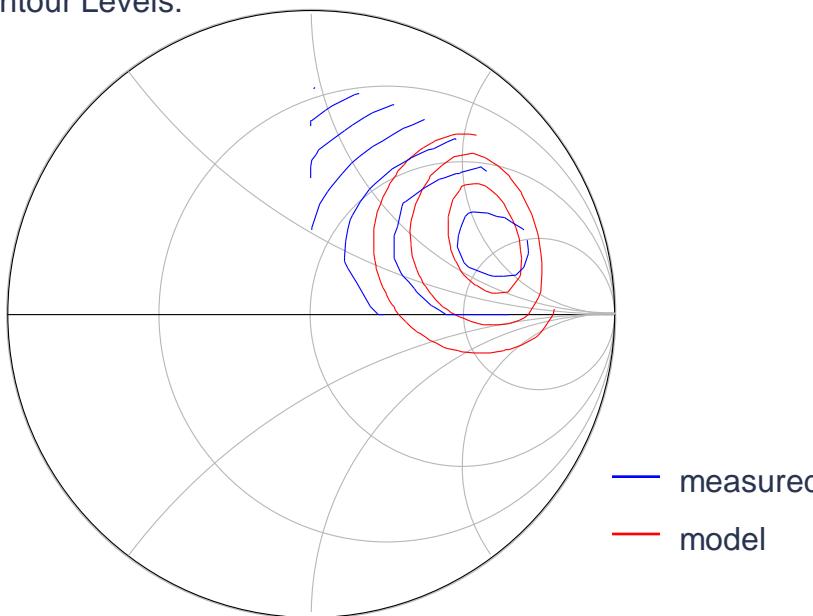

- On-wafer load-pull of 0.5 mm HEMT
- Measured at 3.5 GHz,  $V_{DS}=28V$ ,  $I_d \sim 25\% I_{DSS}$ , 25°C chuck temperature
- PAE contours not used for modeling due to sensitivity to harmonic loading – PAE verified using hybrid amplifier measurements
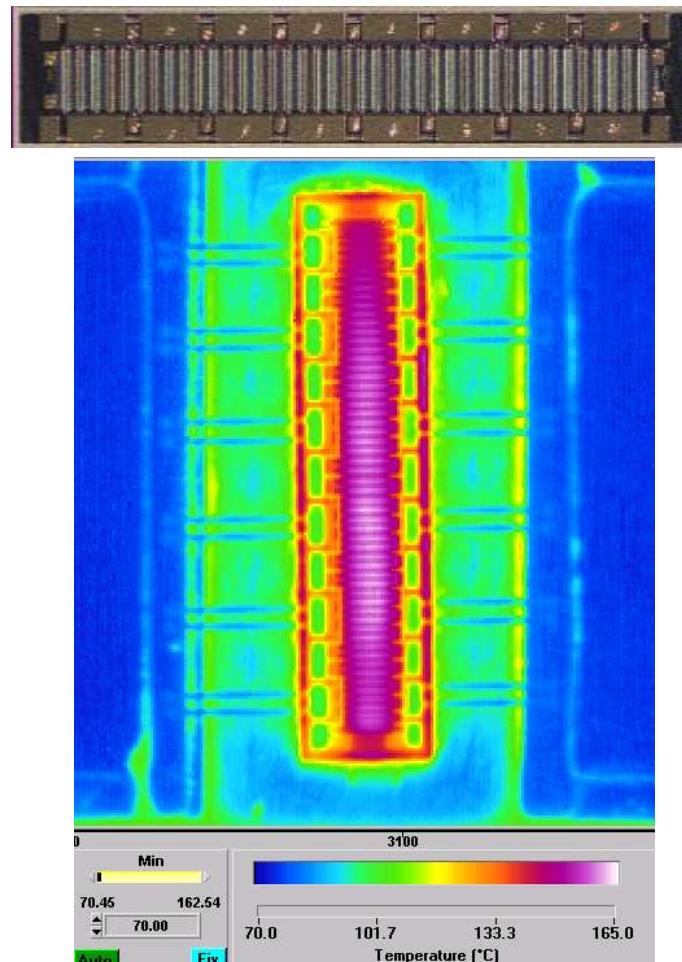
# Basic Thermal Features of High Voltage GaN

- 120 Watts CW RF from a 28.8mm HEMT operating at 28 volts drain voltage
- Assume 60% DC to RF conversion efficiency
- 80 watts dissipated heat
- Active chip area is 2.5 sq. mm so heat density is > 20 kilowatts per square inch !
- Much emphasis on new amplifier architectures to improve drain efficiencies



# **Thermal Modeling**



# Introduction

- Use of Infrared microscopy and finite element analysis are used to produce accurate channel to case temperature differentials
  - Junction to case thermal resistance can then be calculated
- Steady state thermal FEA, using Ansys software, is done where temperature dependence is accounted for in the GaN, SiC and Au materials
- Method has been extended to transient analyses (for pulsed and modulated (DC and/or RF carrier) where the density and specific heat of the materials are also required to calculate time constants
  - Dramatic (and useful!) differences in effective thermal resistances between short pulses and CW – by factors of 4 or more

# Thermal Conductivities of Relevant Materials

Material	Thermal Conductivity (W/mK)
GaN	130
AlGaN	19
SiN (passivation)	33
SiC	430
Au	317
AuSn (die attach)	57
CuMoCu (package)	300
Cu (fixture)	370

# Thermal Analyses and Measurements

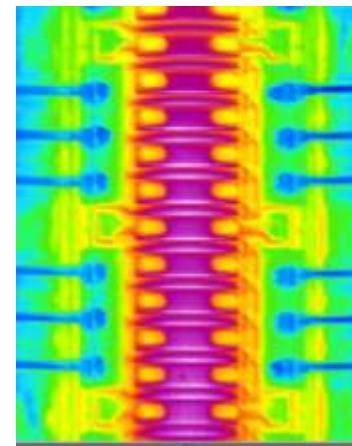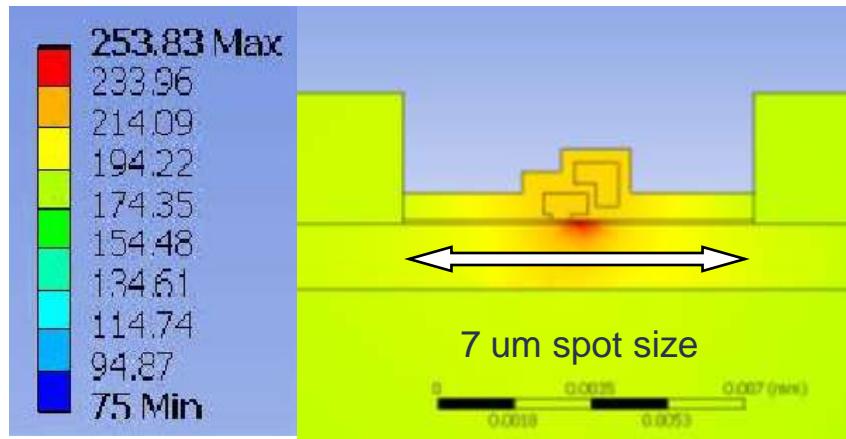


IR Scan

- 4 mil thick 14.4mm GaN HEMT
- 60 mil thick CuMoCu package dissipating 4 watts/mm (58 W)
- Thermal gradient is very high surrounding the heat source  
58C drop at a distance of 3.5um from the heat source!
- 38C drop through the AlGaN layer
- 46C drop through the GaN layer
- Accounts for temperature difference between the actual channel and the “average” temperature measured by the IR system (across the spot size)

## Confidence Intervals


Parameter	Estimate	Lower CI	Upper CI	1-Alpha
Mean	1.925	1.858268	1.991732	0.950
Std Dev	0.079821	0.052776	0.162458	
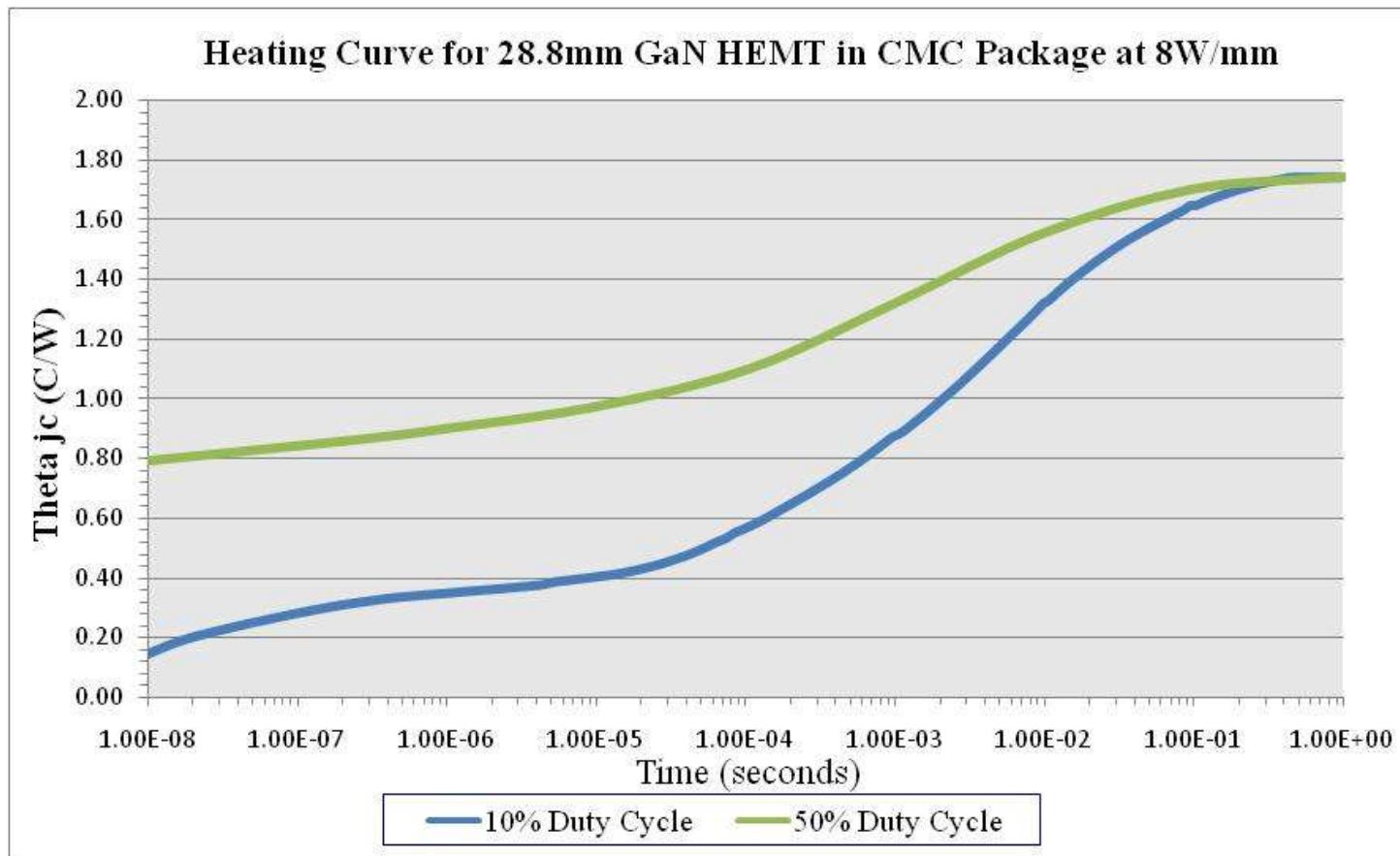
# Effective Thermal Resistance versus Pulse Width




- Transient Thermal Responses of a 28.8mm GaN HEMT in a 60 mil thick CuMoCu package dissipating 8W/mm at 10% and 50% duty cycles
- Two distinct slopes show the different transient thermal properties of the die and the package
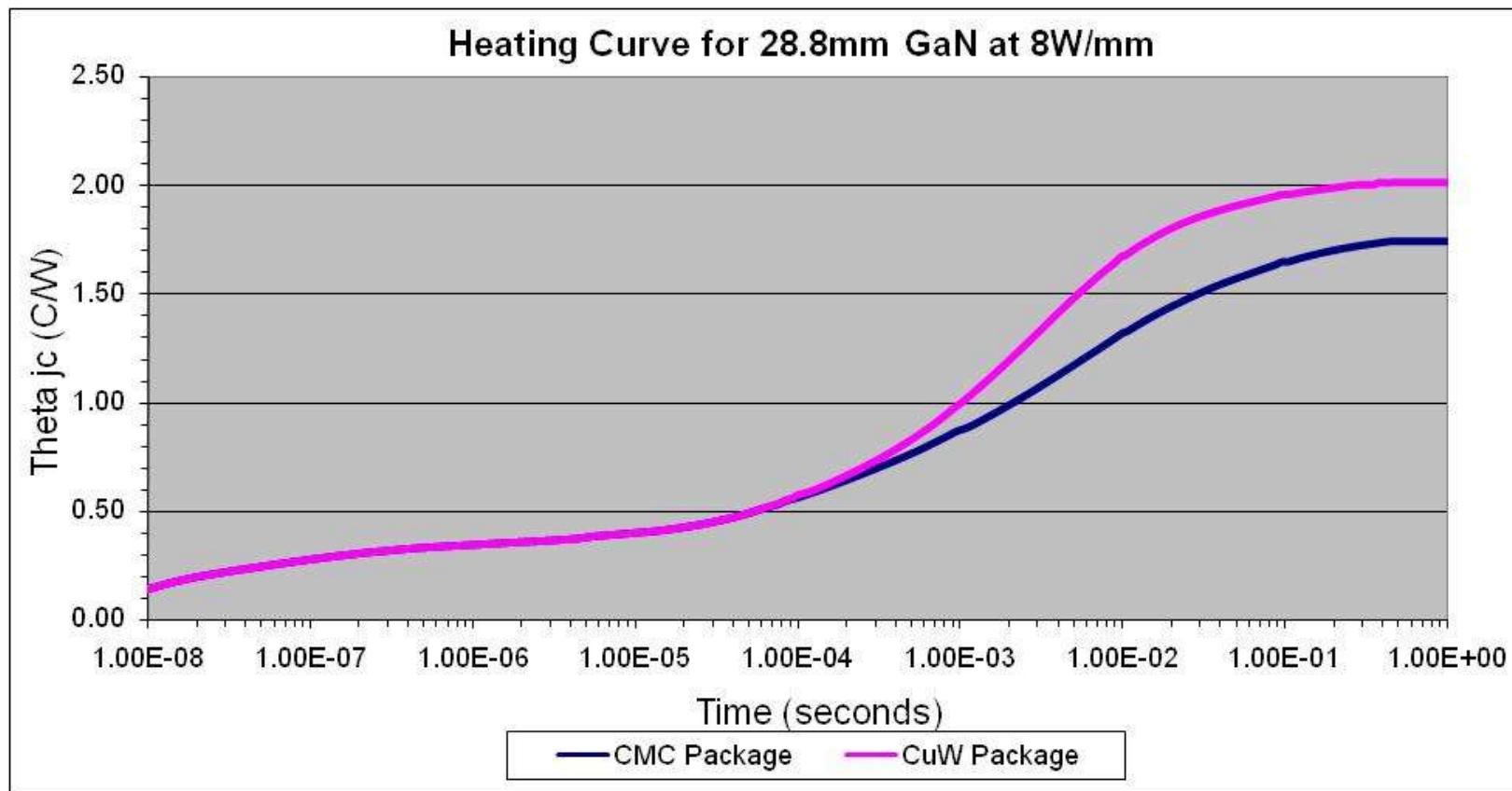
# Effective Thermal Resistance versus pulse width for two different package flange materials




- Difference in thermal resistance of same 28.8mm GaN HEMT mounted in 60 mil thick CuMoCu versus 40 mil thick CuW package
- Note that the thermal resistance up to 100 usec pulse width is same and then effect of package time constant can be seen
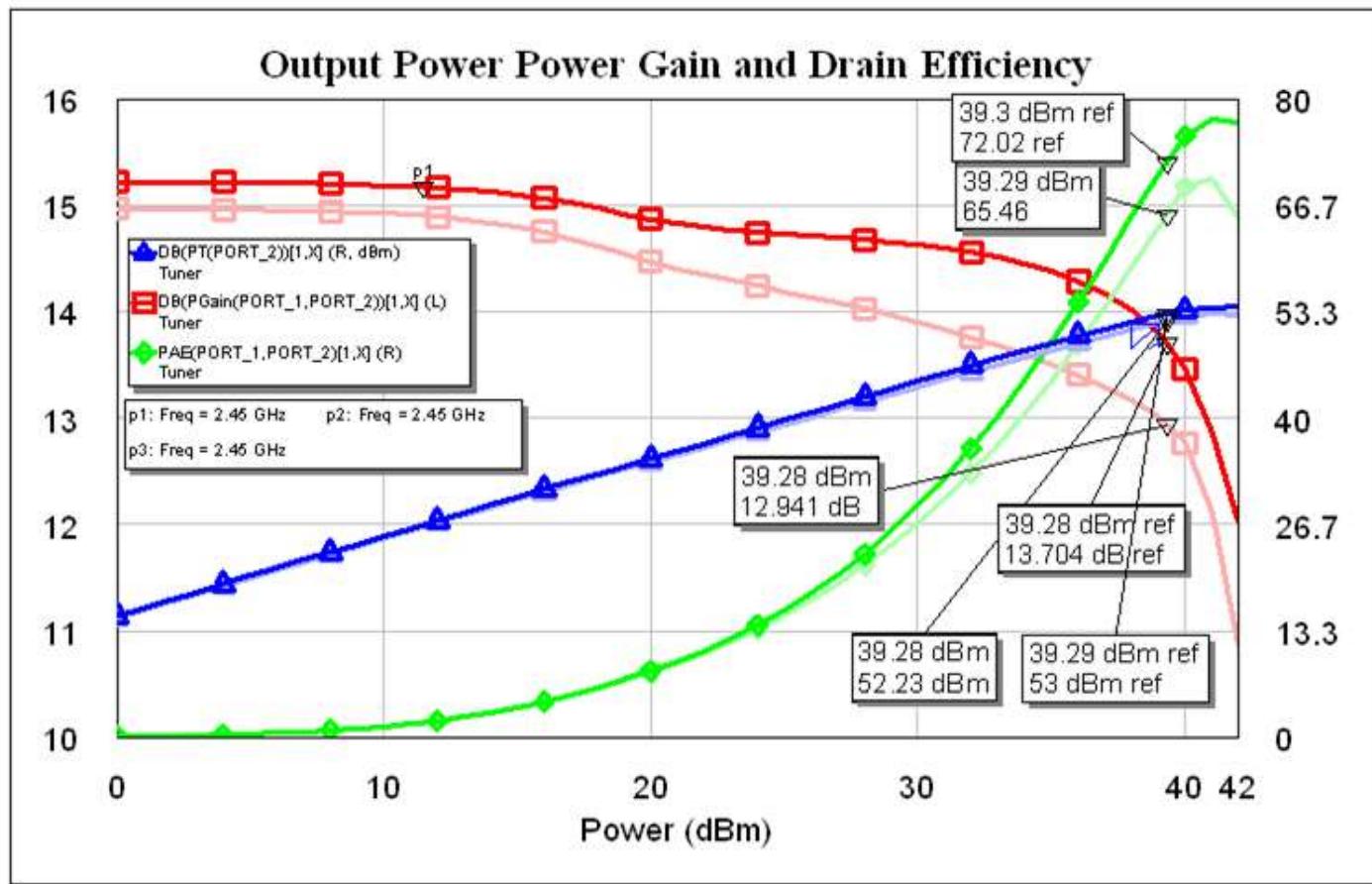
# Example of including self-heating model for efficient Class A/B power amplifier




- Operation of 28.8mm GaN HEMT with and without self-heating
  - Bolder colors are without self-heating included in simulations

# Basic Doherty Amplifier Configuration

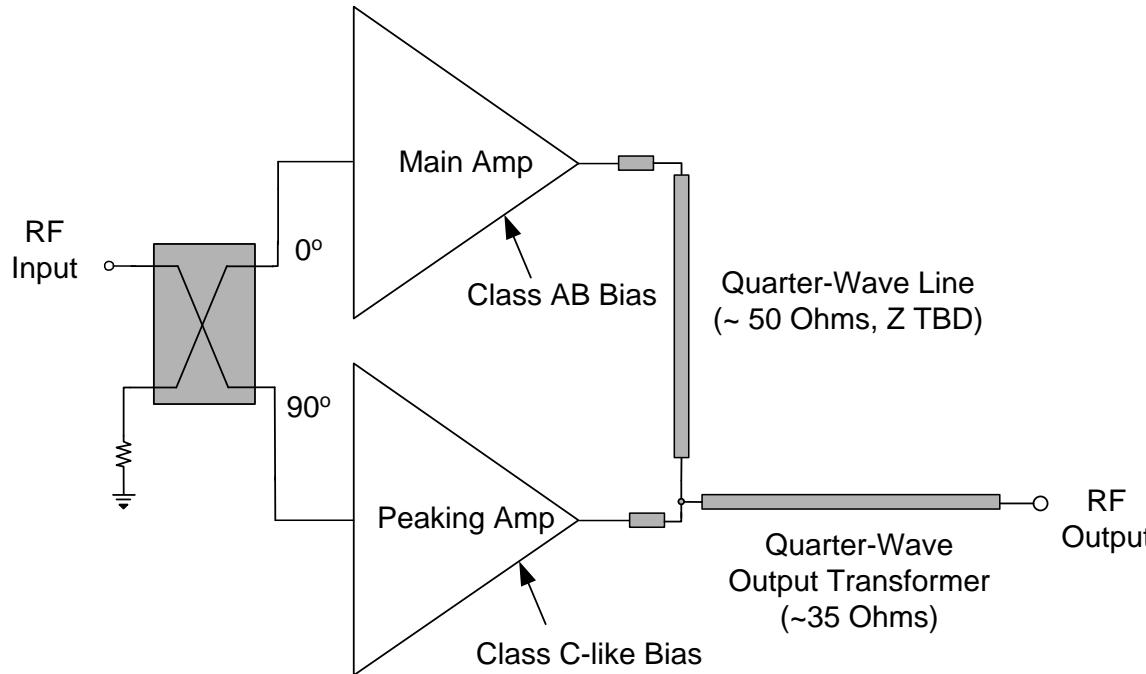

- The Doherty amplifier configuration is becoming more and more popular as a means of improving overall DC to RF conversion efficiency
- Up to certain input power levels the carrier amplifier saturates earlier than a conventional Class A/B Amplifier because of the load impedance it sees – the peaking amplifier is still OFF
- Above a certain input power level the peaking amplifier turns ON and contributes power as well as altering the load line to the carrier amplifier

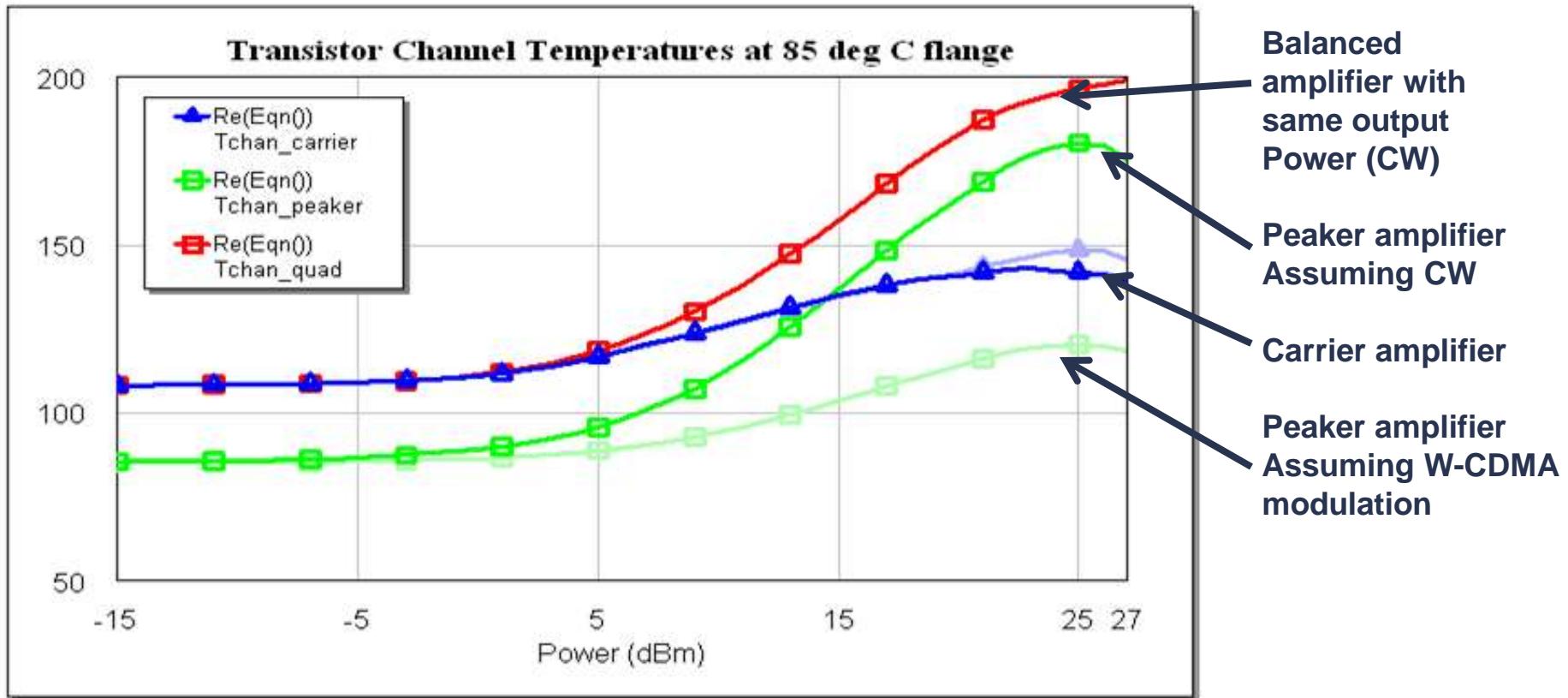
# Example of using self-heating model in a Doherty Amplifier



- Transistors operating at 7 W/mm at peak power
- Bolder colors show channel temperatures if CW is assumed
- lighter traces show channel temperatures when the Doherty amplifier is handling W-CDMA




# Noise Modeling
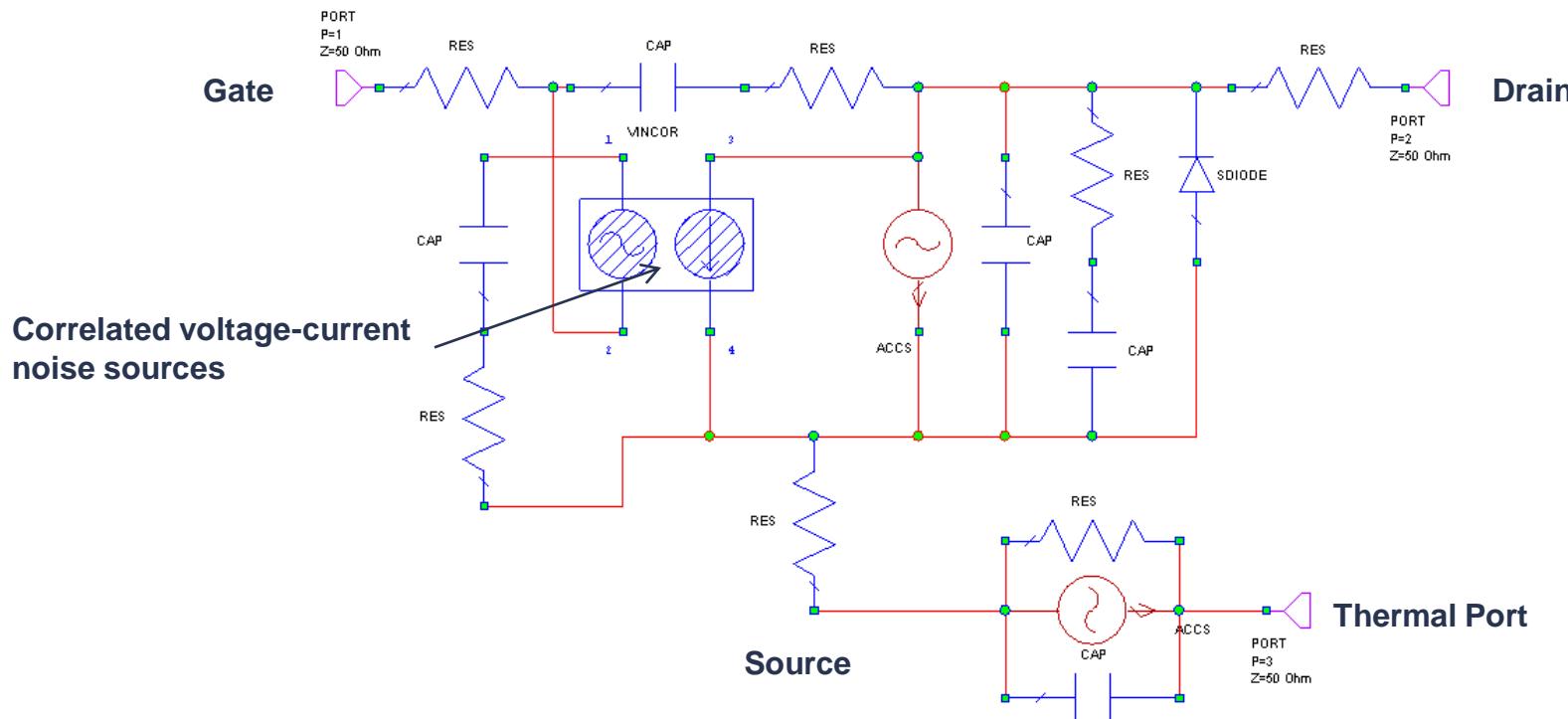
# Simplified Nonlinear HEMT Model including noise





Noise is generated from parasitic resistive elements as well as intrinsic noise sources as shown here. Noise sources are defined by voltage and current noise sources which are correlated.

# Noise Parameters

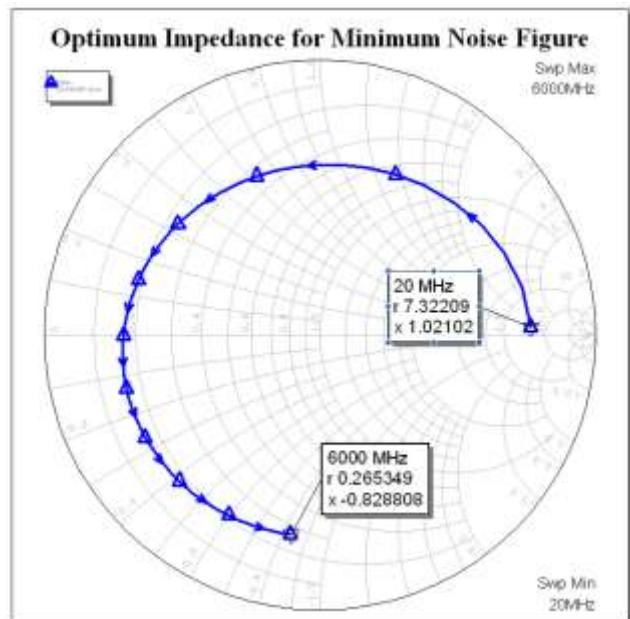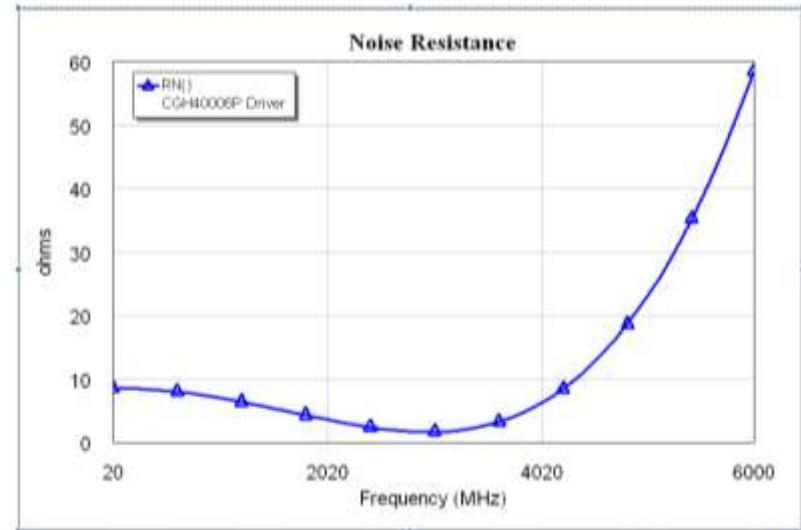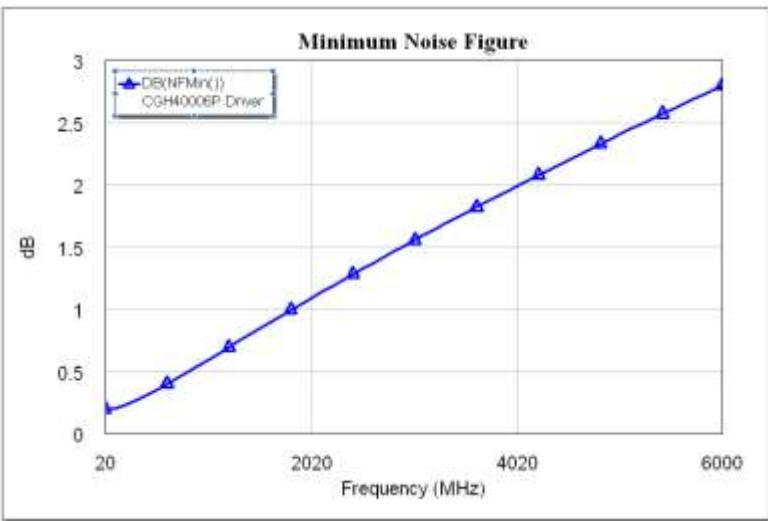

Noise parameters simulated from extracted model are shown for CGH40006P  
Conditions are Vdd=28 volts, Idq=65 mA  
Frequency Range is 20 to 6000 MHz  
Original noise parameters measured “on-wafer” using small gate width transistors. Noise parameters are scaled from these devices to required sizes


# Noise Figure and Temperature

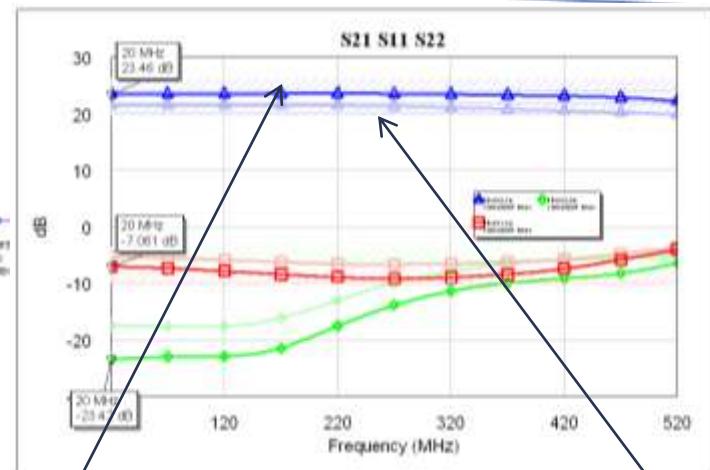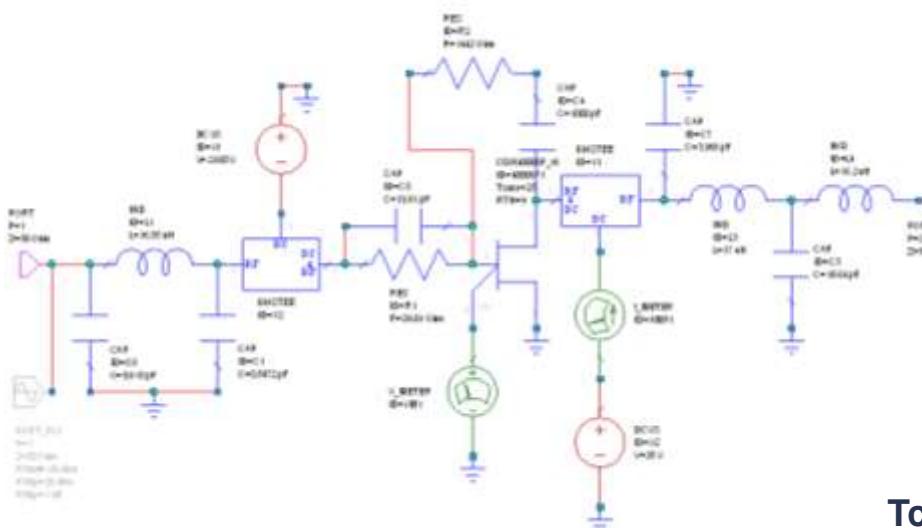



Tcase=-40C

Tcase=150C

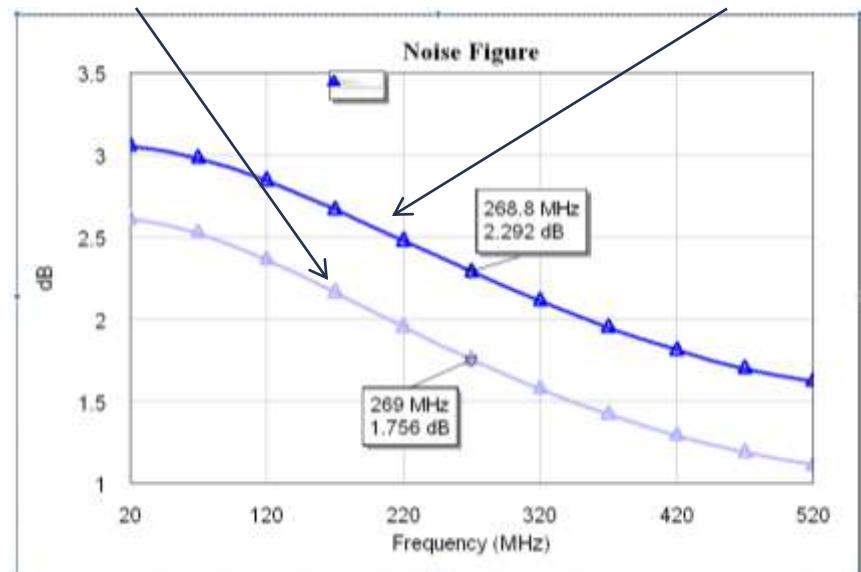Noise parameters (as well as other Parameters) are temperature dependent as shown aside for a CGH40006P based amplifier operating from 20 MHz to 520 MHz






# 0.4um GaN HEMT Noise Model

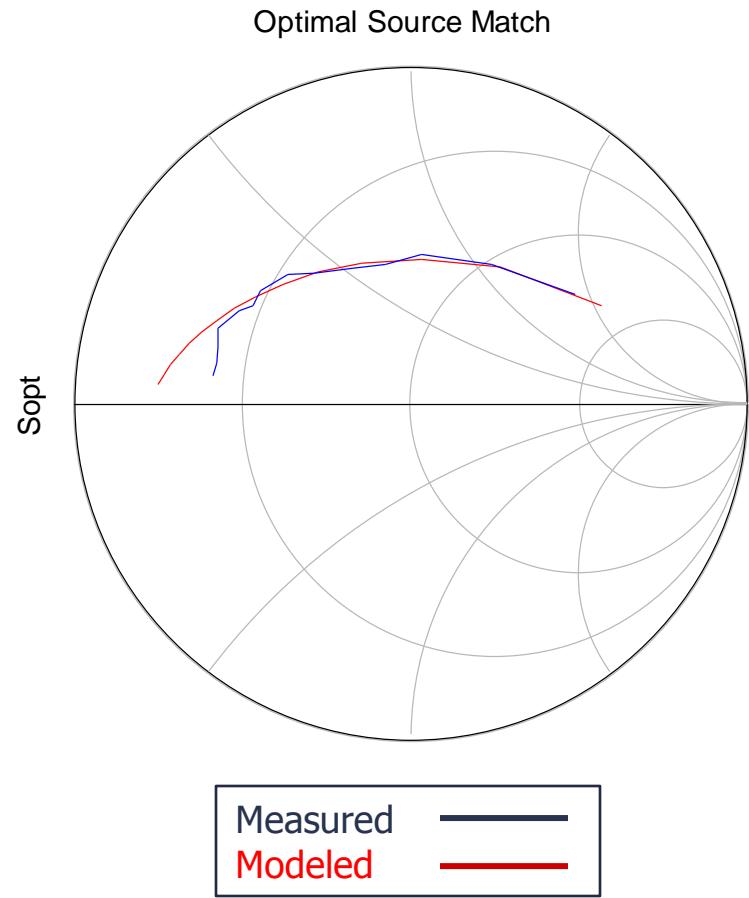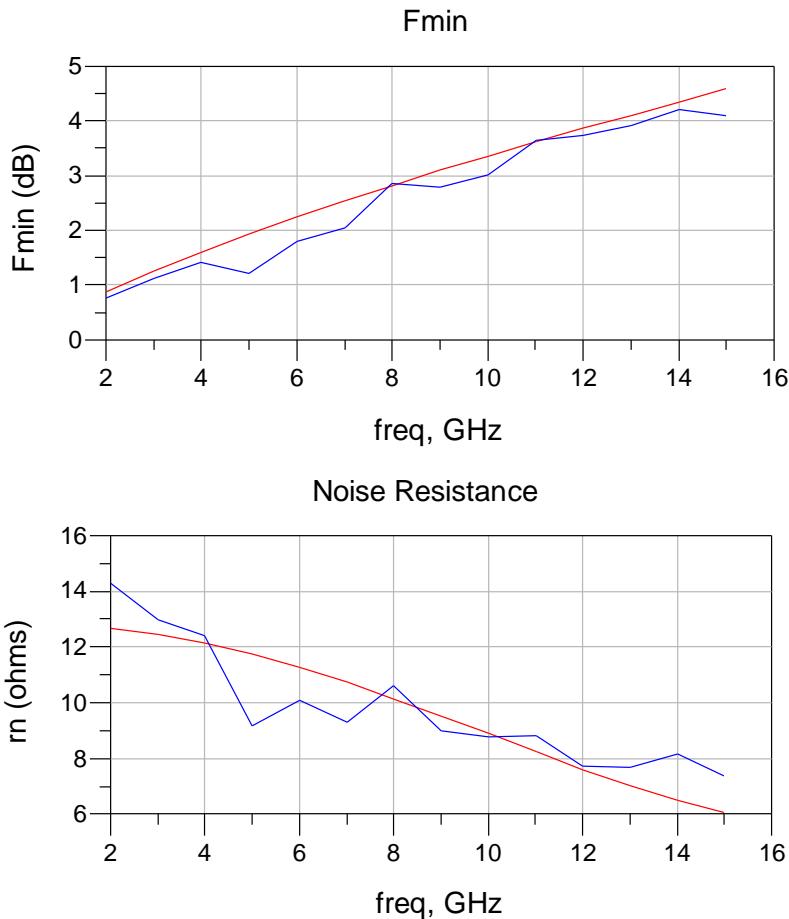




- Good model agreement with measured data

# High Dynamic Range GaN HEMT LNA

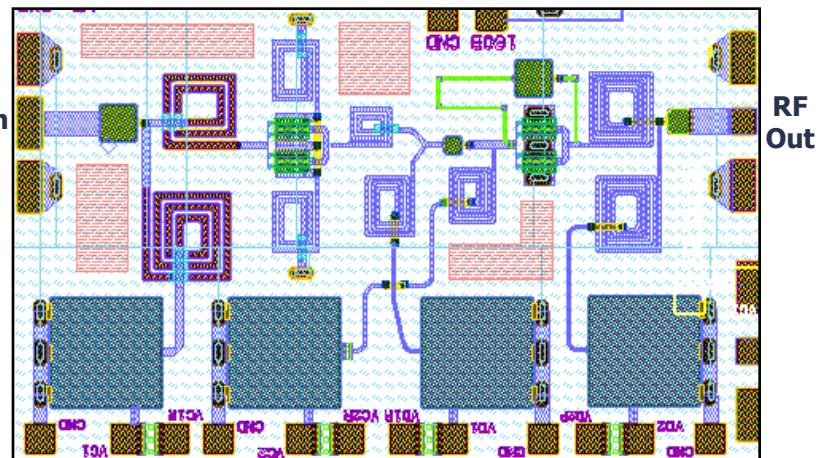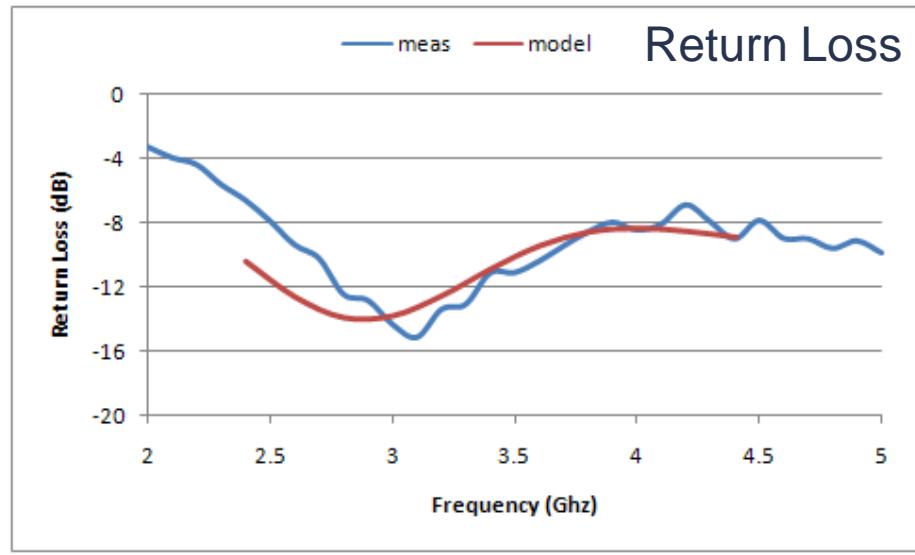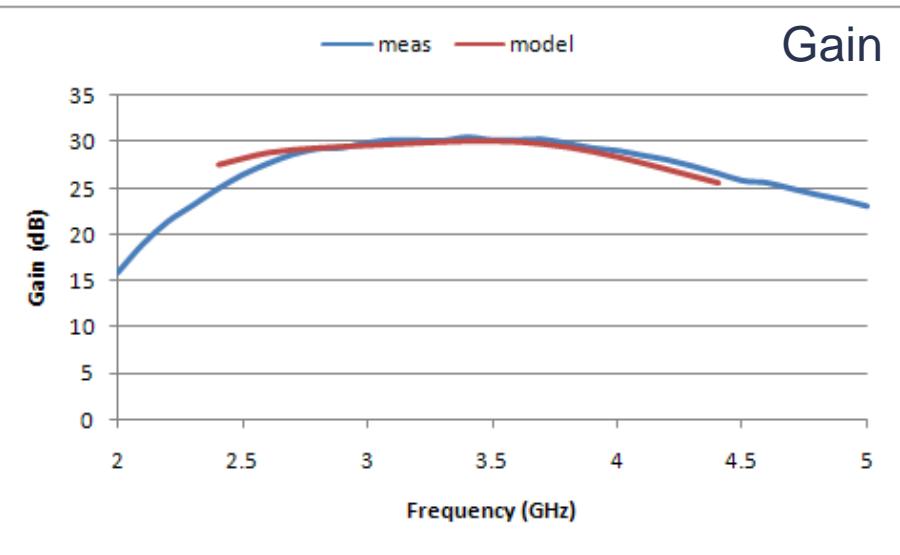

- $V_D = 24V$
- 2-stage LNA
- 30 dB Gain
- 1.7mm wide by 2.7mm
- Excellent Modeled vs. Measured Performance


# High Dynamic Range GaN HEMT LNA

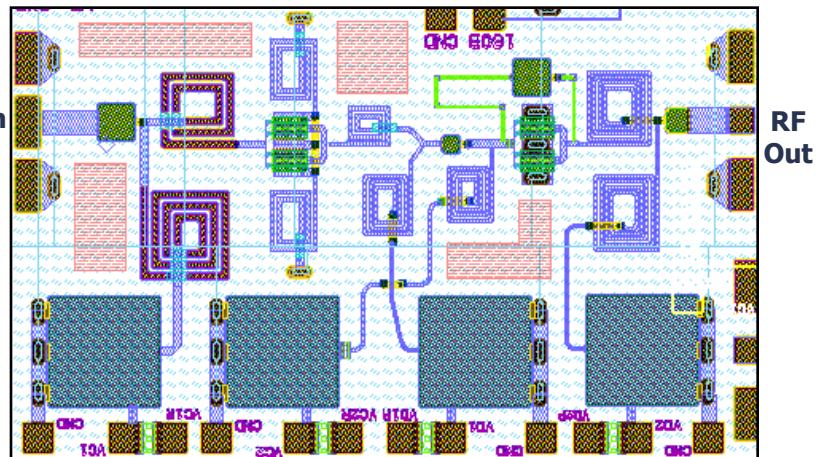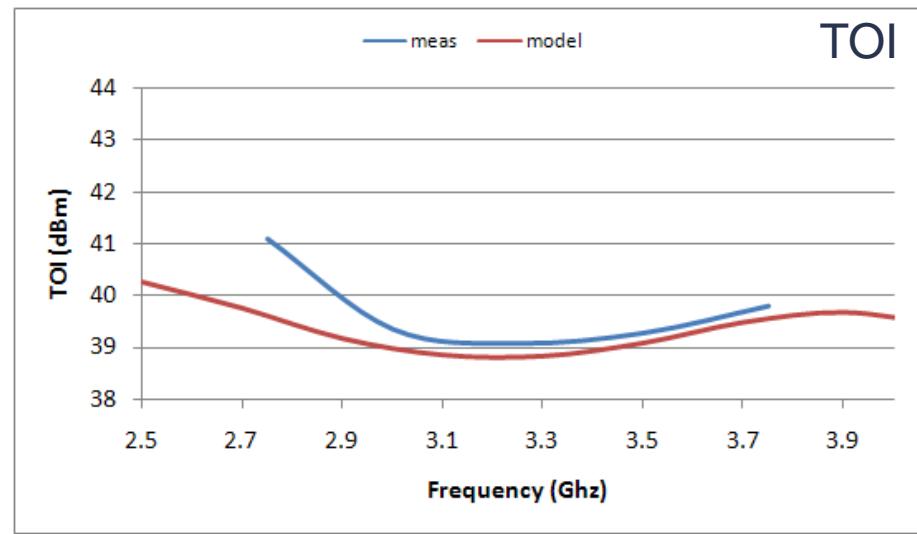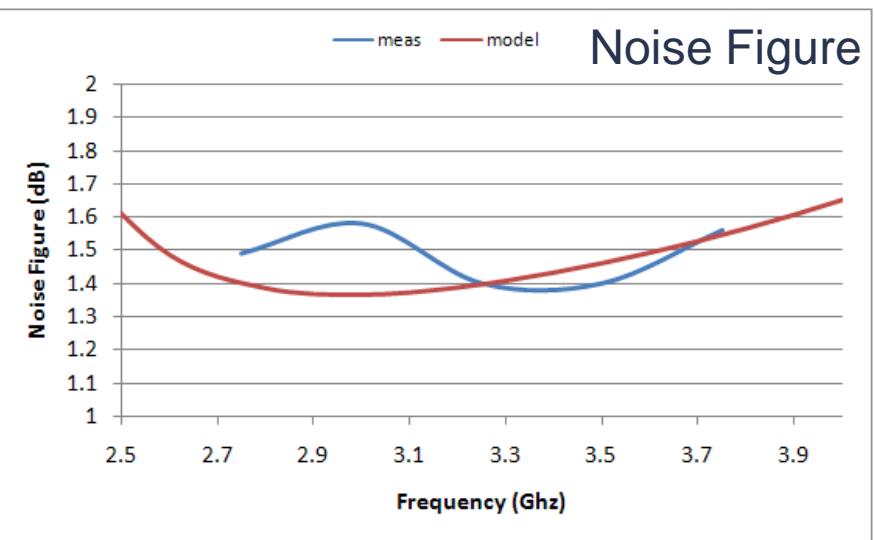


- $V_D = 24V$
- 2-stage LNA
- High Input TOI  $\sim 10$  dBm
- 1.7mm wide by 2.7mm

# **Examples of Package Models**

# 440166 Package Model for CGH40010F

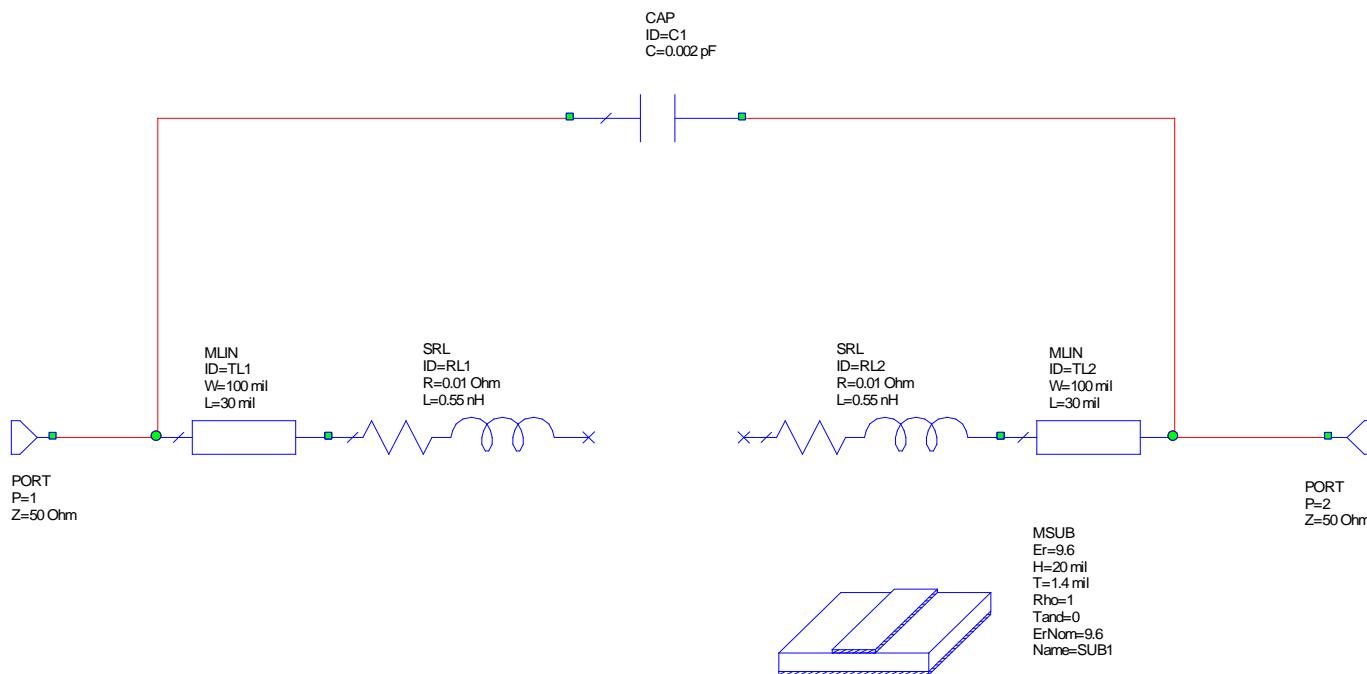

# 440193 Package Model for CGH27060F

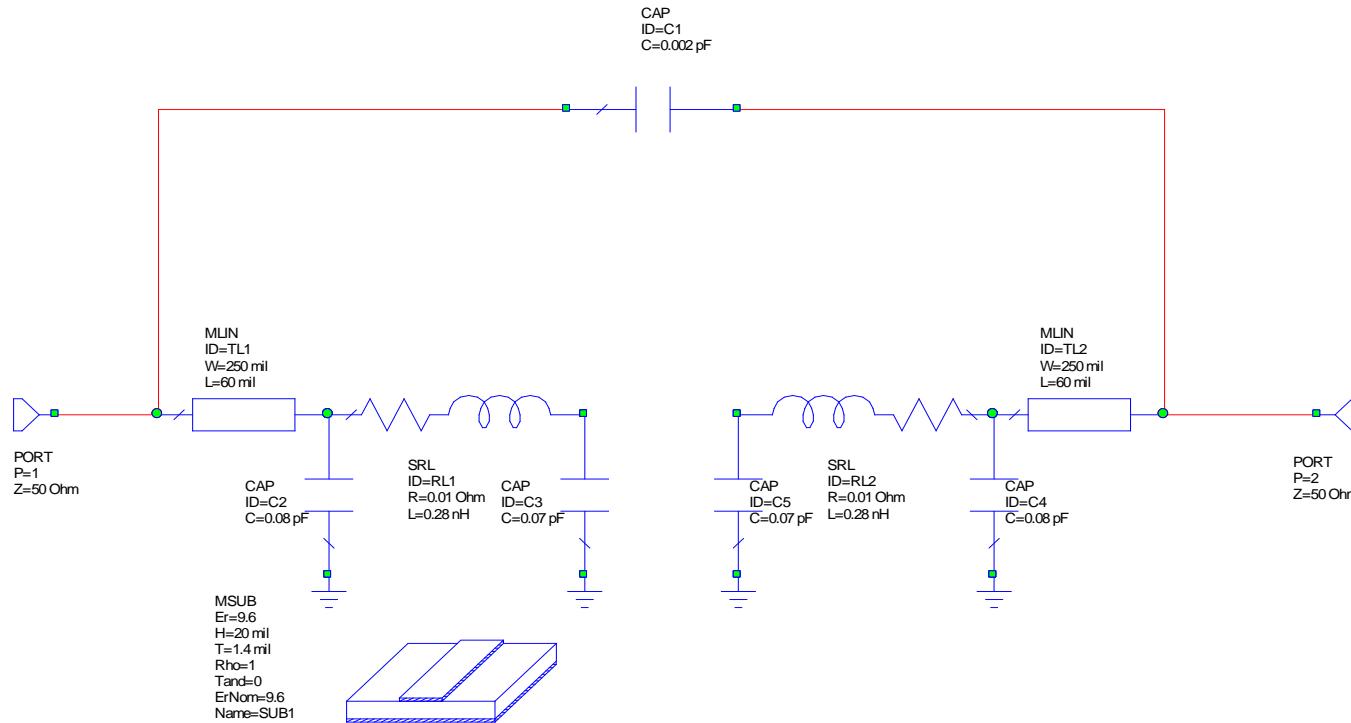

# **Design Examples**



# **Example 1**

## **Basics**


# Basic uses for large-signal models

- DC characteristics
- Generation of s-parameters at different bias points
- GMAX, MSG and K factor
- Generation of source and load pull contours
- AM to AM and AM to PM
- Effects of transistor self-heating
- Harmonic terminations and harmonic analysis

# Generating I-V Curves

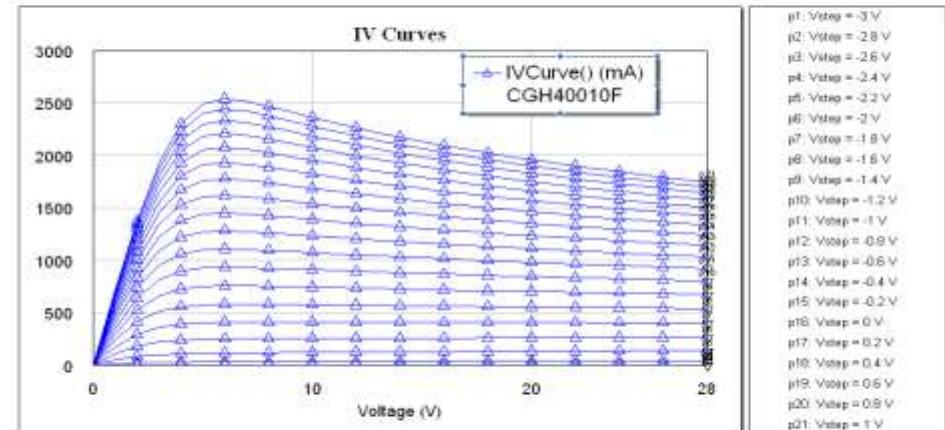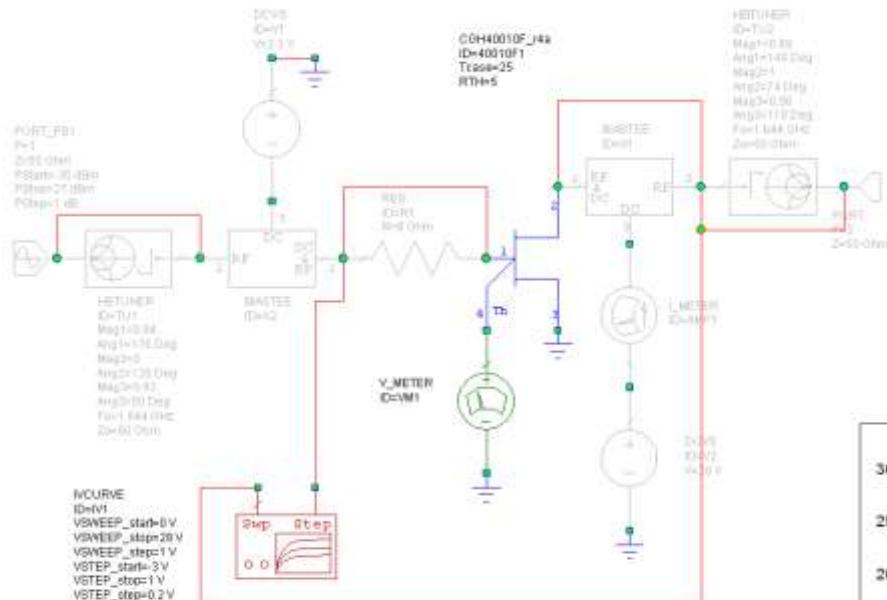

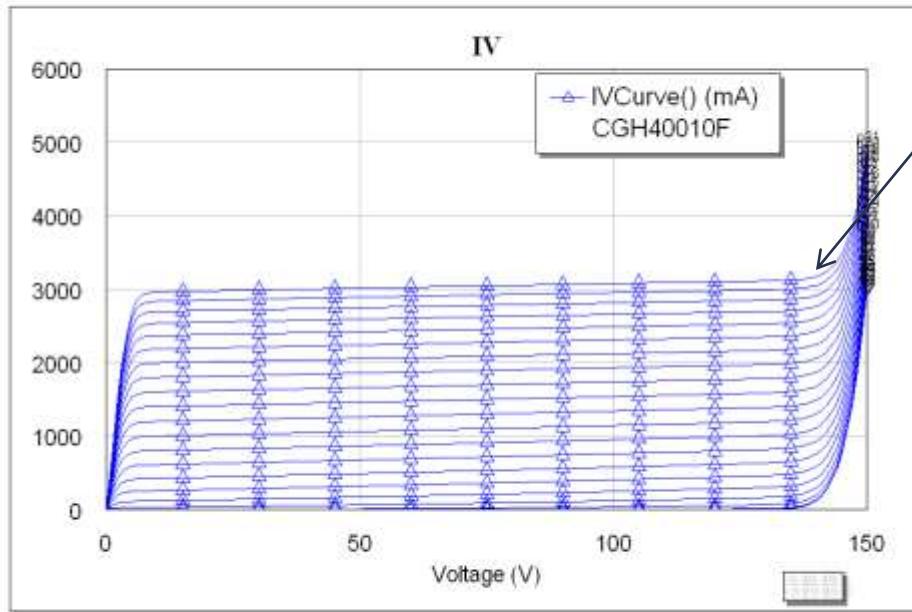
# IV Curves showing Breakdown and Effect of Self-Heating




Self-Heating Disabled

Drain to source breakdown

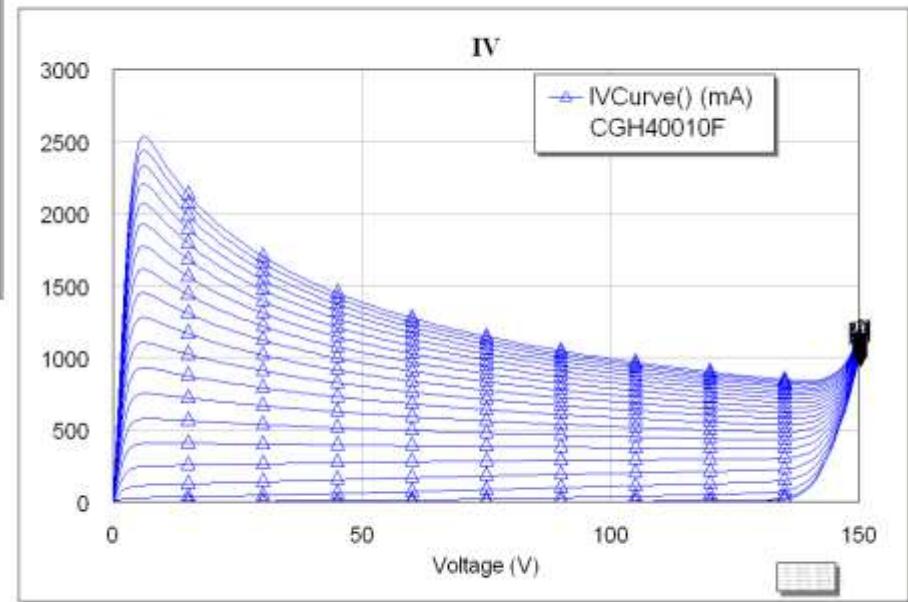

Self-Heating Enabled


# Generating s-parameters

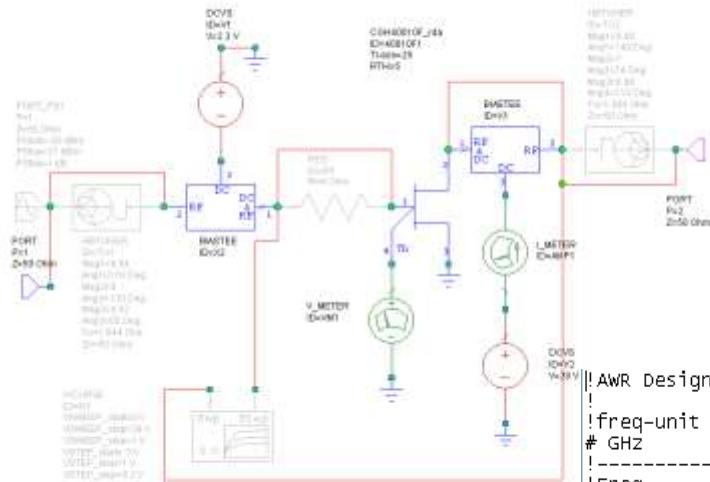


AWR Design Environment (4254) wed Apr 29 14:40:51 2009

#	freq-unit	param-type	data-format	keyword	impedance-ohms			
	GHz	S	MA	R	50			
1	Freq	Mags11	Angs11	Mags21	Angs21	Mags12	Angs12	Mags22
0.5	0.89226	-129.82	17.092	105.62	0.034264	18.391	0.39874	-102.94
0.75	0.87939	-148.62	12.022	92.777	0.035969	6.9418	0.36438	-120.12
1	0.87458	-159.87	9.1924	83.586	0.036408	-0.83357	0.35651	-130
1.25	0.87269	-167.74	7.415	76.034	0.036374	-6.9488	0.36003	-136.39
1.5	0.87214	-173.85	6.2022	69.352	0.036099	-12.166	0.36933	-141.01
1.75	0.87226	-178.95	5.3245	63.19	0.035673	-16.827	0.38183	-144.73
2	0.87278	176.56	4.6613	57.368	0.03514	-21.105	0.3961	-147.98
2.25	0.87352	172.46	4.1436	51.783	0.034524	-25.095	0.41128	-151
2.5	0.87438	168.6	3.7292	46.371	0.033841	-28.852	0.42676	-153.93
2.75	0.87529	164.89	3.3908	41.088	0.033104	-32.409	0.44214	-156.84
3	0.87619	161.26	3.1102	35.903	0.032322	-35.785	0.45709	-159.77
3.25	0.87704	157.66	2.8744	30.792	0.031505	-38.99	0.47141	-162.74
3.5	0.87782	154.07	2.6742	25.734	0.030659	-42.029	0.48492	-165.76
3.75	0.8785	150.43	2.5029	20.711	0.029792	-44.903	0.49752	-168.86
4	0.87906	146.74	2.3552	15.707	0.028909	-47.606	0.50913	-172.02
4.25	0.87949	142.96	2.2272	10.705	0.028018	-50.13	0.51969	-175.27
4.5	0.87978	139.08	2.1157	5.6904	0.027124	-52.463	0.52917	-178.61
4.75	0.87992	135.07	2.0182	0.64709	0.026236	-54.59	0.53757	177.95
5	0.87994	130.92	1.9326	-4.4406	0.025361	-56.489	0.54488	174.41
5.25	0.87982	126.61	1.8573	-9.5885	0.024511	-58.138	0.55111	170.74
5.5	0.8796	122.11	1.7908	-14.813	0.023698	-59.511	0.55628	166.93
5.75	0.87928	117.43	1.7319	-20.13	0.022939	-60.582	0.56042	162.97
6	0.87892	112.52	1.6793	-25.556	0.022252	-61.331	0.56356	158.84


# GMAX, MSG and K Factor

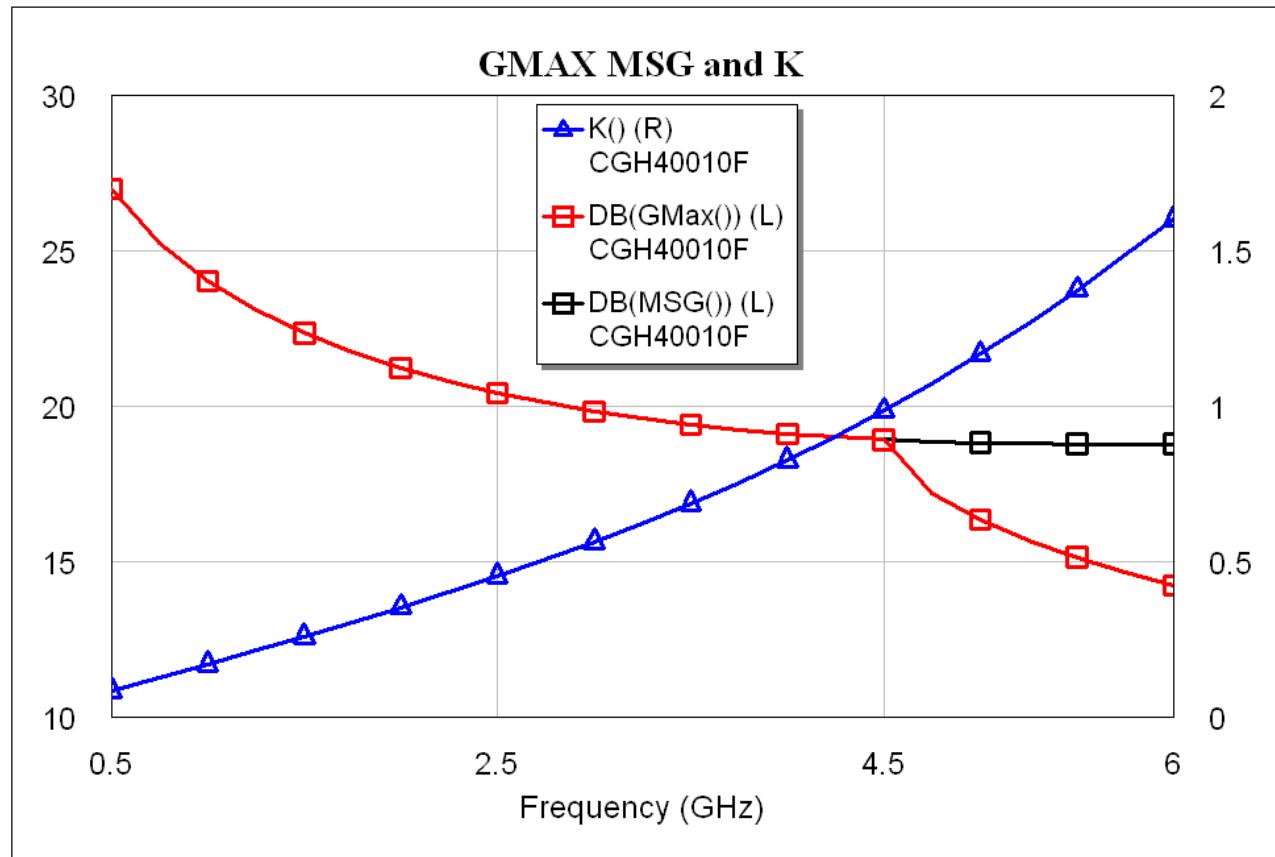

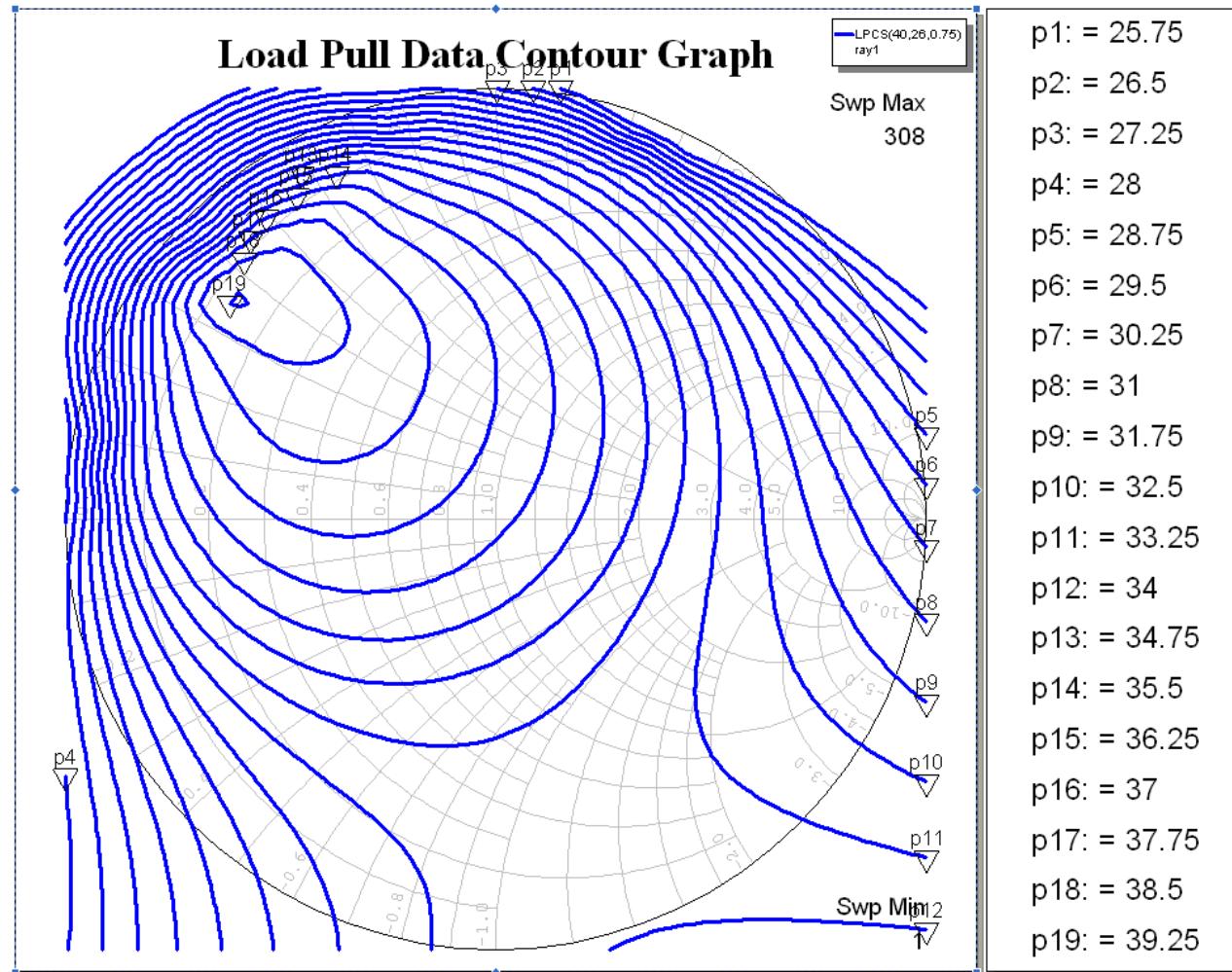
# Generation of source and load pull contours



# AM to AM and AM to PM

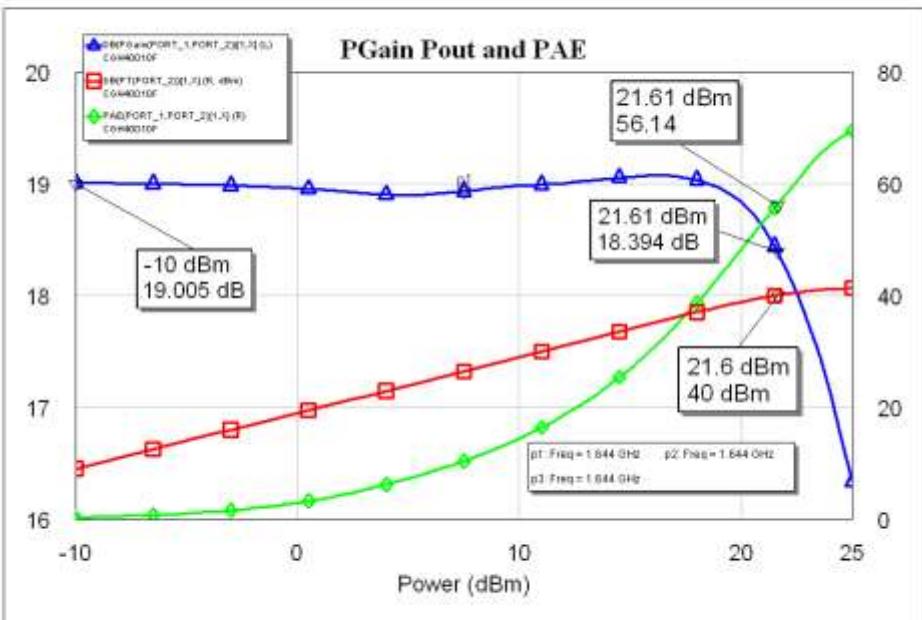


AM to AM Performance

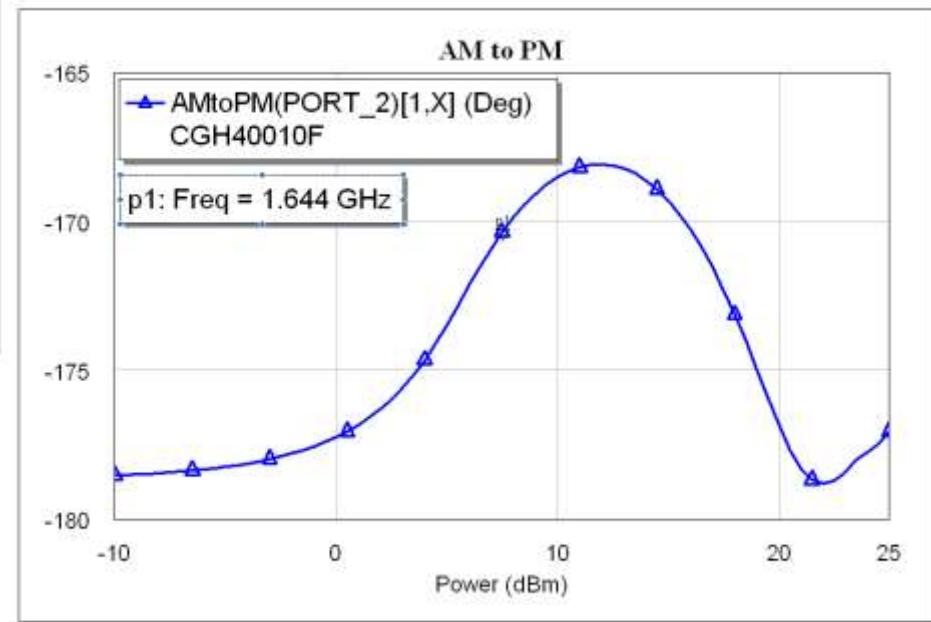


AM to PM Performance

# Effects of transistor self-heating

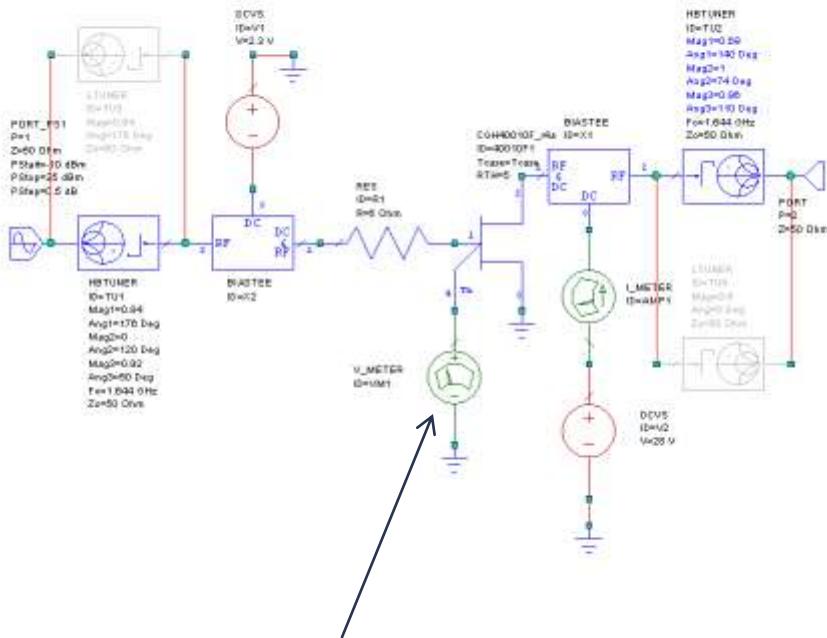


Thermometer

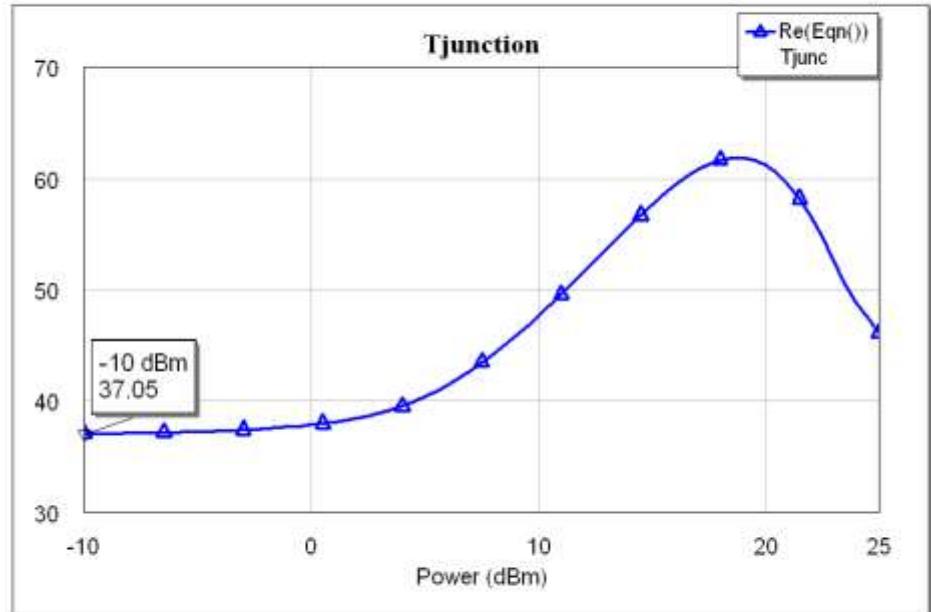

$$T_{\text{junction}} = T_{\text{rise}} + T_{\text{case}}$$


Tcase set to 25 C

# Effect of Self-heating engine in model

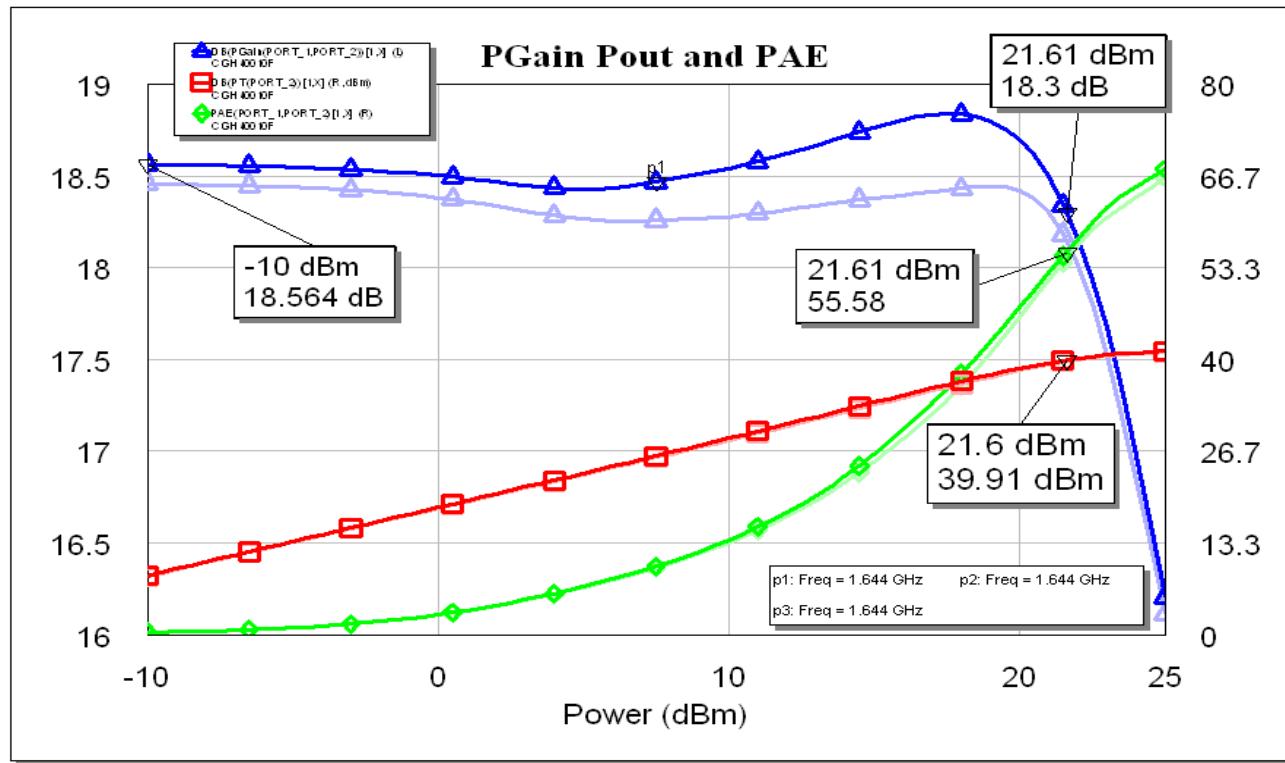


Bold plots are with self-heating turned off

# Harmonic Terminations

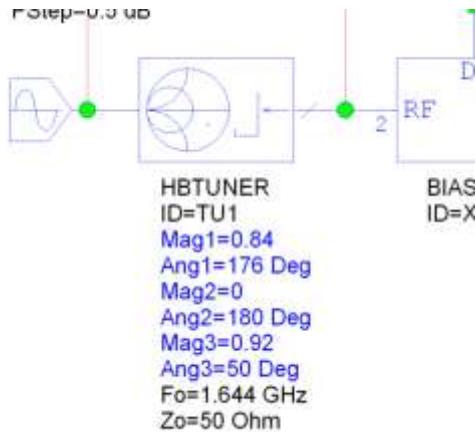


Gate termination

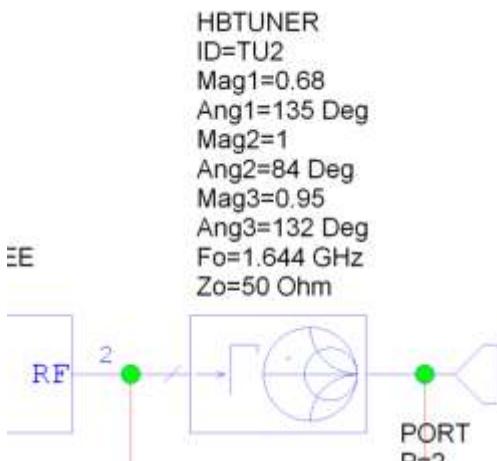


Drain termination

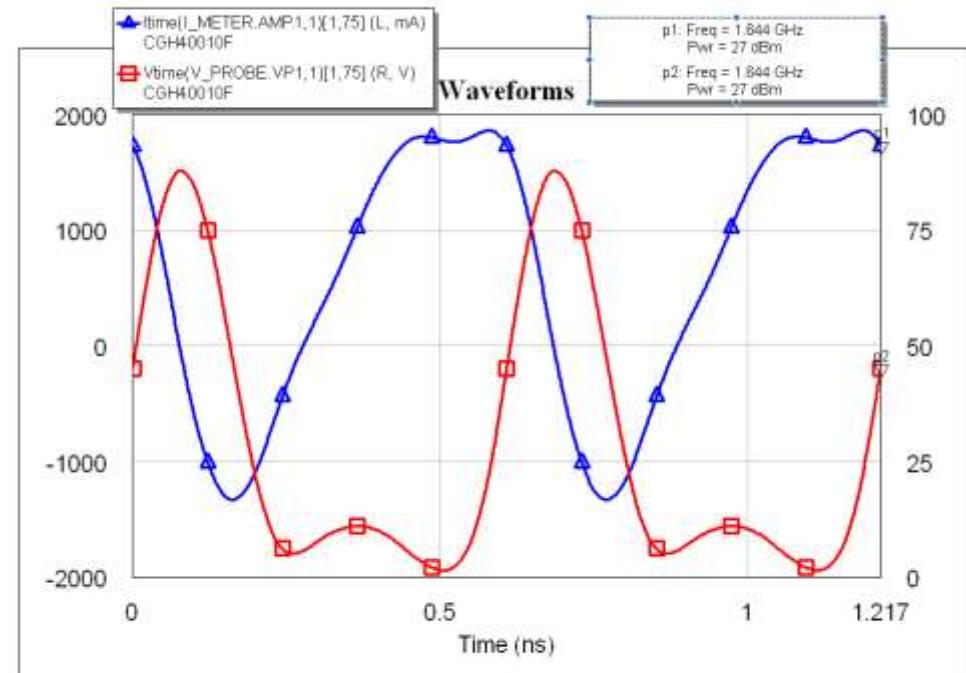$P_{out} = 41 \text{ dBm}$   
4.5 dB into compression  
Drain Efficiency = 75%



Red is drain voltage; Blue is drain current

# Output Signal Harmonic Analysis

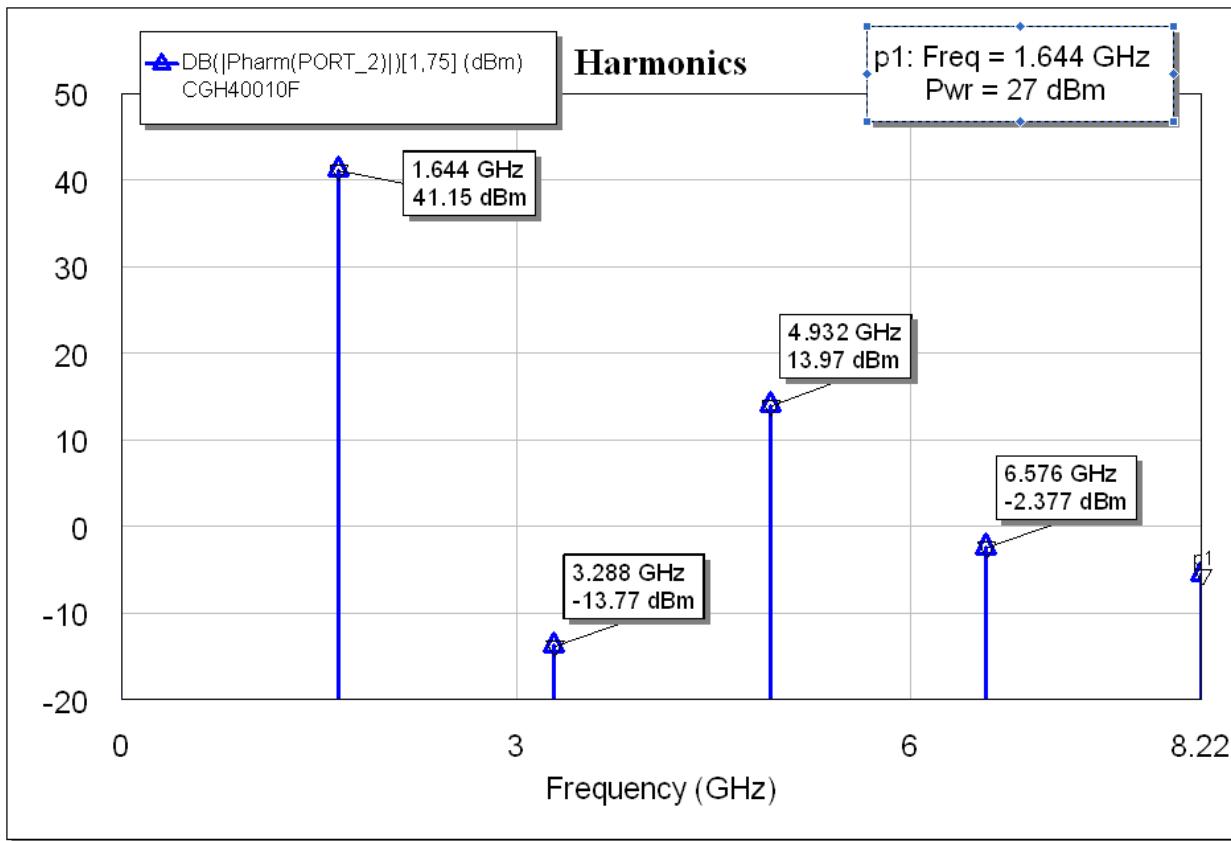


The plot illustrates the frequency spectrum at the output of the amplifier, captured from DC to 8.22 GHz. The harmonic suppressions at the output for the 2nd and 3rd harmonics are -55dBc and -27dBc respectively, indicating that most of the harmonics are re-injected into the PA as expected.

## **Example 2**

# **500 to 2700 MHz Amplifier using Cree CGH40010F**

# 500 to 2700 MHz Amplifier using Cree CGH40010F

Lossy Match

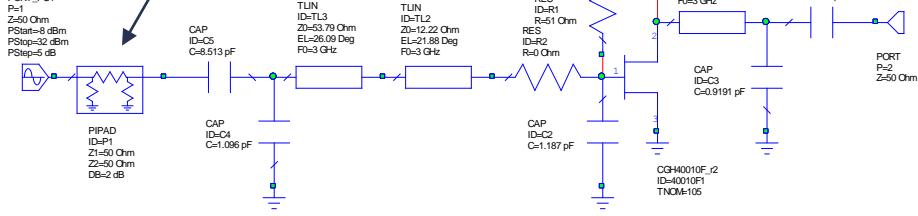


PRELIMINARY



## CGH40010
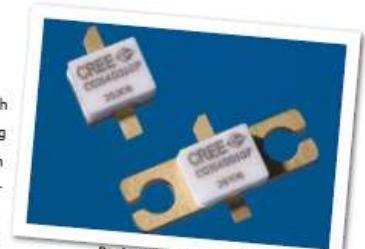
### 10 W, RF Power GaN HEMT

Cree's CGH40010 is an unmatched, gallium nitride (GaN) high electron mobility transistor (HEMT). The CGH40010, operating from a 28 volt rail, offers a general purpose, broadband solution to a variety of RF and microwave applications. GaN HEMTs offer high efficiency, high gain and wide bandwidth capabilities making the CGH40010 ideal for linear and compressed amplifier circuits. The transistor is available in both screw-down, flange and solder-down, pill packages.



Package Types: 440166, & 440196  
PN's: CGH40010F & CGH40010P

## FEATURES

- Up to 4 GHz Operation
- 16 dB Small Signal Gain at 2.0 GHz
- 14 dB Small Signal Gain at 4.0 GHz
- 13 W typical  $P_{3dB}$
- 65 % Efficiency at P3dB
- 28 V Operation

## APPLICATIONS



- 2-Way Private Radio
- Broadband Amplifiers
- Cellular Infrastructure
- Test Instrumentation
- Class A, AB, Linear amplifiers suitable for OFDM, W-CDMA, EDGE, CDMA waveforms



Courtesy: L3 Communications  
TRL Technology UK

CREE

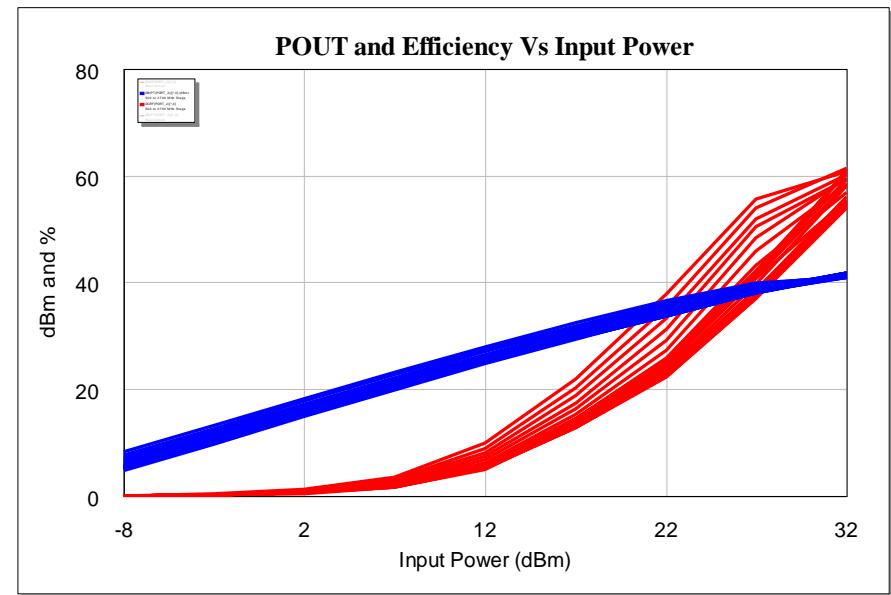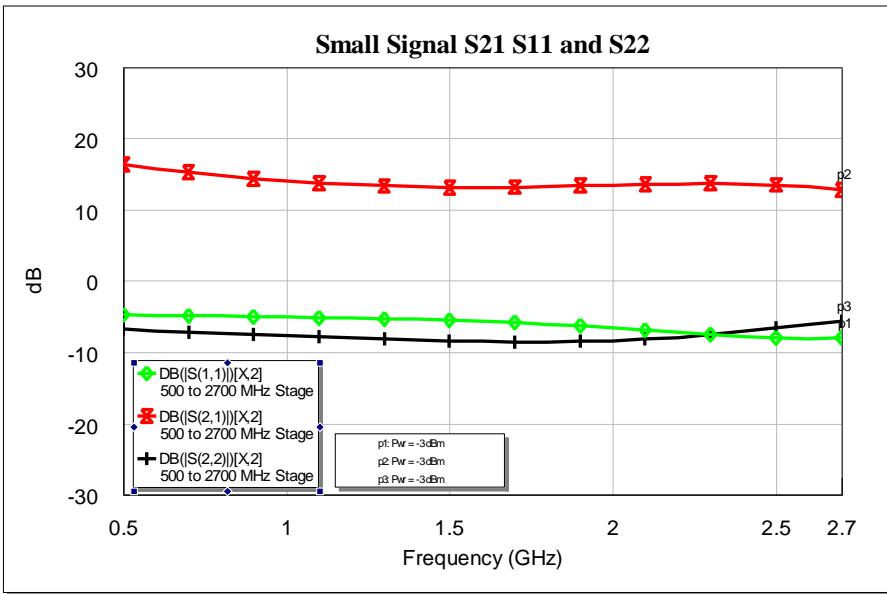
# Simulated Performance of 500 to 2700 MHz GaN HEMT PA




- Worst Case Heat Dissipation is 9 watts
- Theta-jc of packaged transistor is 5 deg C/watt
- Max. channel temperature at 85 deg C case is 130 deg C.
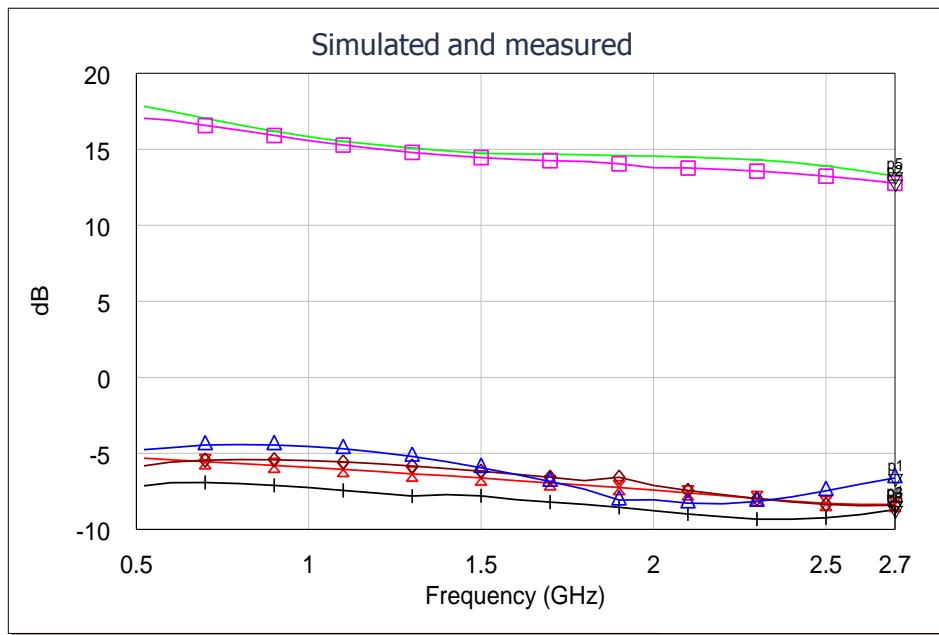
# Measured Performance of 500 to 2700 MHz GaN HEMT PA

- Excellent agreement between simulations and measurements
- Measured efficiencies between 50 and 78% over the band



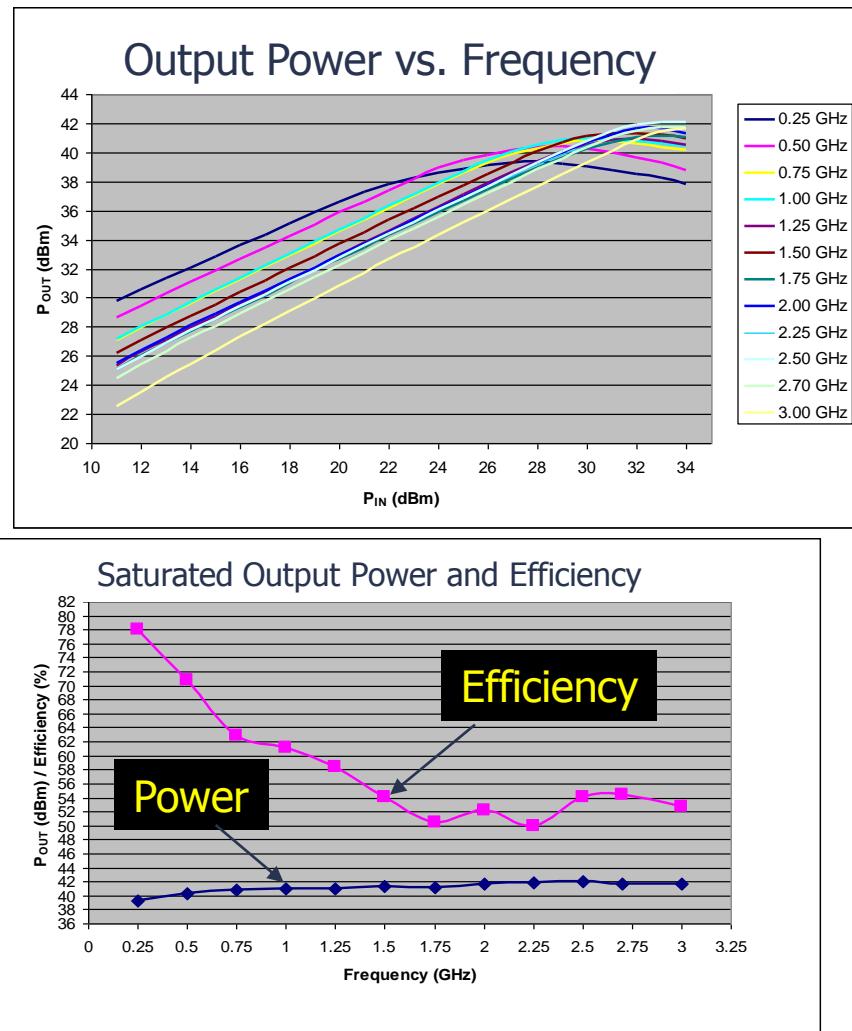Courtesy: L3 Communications  
TRL Technology UK




# **Example 3**

## **Various Broadband Amplifier Design Approaches**

# Broadband Amplifier Performance
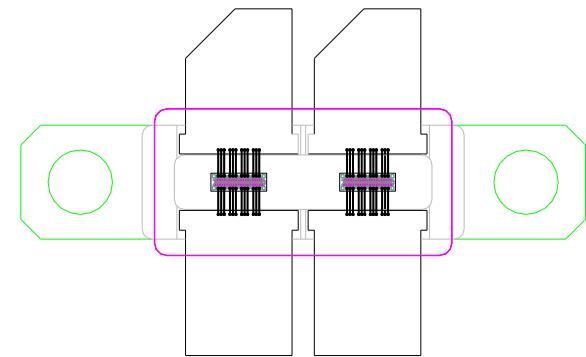
## Trade-Off Analysis - Background



- Broadband (0.8 to 2.2 GHz) push-pull amplifier to provide 100 watts peak power
- Two GaN HEMT die in “Gemini” package
  - HEMTs attached to composite material shims within Cu-Mo-Cu package
- Study drain efficiencies over the band and impact on thermal management
  - Comparison of different matching approaches and termination impedances




Theta-jc is 1.1 deg C/watt
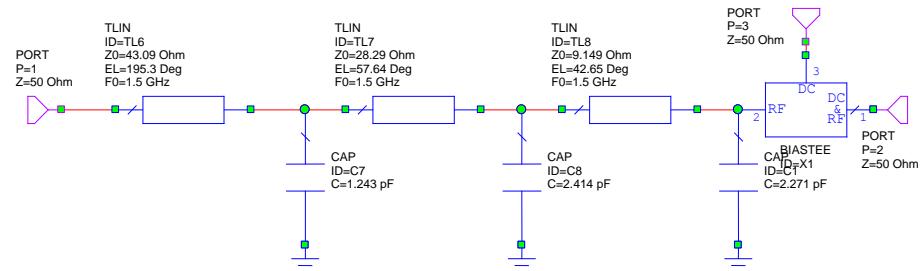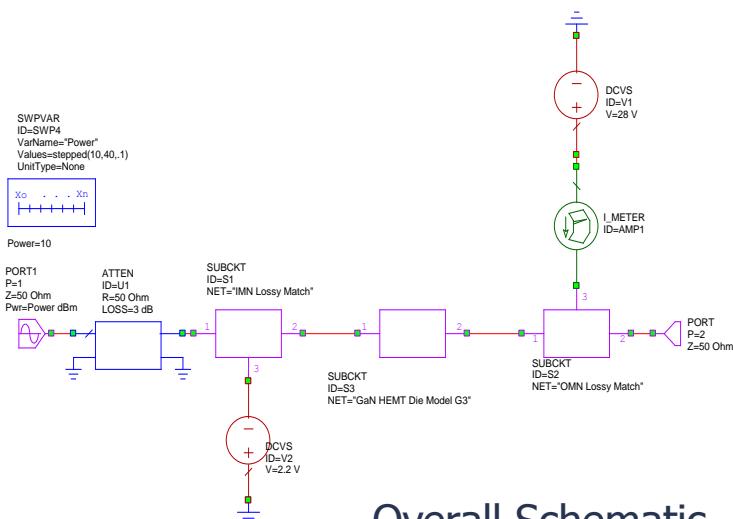
# Basic Amplifier

- Different matching topologies
  - Drain-to-Gate Feedback
  - Lossy Match
  - Multi-section reactive
  - Lossy Match with Feedback
- Concentrate on Lossy Match case




Input Match Schematic

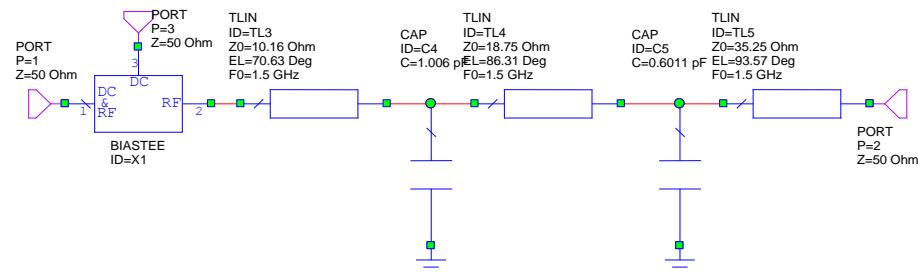

Output Match Schematic

# Simulated Amplifier Performance

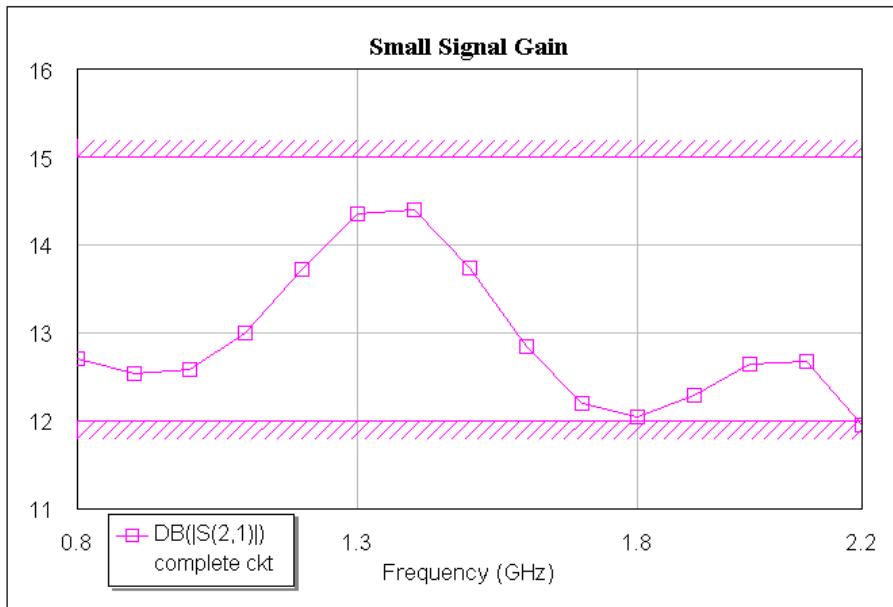

**Small Signal Gain**


Gain =  $13.2 \text{ dB} \pm 0.8 \text{ dB}$

$P_{\text{OUT}}$  = 46 to 59 watts

Drain Efficiency = 49 to 66%

Worst Case Dissipated Heat is 54 watts  
(per transistor)

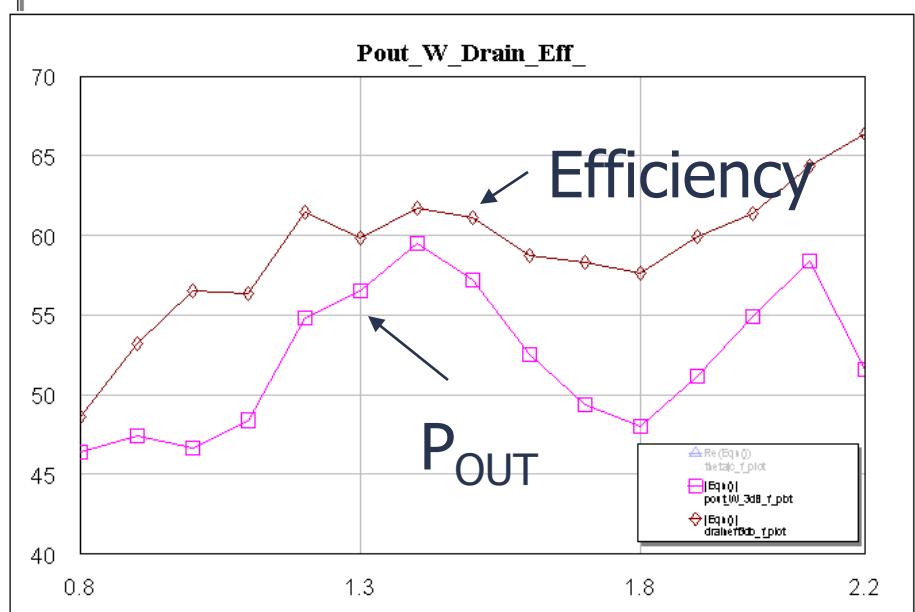
**Output Power at  $P_{3\text{dB}}$  and Drain Efficiency**



# Thermal Performance


- Assuming  $T_J$  limit of 200°C, maximum dissipated heat of 108 watts and  $\theta_{JC}$  of 1.1 deg C/Watt leads to a maximum case temperature of 81 deg C
- The thermal characteristics of the die and the package are very important
  - The design requires a composite material shim such as silver-diamond ( $\theta_{JC} = 550 \text{ W/mK}$ ) mounted on a Super-CMC package flange ( $\theta_{JC} = 370 \text{ W/mK}$ )
- Before full electrical design is completed broadband amplifiers require thermal design even with GaN HEMTs!

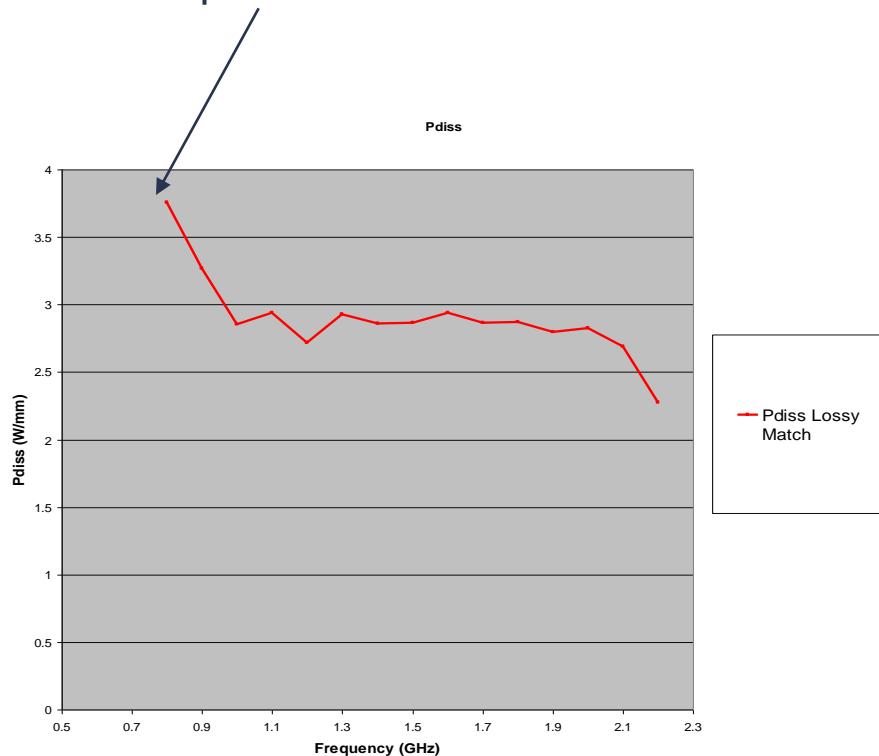3.75 W/mm dissipated  
54 watts per transistor



Dissipated Power as a function of frequency
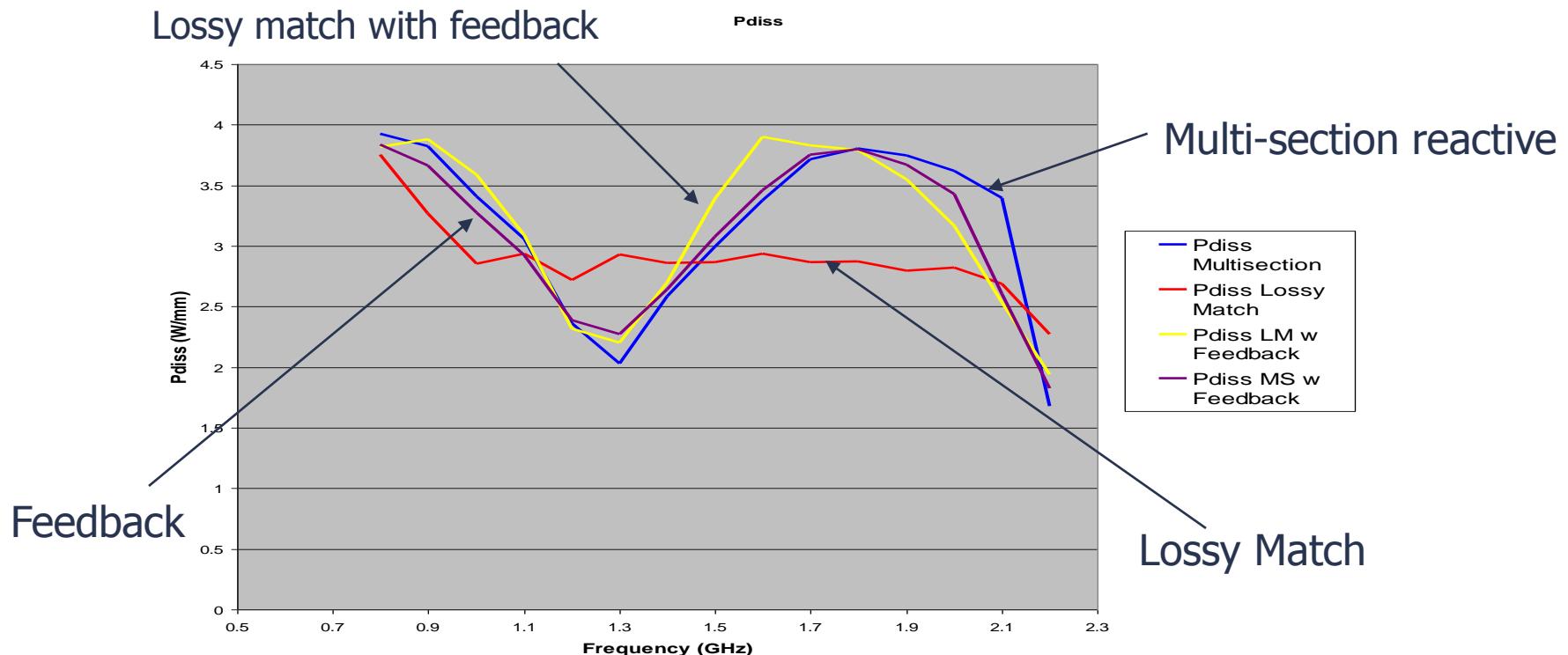
# Comparison of Dissipated Power vs. Frequency for 4 Amplifier Approaches





- Large-Signal Modeling of Broadband Amplifiers invaluable in selecting optimum topology for both electrical and thermal performance

# Measured 0.5 to 2.5 GHz Push-Pull Amplifier Performance



Power out at Device Sat (W)

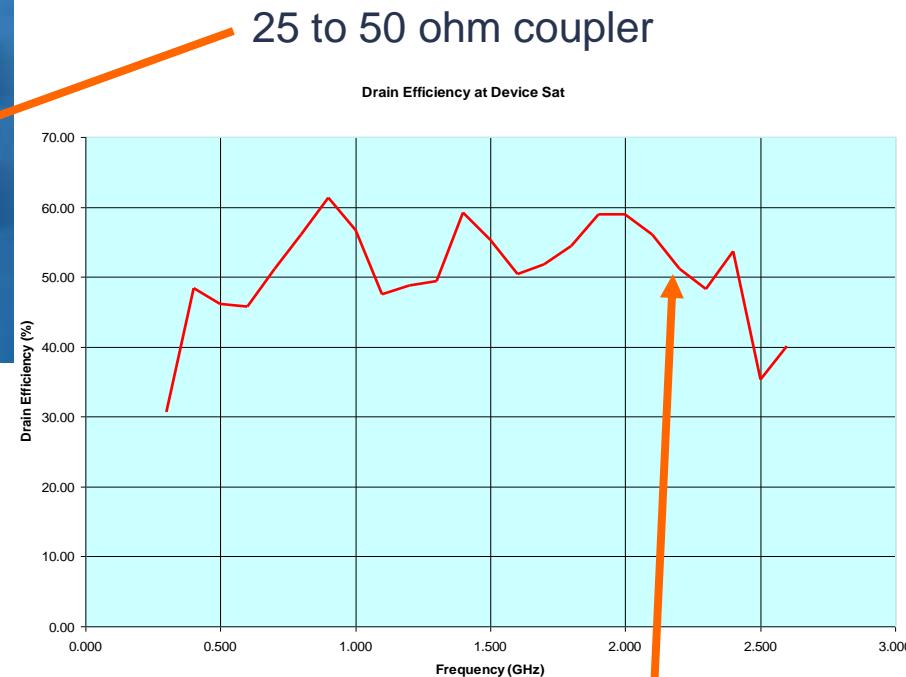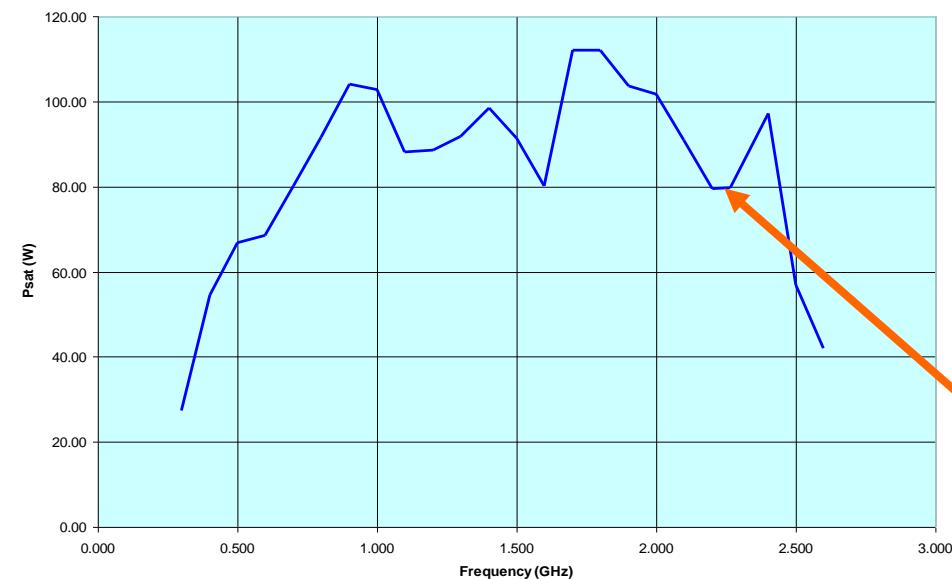

Full amplifier with  
coupler insertion losses  
Average Gain = 15 dB  
Psat > 80 watts and  
Drain Efficiencies > 45%

**CREE**


# **Example 4**

## **2 to 6 GHz Broadband PA using CGH40010F**


# Summary

- 2000 to 6000 MHz amplifier using packaged CGH40010F GaN HEMT transistor
- Design uses GaN HEMT Transistors operating at nominal drain to source rail of 28 volts
- Amplifier designs use transmission lines, open-circuit stubs and capacitors
- Matched to 50 ohm input and output impedances


# Amplifier Schematic

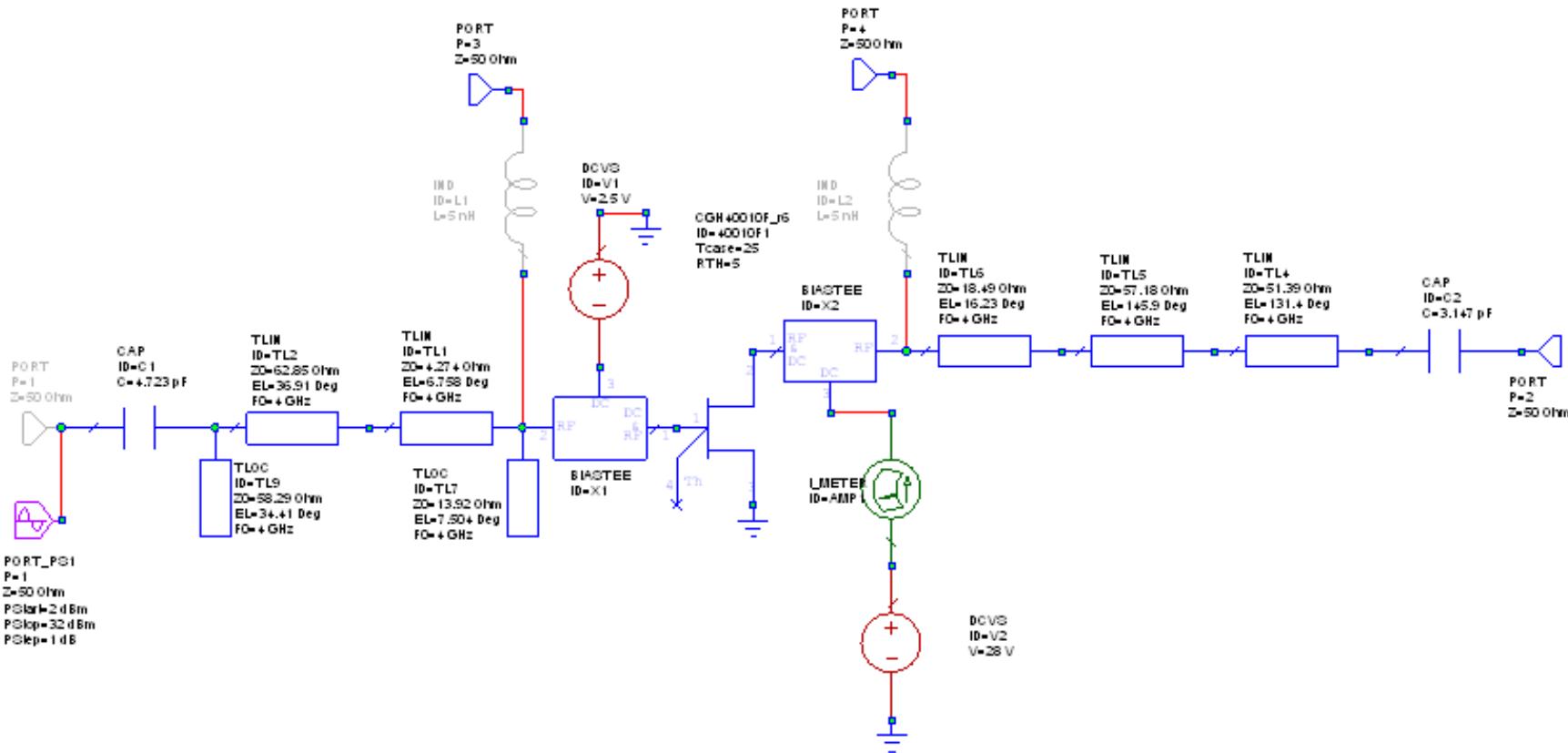

# Detail of Input Match

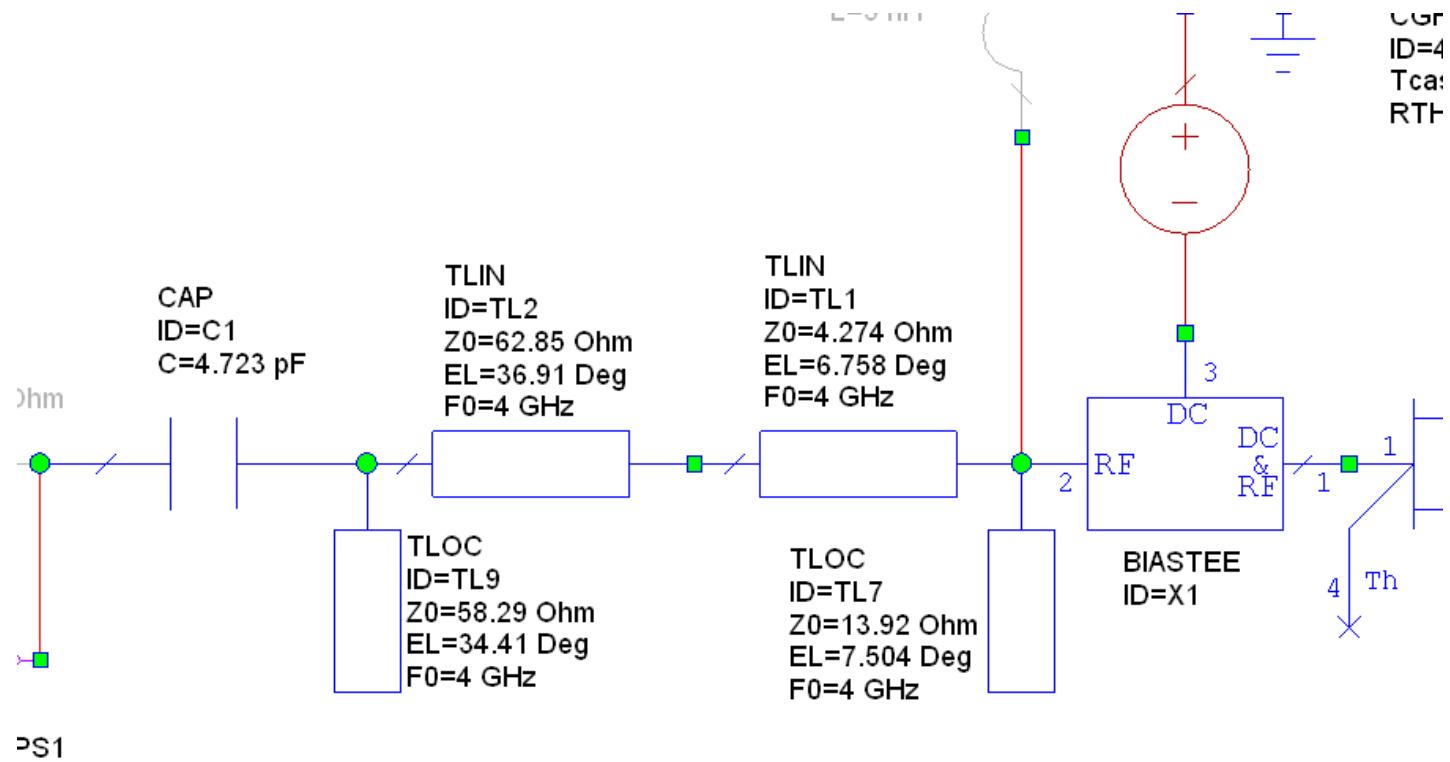


# Detail of Output Match

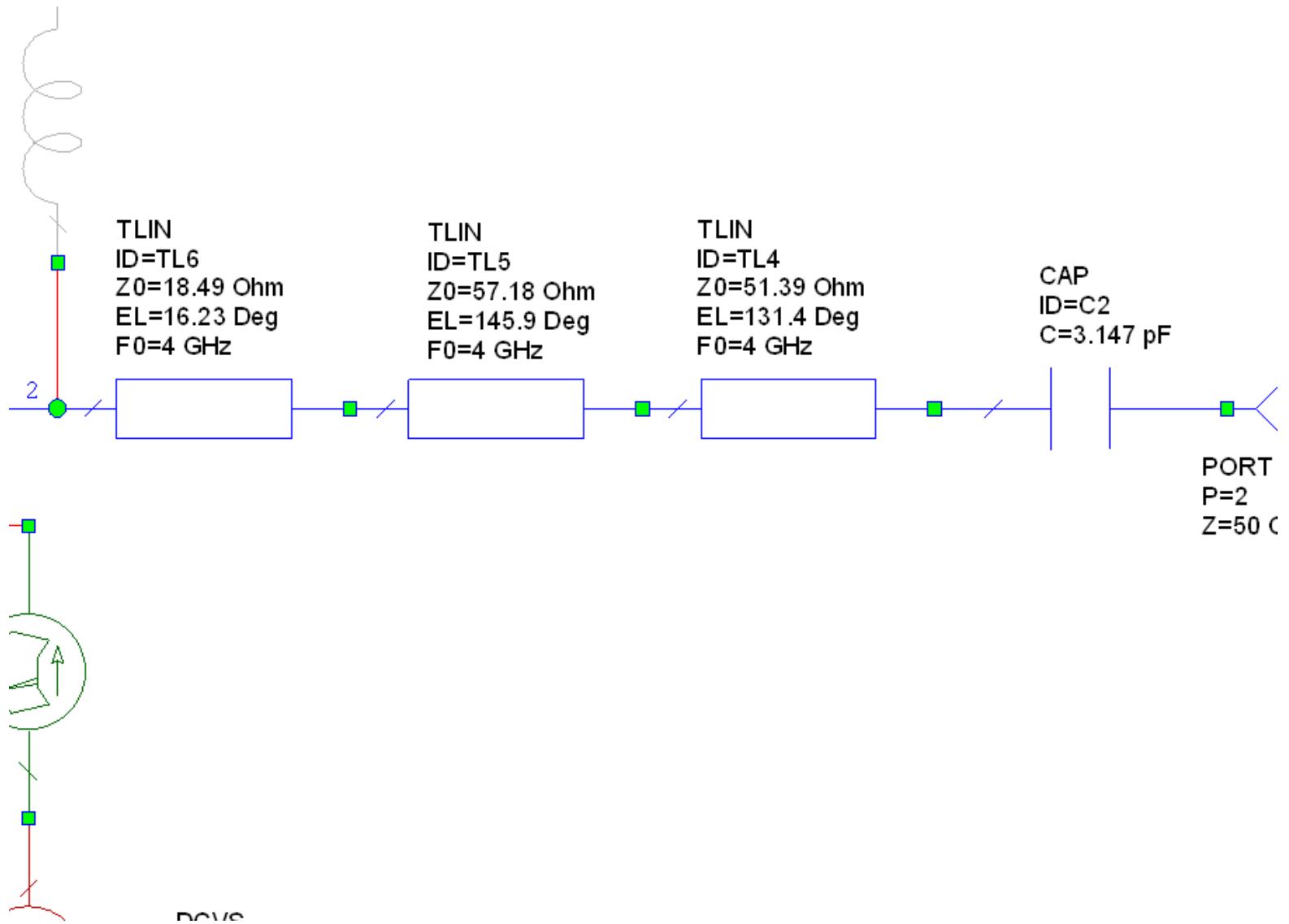


DOVS

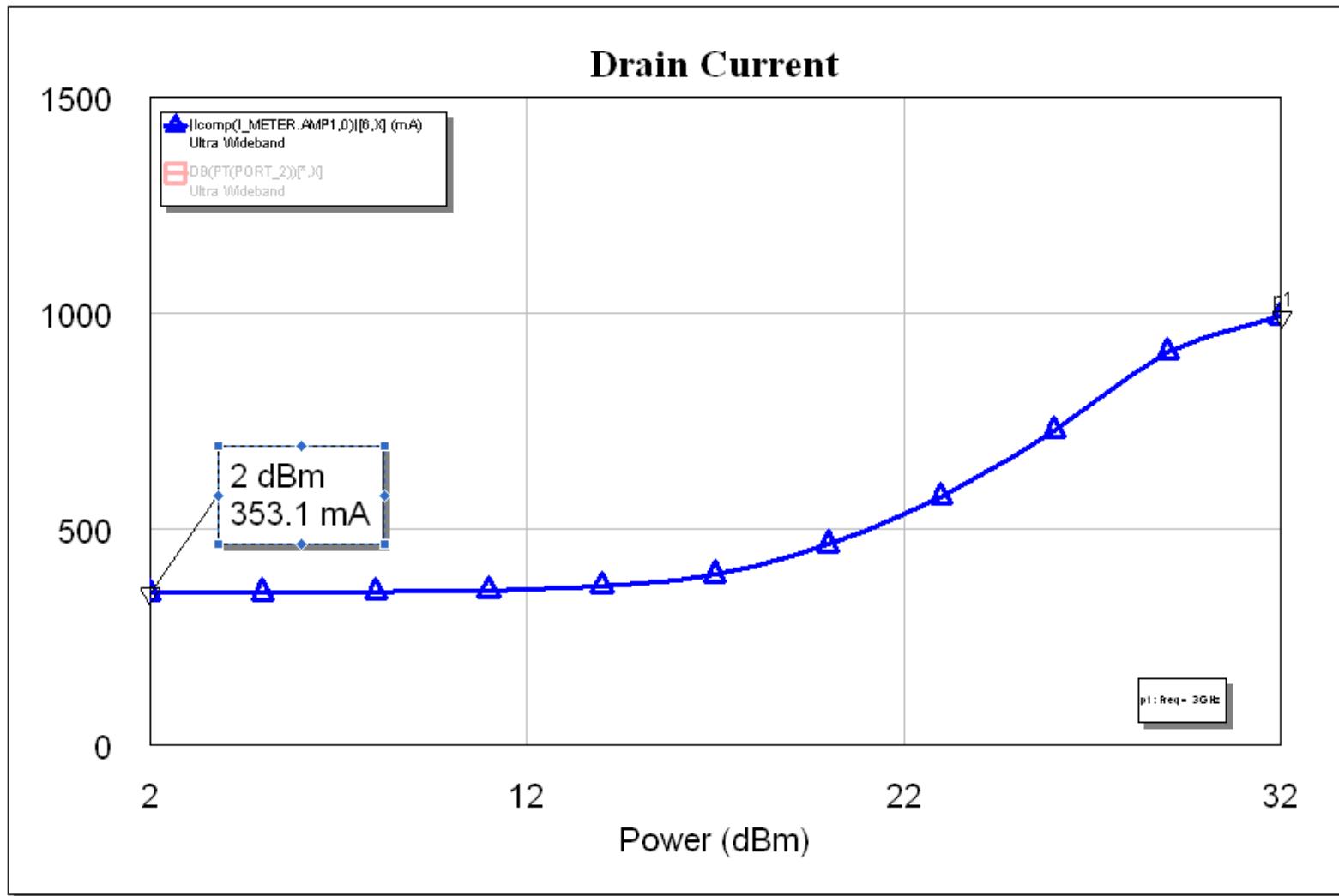
# DC Current versus Input RF power at 3 GHz



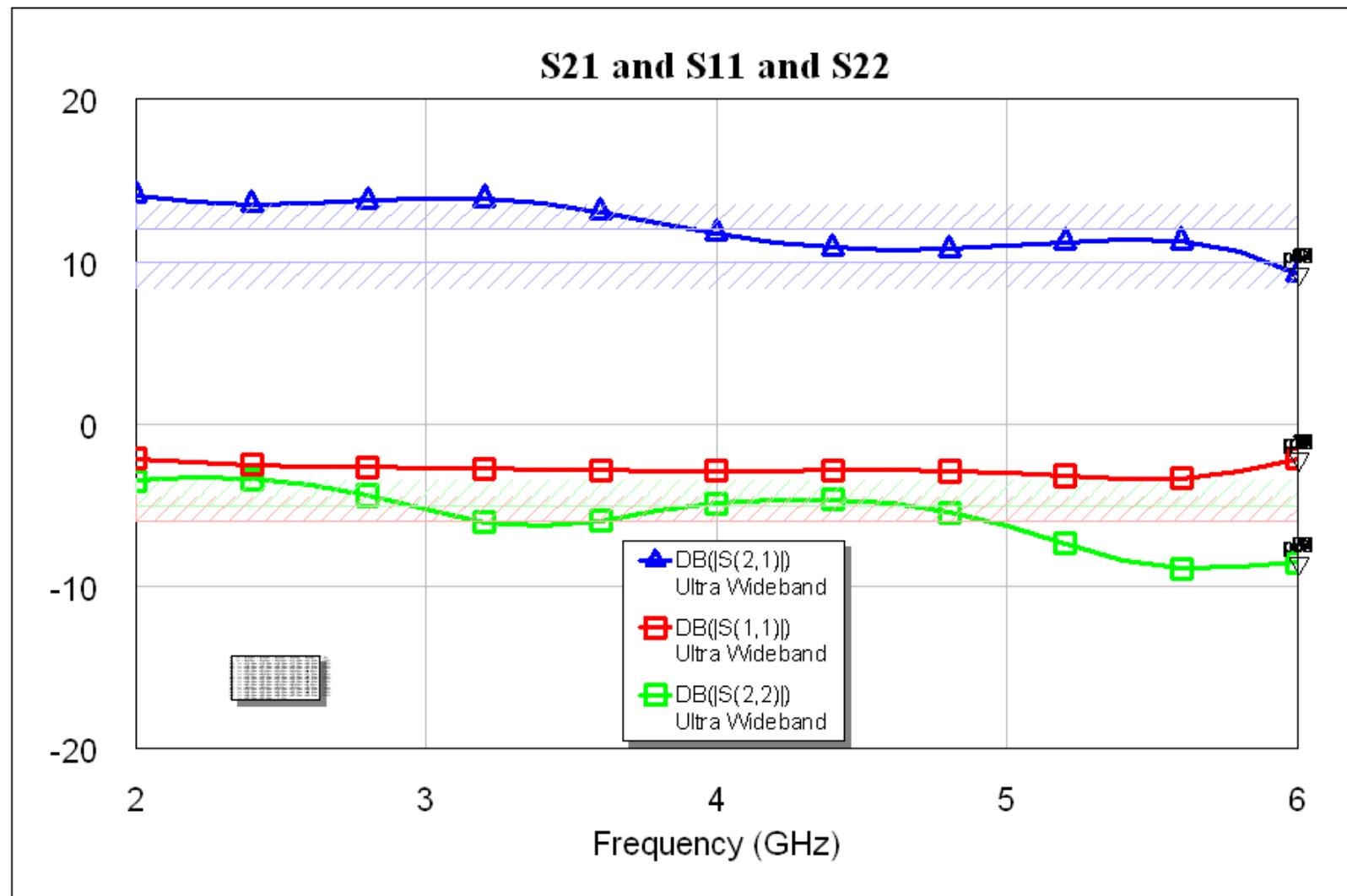
# Small signal gain, input and output return losses




# Output Power and Efficiency at 3.6 GHz

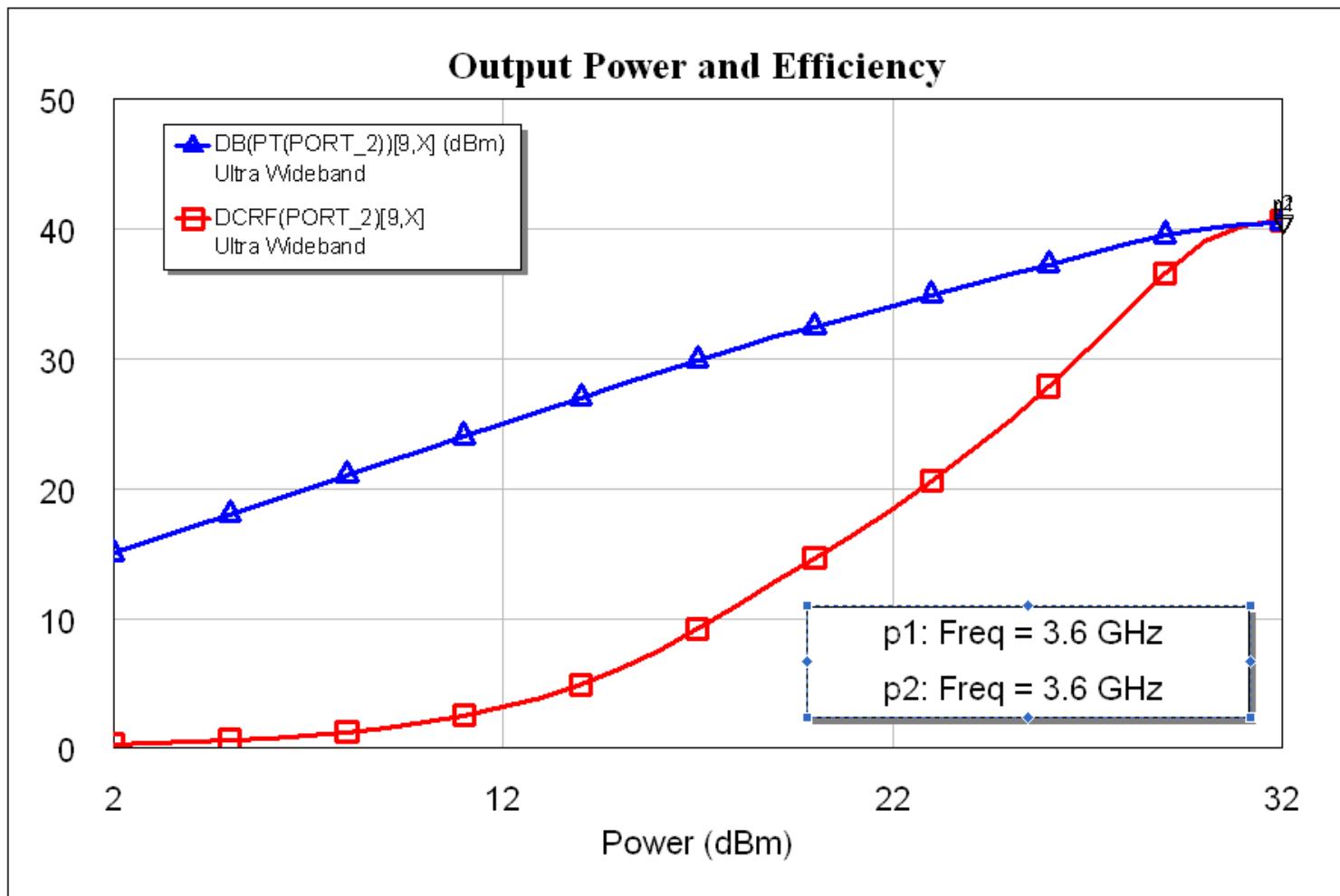
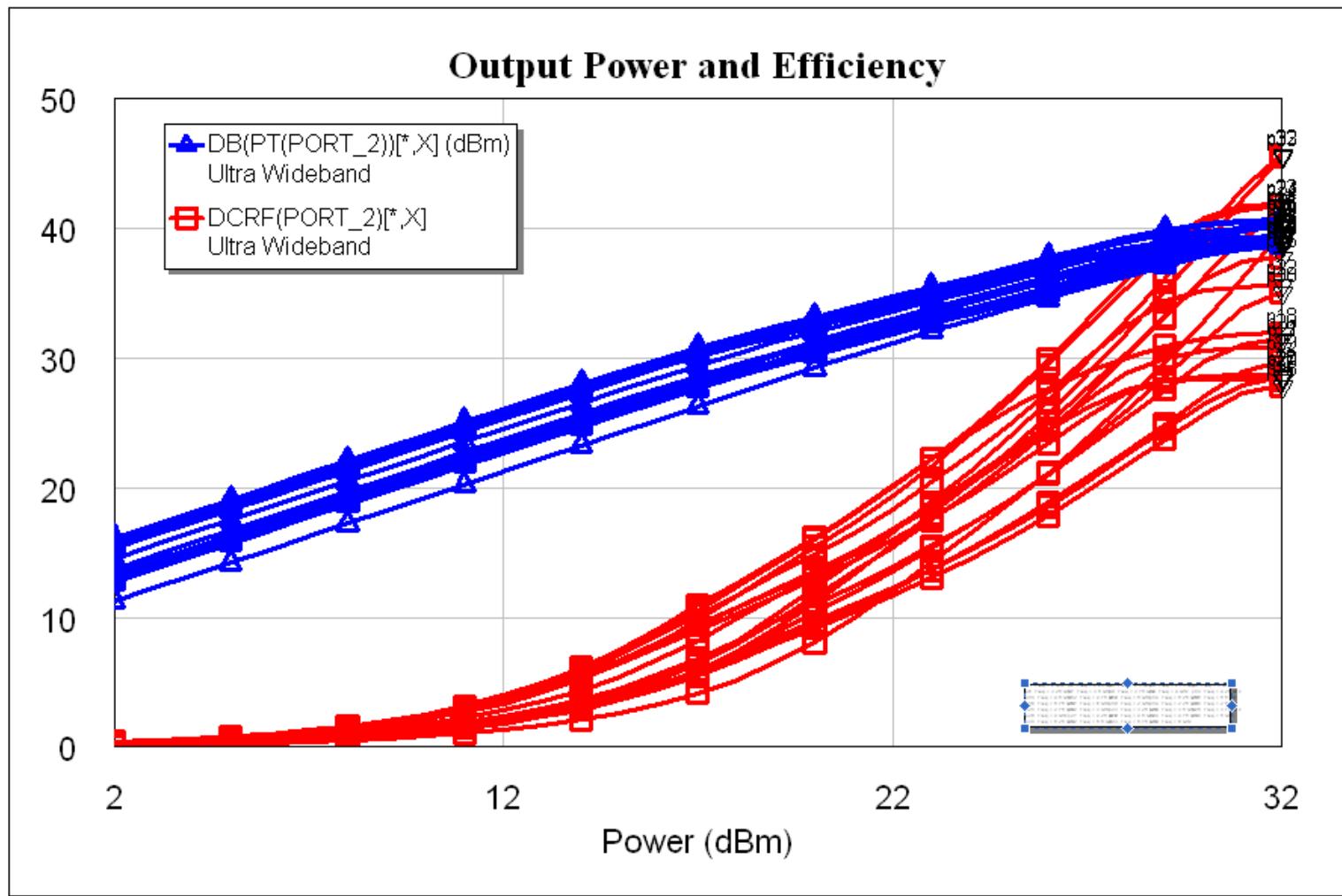
# Output Power and Efficiency versus Frequency


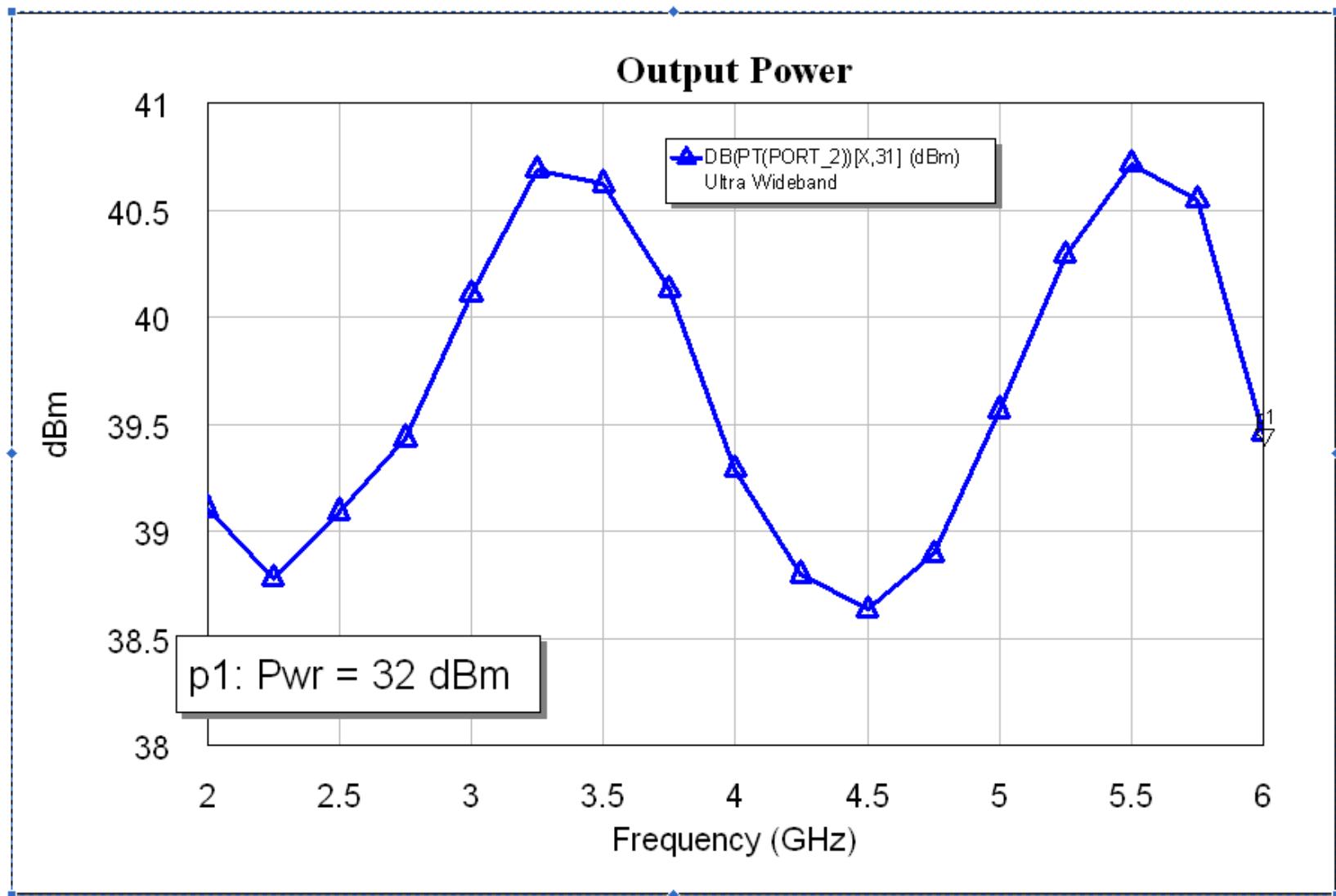
# Saturated Output Power versus Frequency




# **Cree versus Eudyna!**

# Eudyna 10 watt GaN HEMT


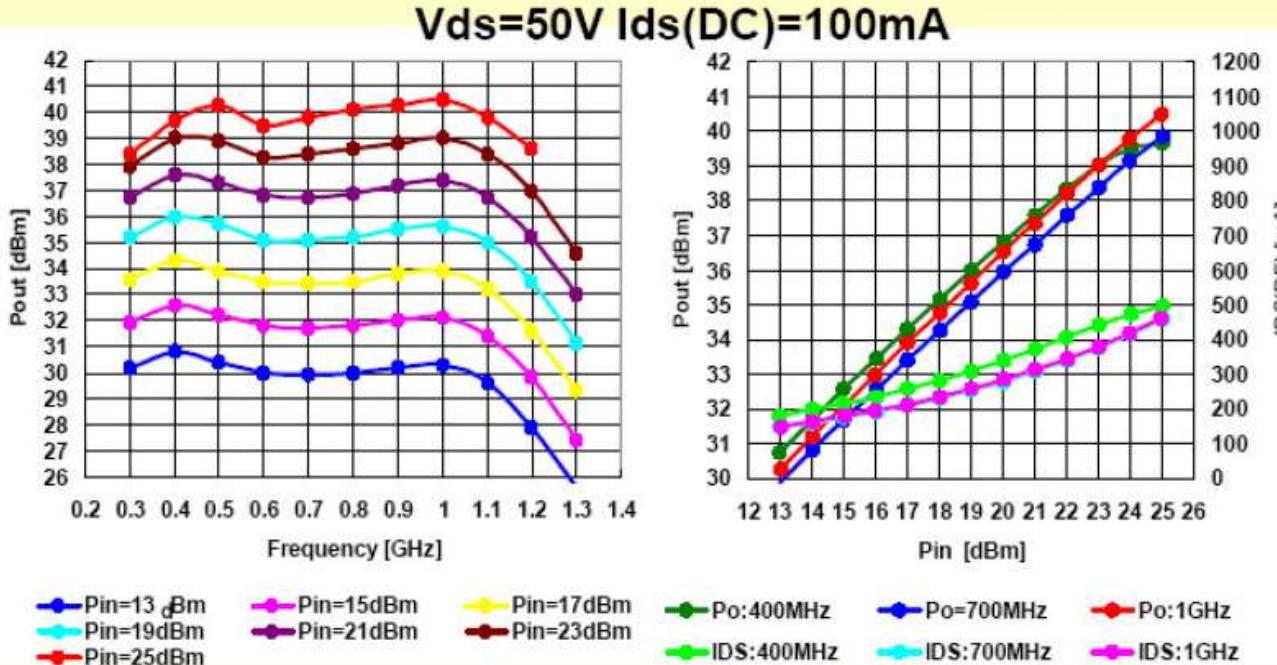
## Broad Bandwidth Operation *Actual Measurement Results*



**Eudyna**

0.3 to 1 GHz 10 Watt Amplifier


17 dB small-signal gain

40% drain efficiency at 10 watts RF output power

21

# Cree 10 watt GaN HEMT

$V_{DS} = 28$  volts  $I_{DQ} = 200$  mA

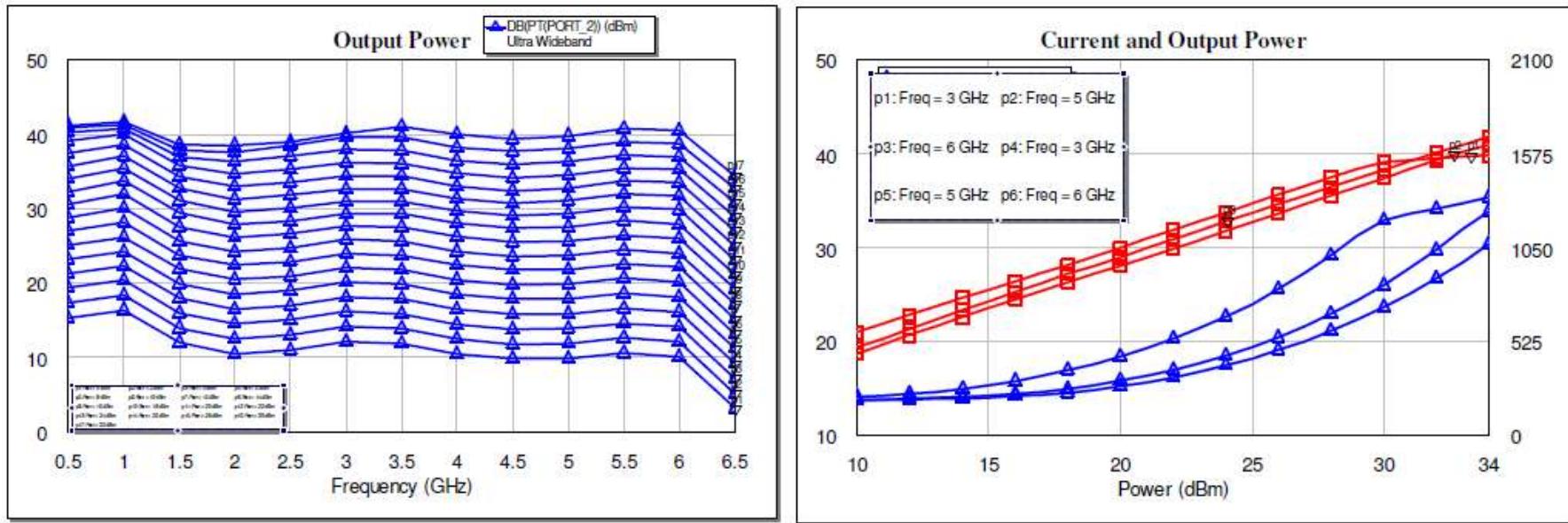

Pin is 0 to 32 dBm in steps of 2 dBm

## Cree 0.5 to 6 GHz 10 Watt Amplifier

10 to 14 dB small-signal gain

30 to 40% drain efficiency at P-1dB RF Output Power

Direct consequence of Cree's higher power density and lower capacitance per Watt!



# **Example 5**

## **Linear WiMAX Amplifier**


### **Simulation versus Measured Data**

#### **for the CGH27060F**

# Linear WiMAX Amplifier
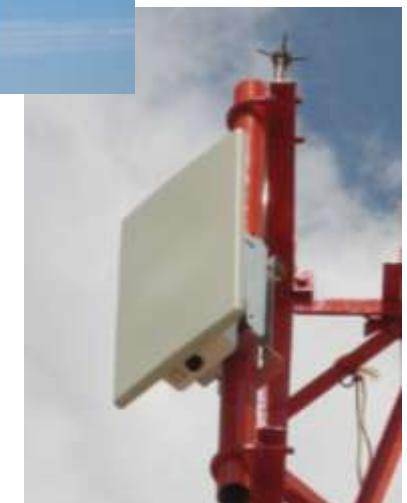
## Simulation versus Measured Data


- 60 Watt, 2.3 to 2.8 GHz linear amplifier design
- Developed an accurate packaged transistor model using the Cree GaN HEMT scale-able die model
- Circuit developed to address Fixed and Mobile Access WiMAX applications such as
  - 802.16-2004
  - 802.16e
  - WiBro
- The design targets were as follows:
  - Average Output Power > 8W
  - EVM < 2.5%
  - Drain Efficiency > 25% (under WiMAX stimulus)




# CGH27060F Packaged Device Model

ID=CGH27060


TNOM=25

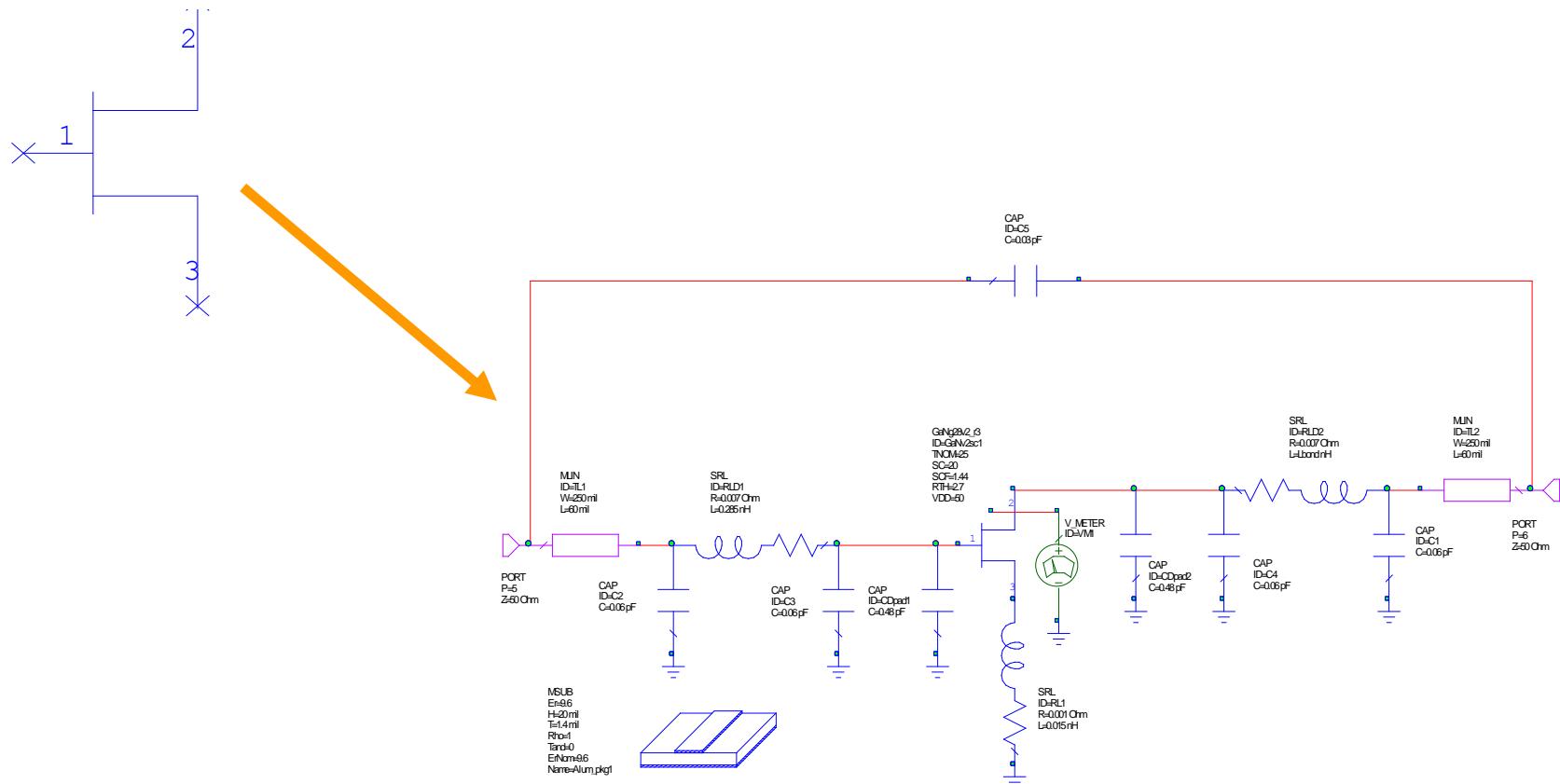




# Input Circuit Model

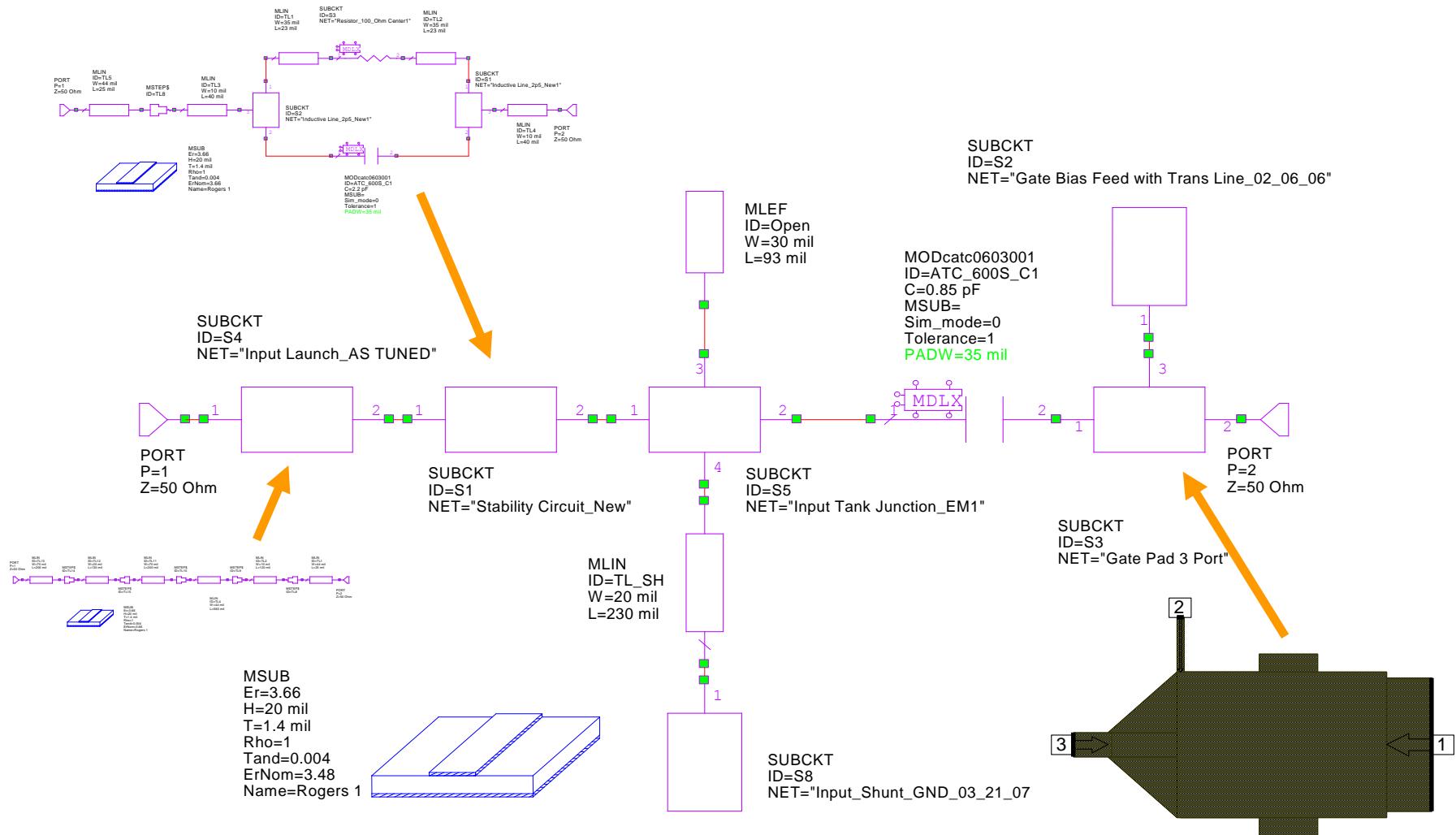

# Output Circuit Model

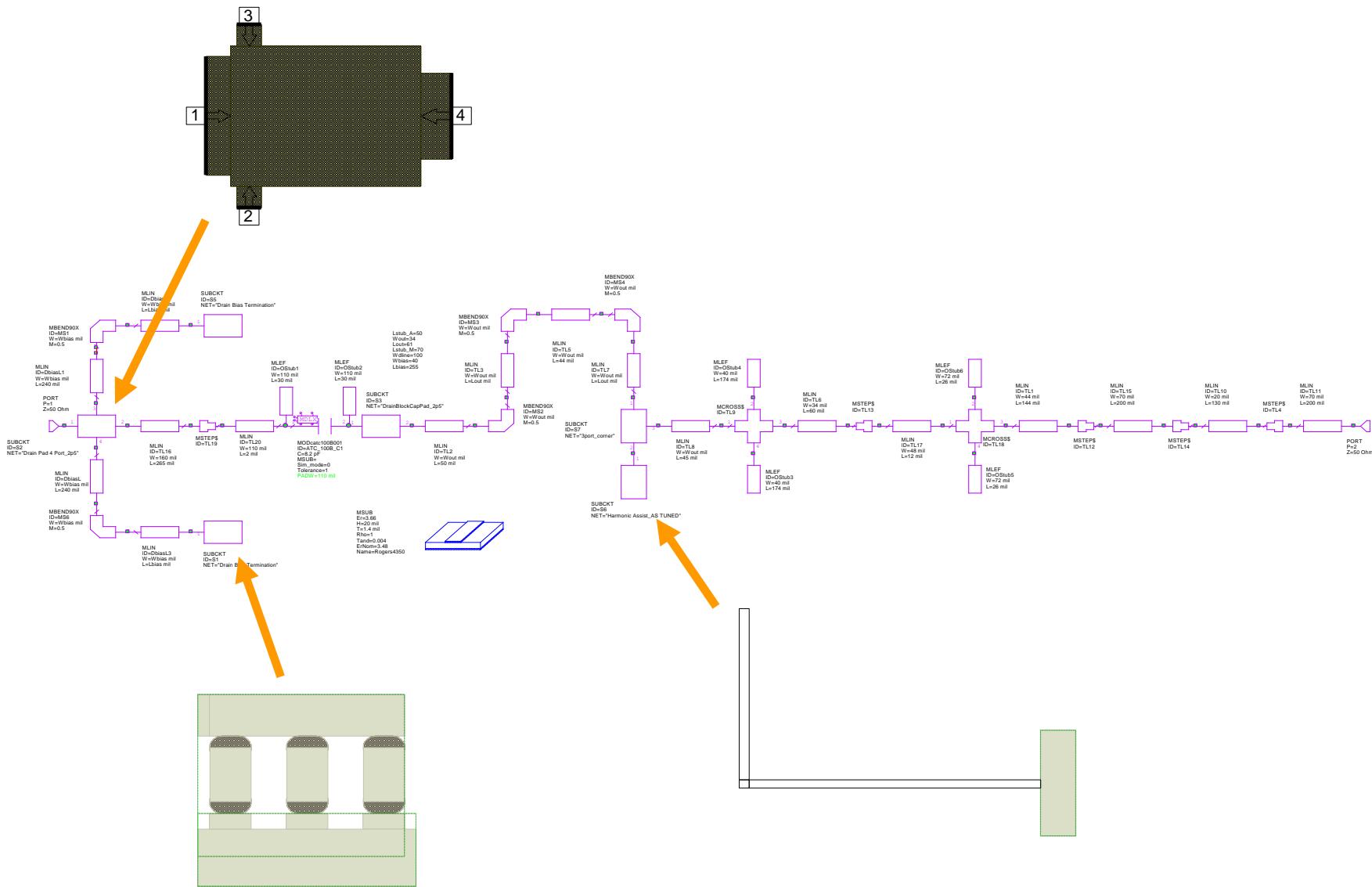


# Fully Modeled Layout of Amplifier

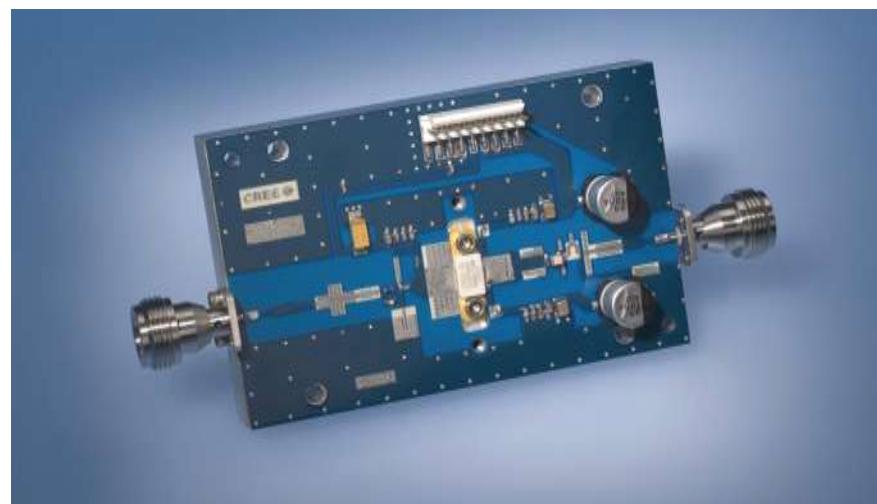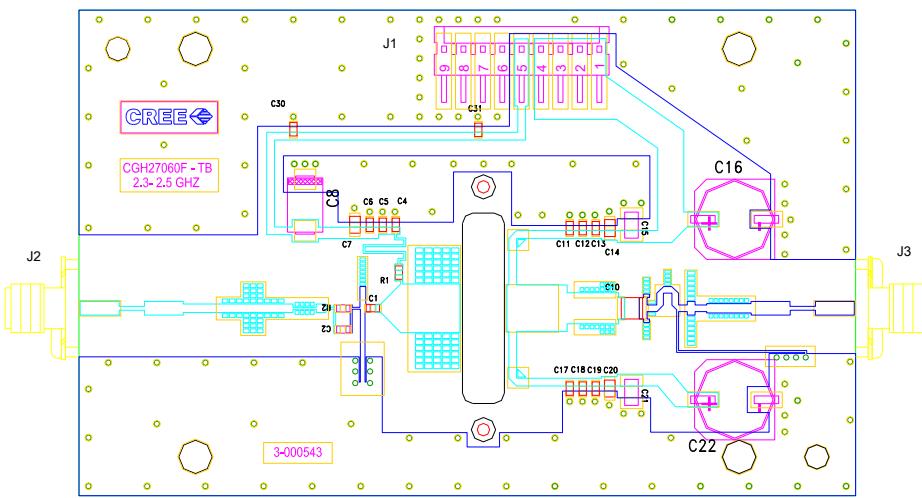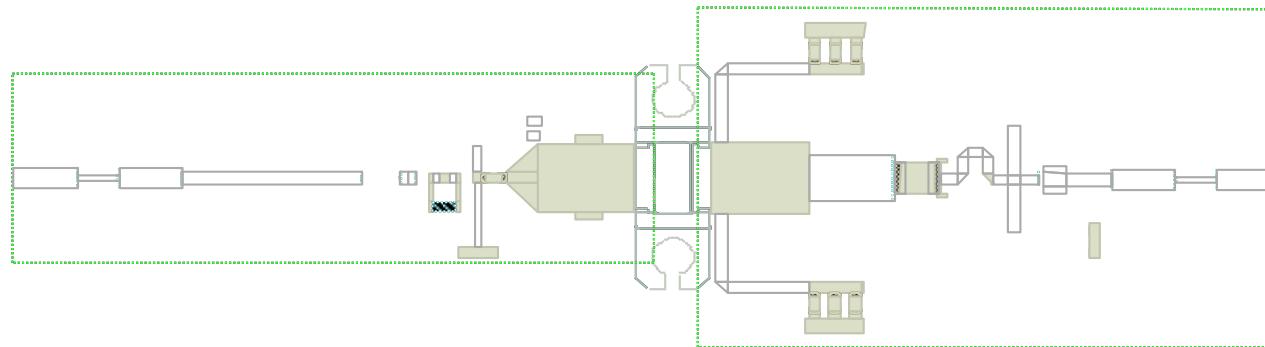


## Actual Printed Circuit Board


# Simulated and Measured Amplifier

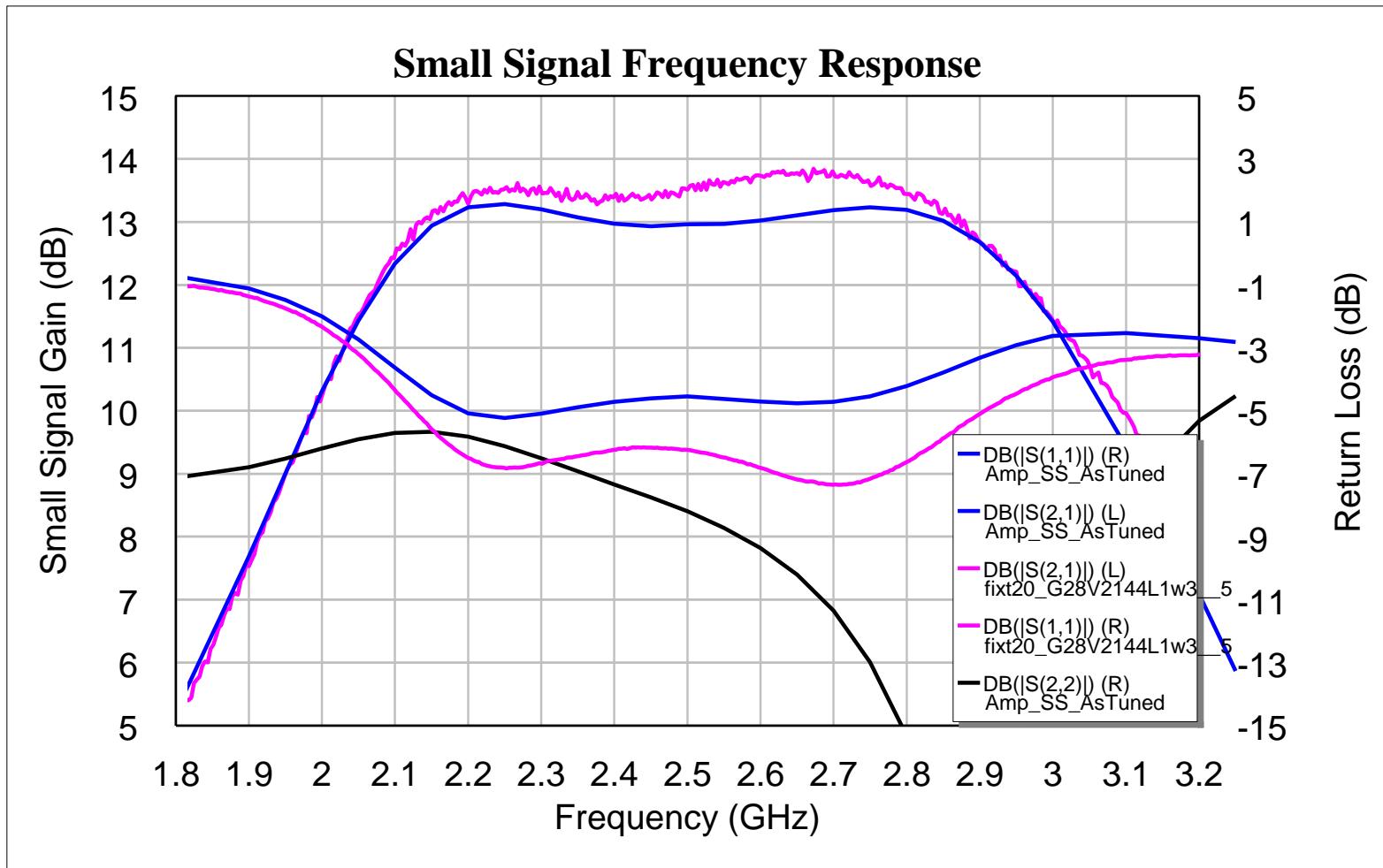


# Simulated Linearity of Amplifier

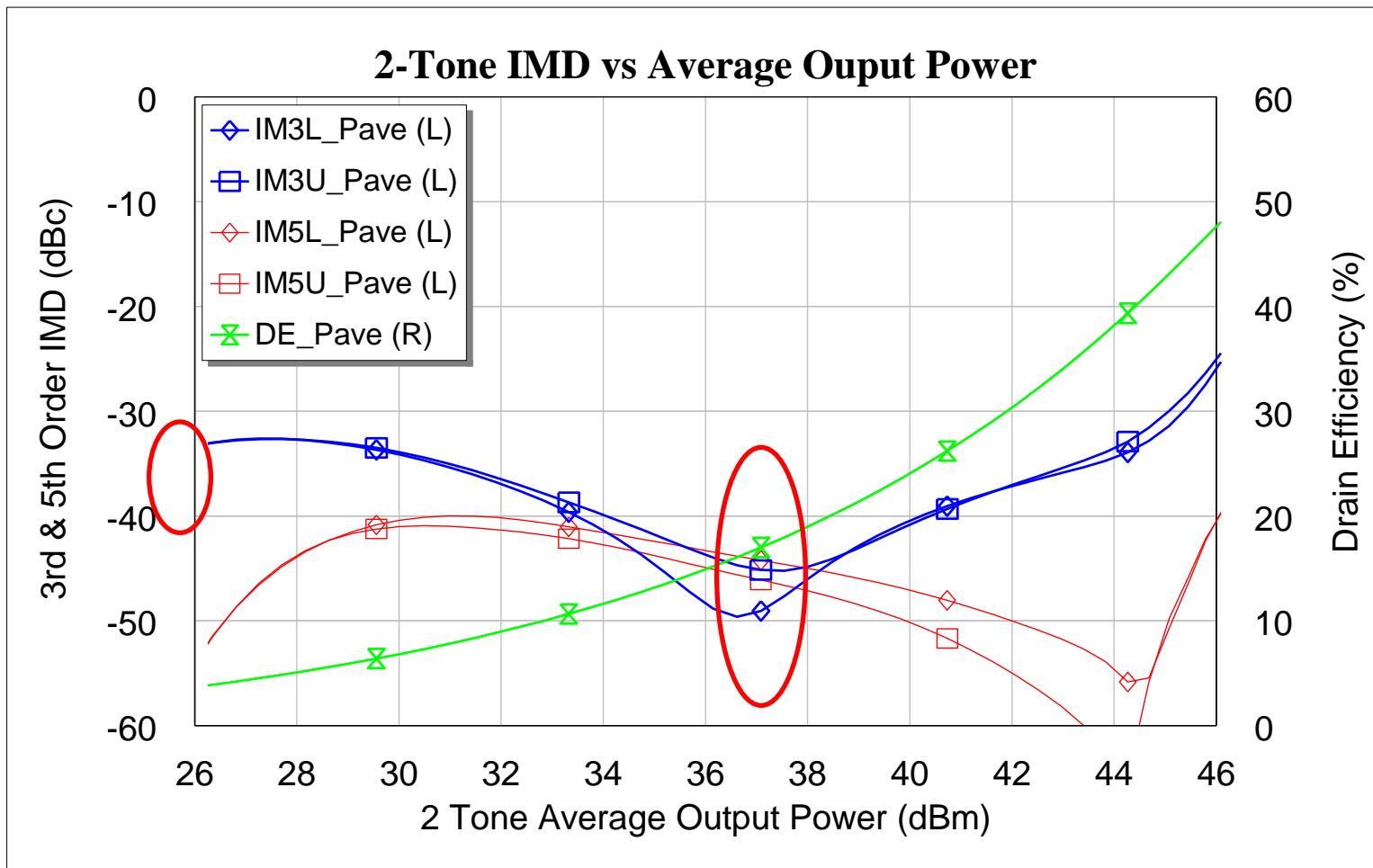

# Measured Linearity of Amplifier

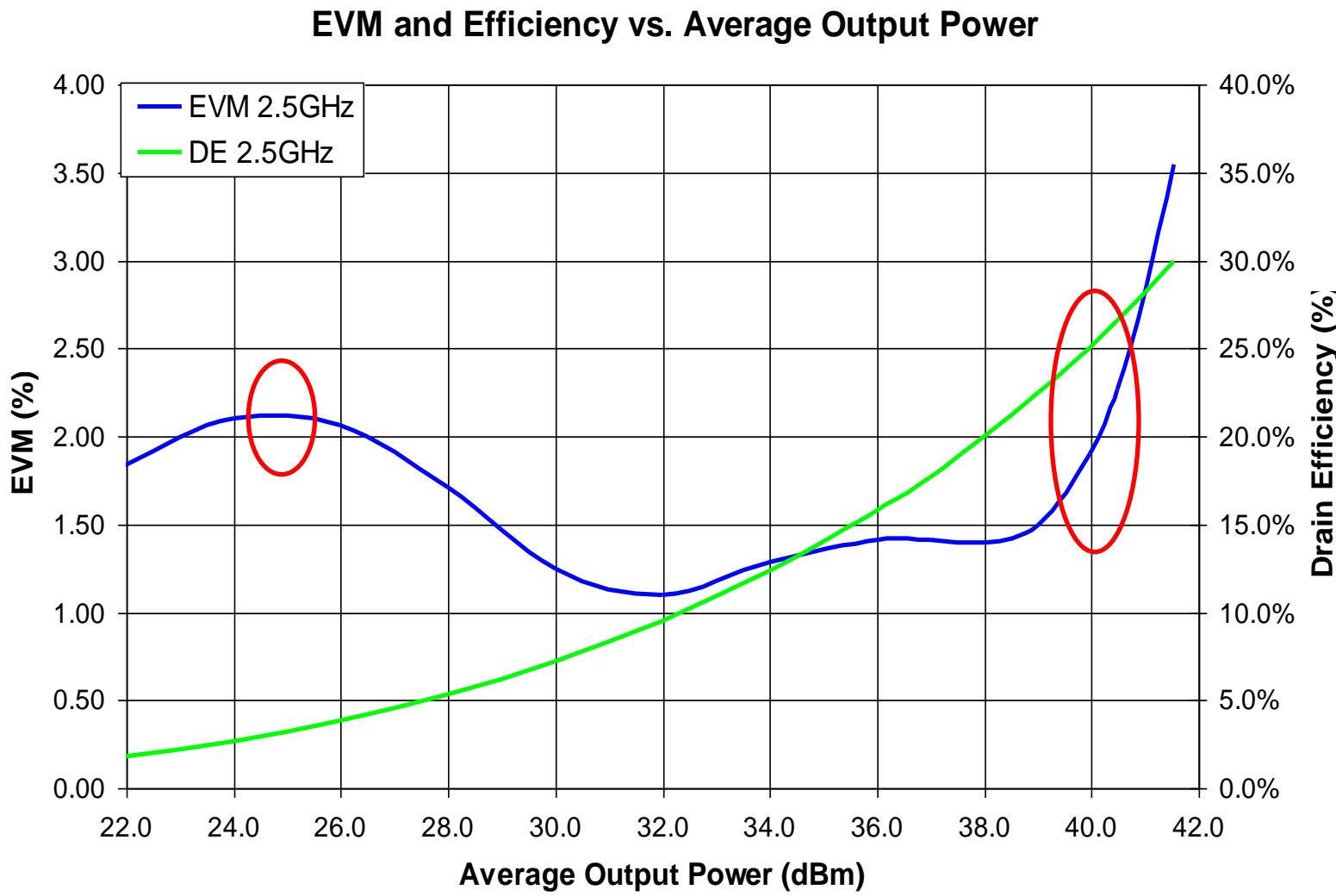

# Measured Linearity of Amplifier

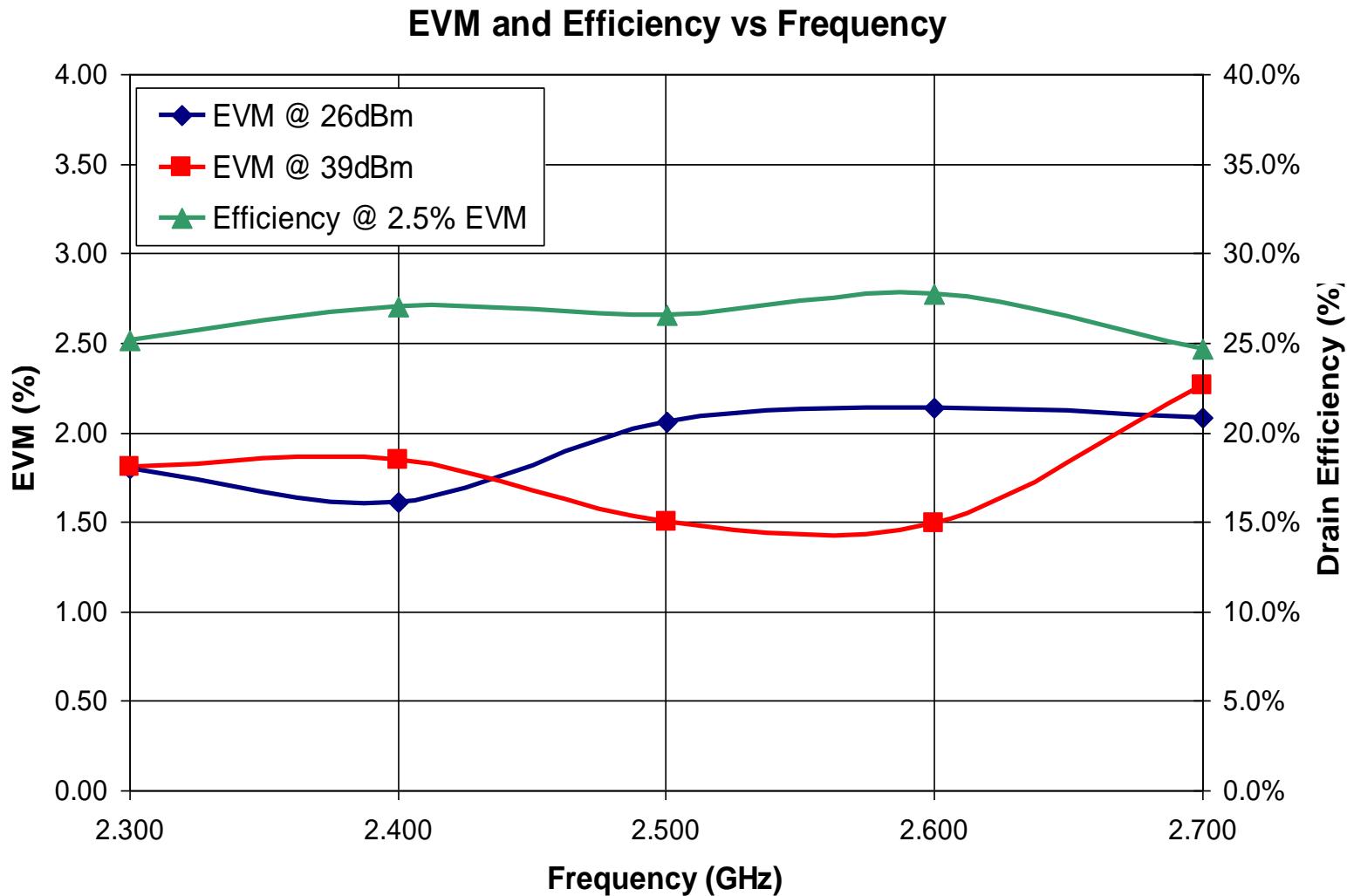

# **Example 6**


## **6 GHz Linear Amplifier using CGH55015F Transistor suitable for OFDM**

# Summary


CGH55015F is electrically “short”

- Suitable for operation up to 6 GHz for linear applications
- Maximum available gain will be traded for linearity
- Use IM3 as a figure of merit for acceptable EVM
  - Better than 40 dBc IM3 is equivalent to < 2.5% EVM
  - Needed at both 2 watts PAVE under OFDM and over 15 dB back-off power dynamic range
  - Video “short” used in design to assure low IM3’s
  - 2nd harmonic short used on transistor output to improve linearity
  - IDQ adjusted to 60 mA – value used for linear amplifiers at 2.5 and 3.5 GHz

# PA Schematic

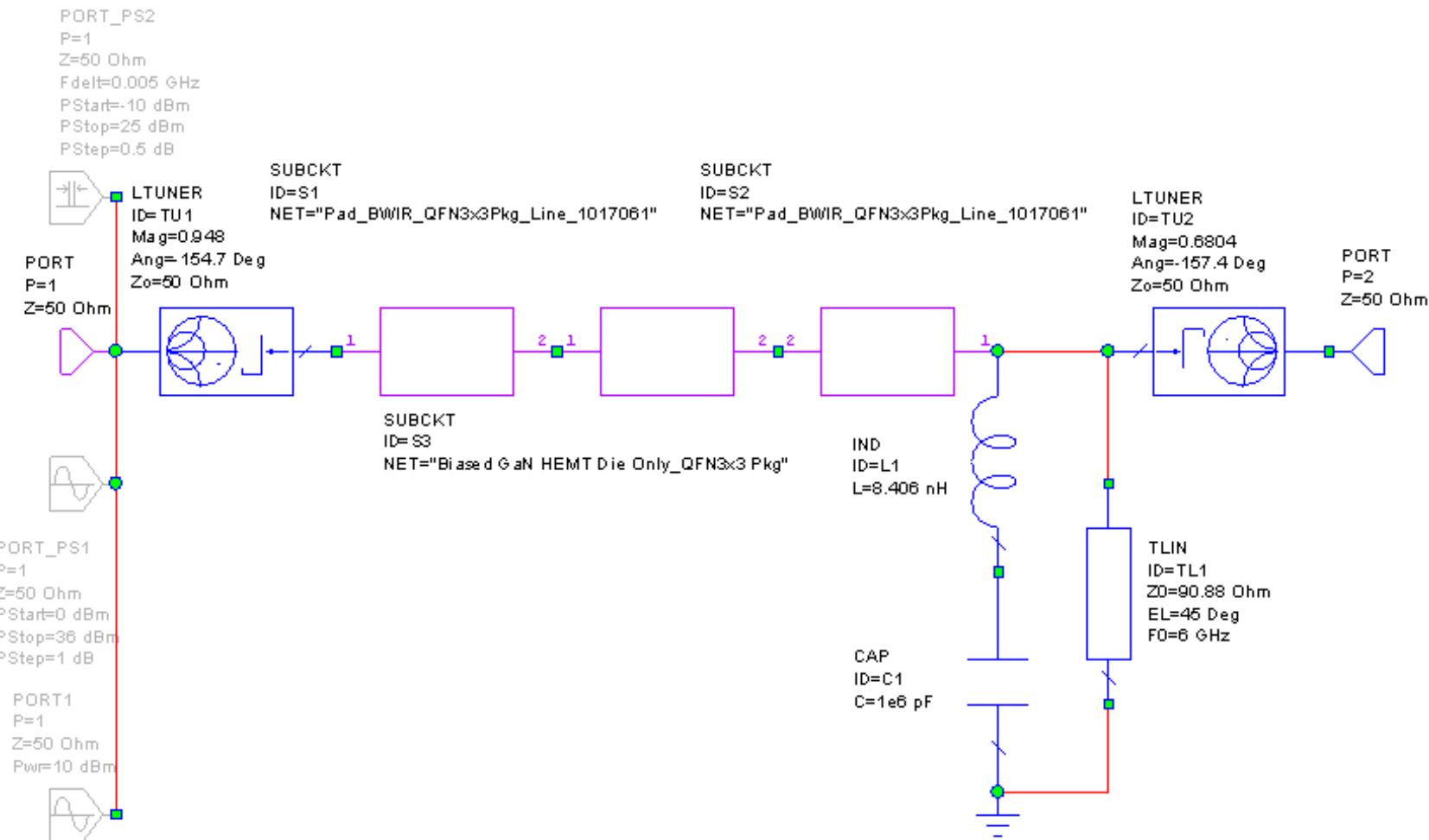

# Source Pull Value at 6 GHz

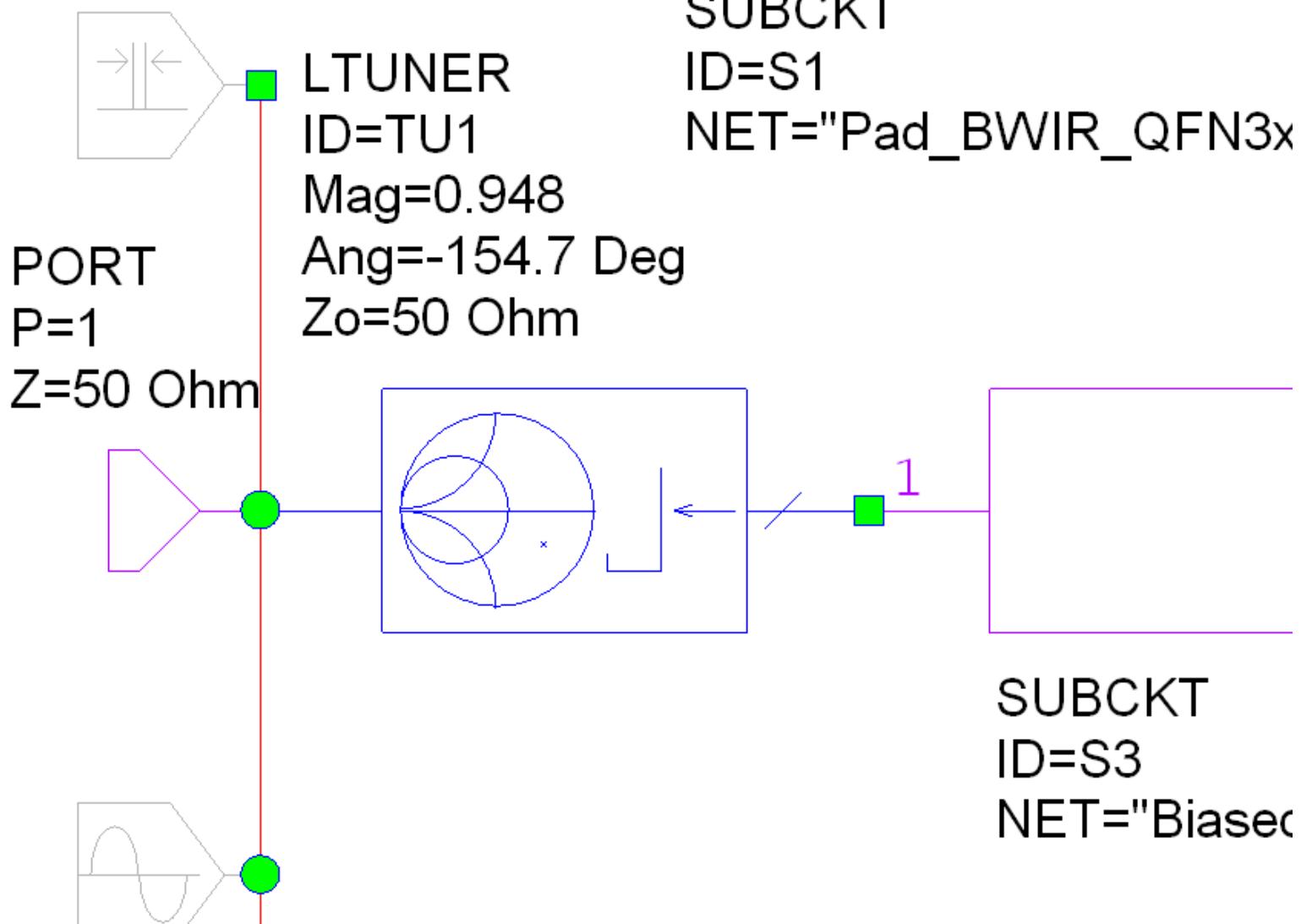


# Load Pull Value at 6 GHz

ne\_1017061"


LTUNER  
ID=TU2

Mag=0.6804  
Ang=-157.4 Deg  
Zo=50 Ohm


PORT  
P=2  
Z=50 Ohn

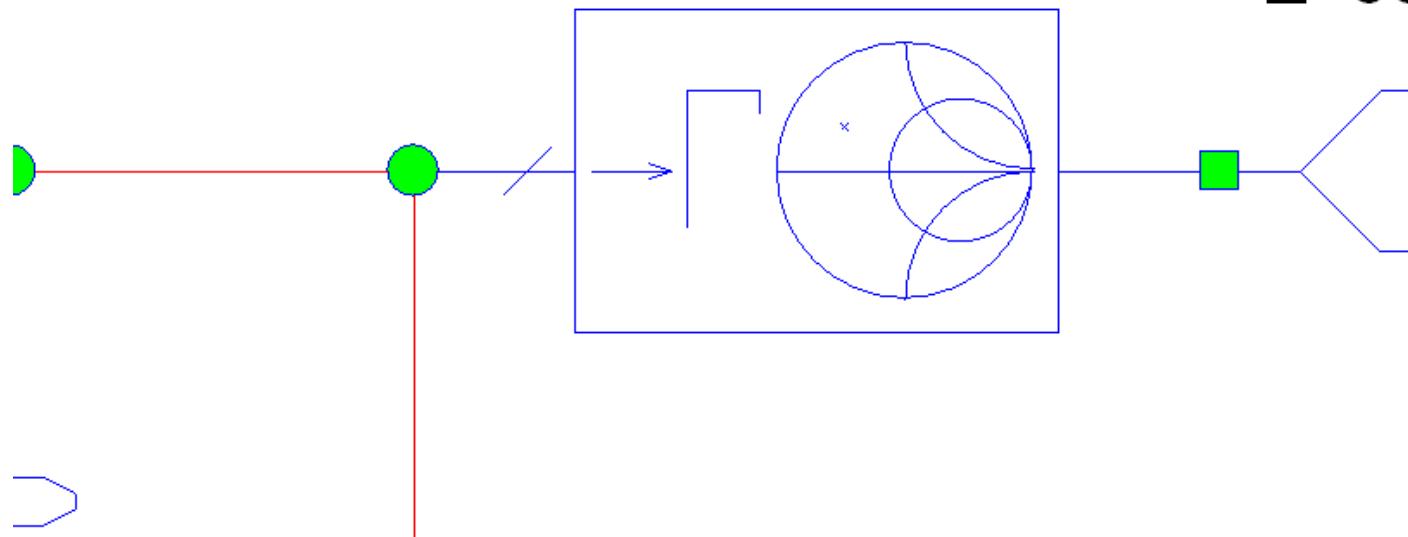


# Video Return and 2nd Harmonic Short

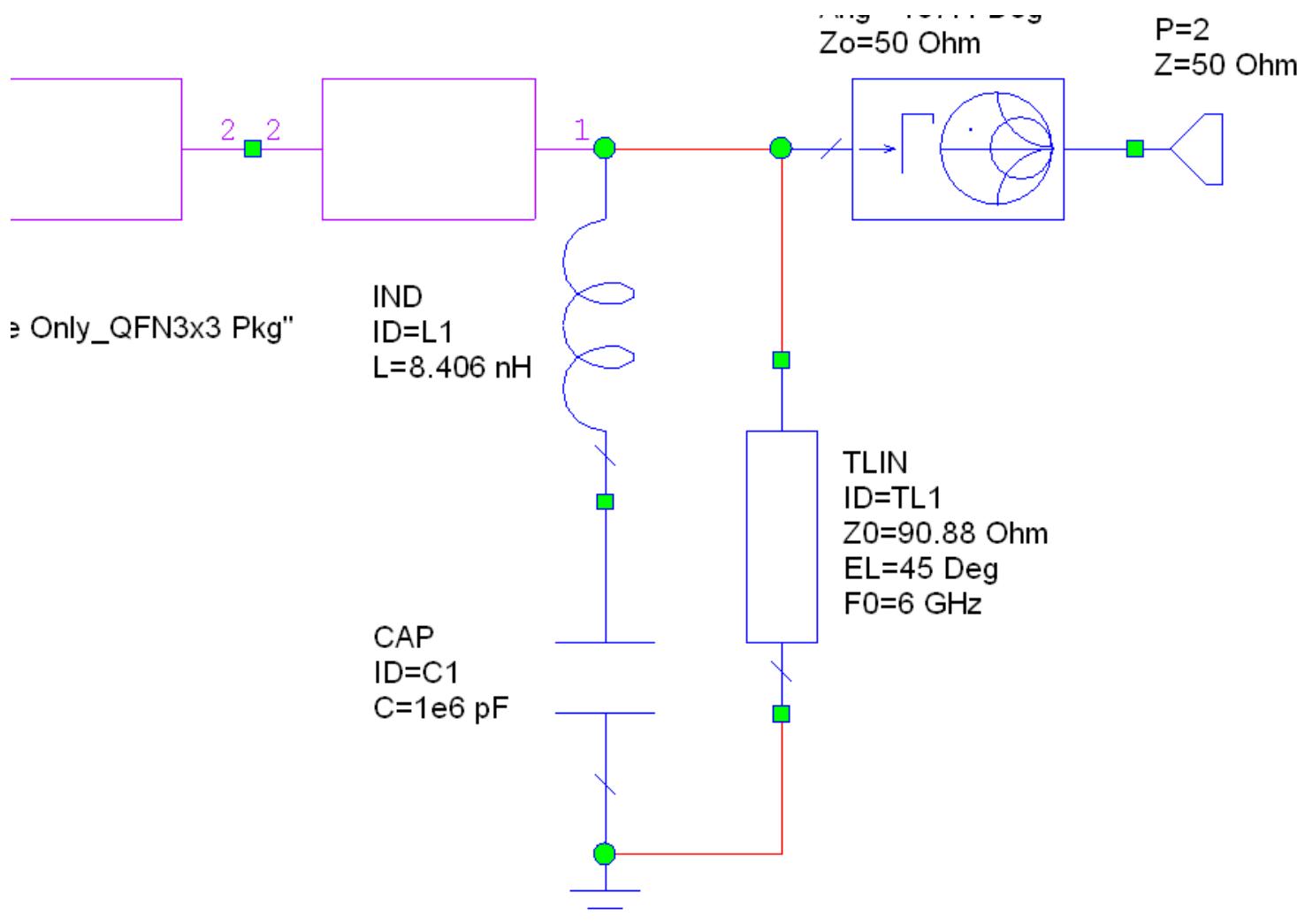

# DC Current versus RF Drive Level

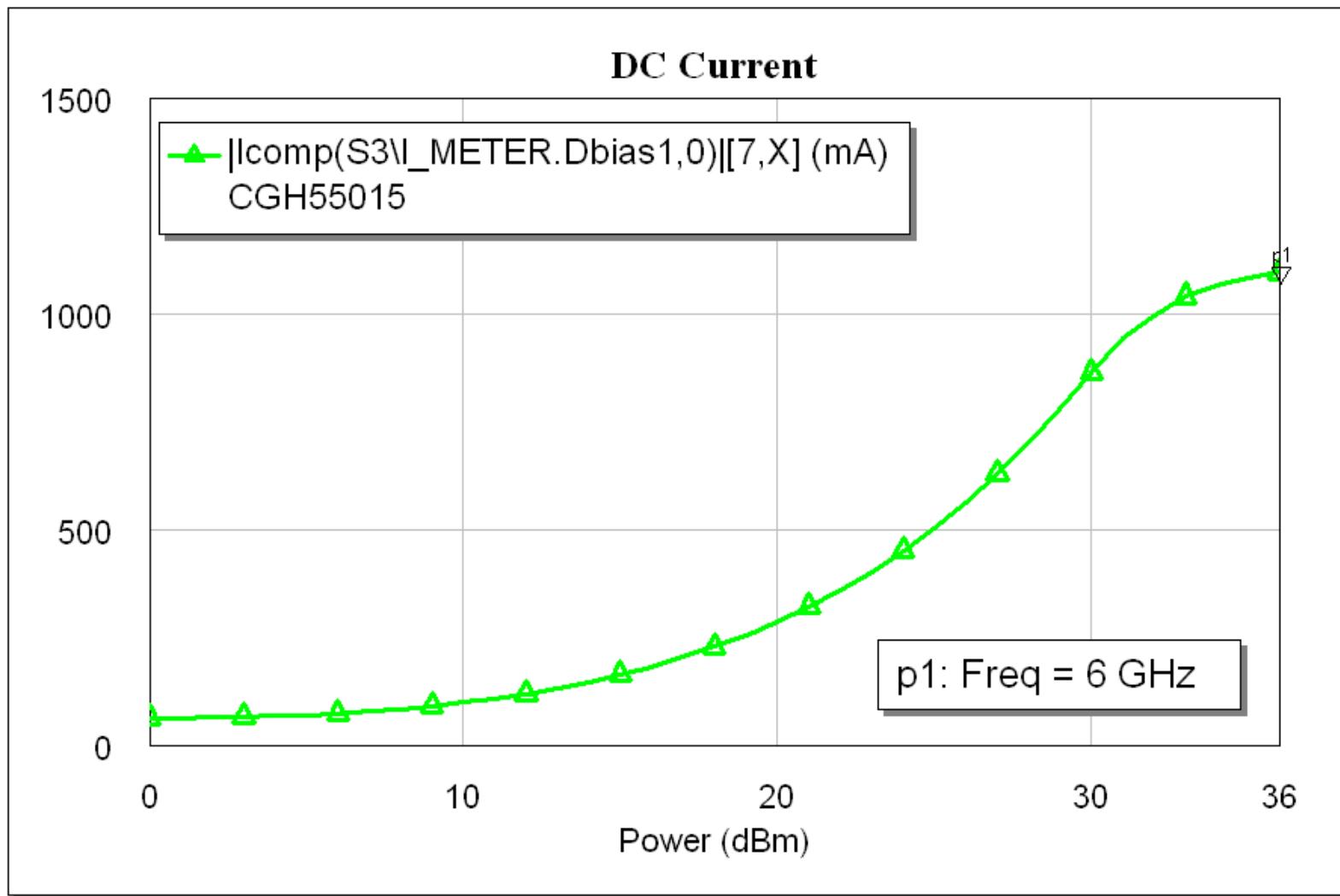


# Maximum Available Gain of CGH55015

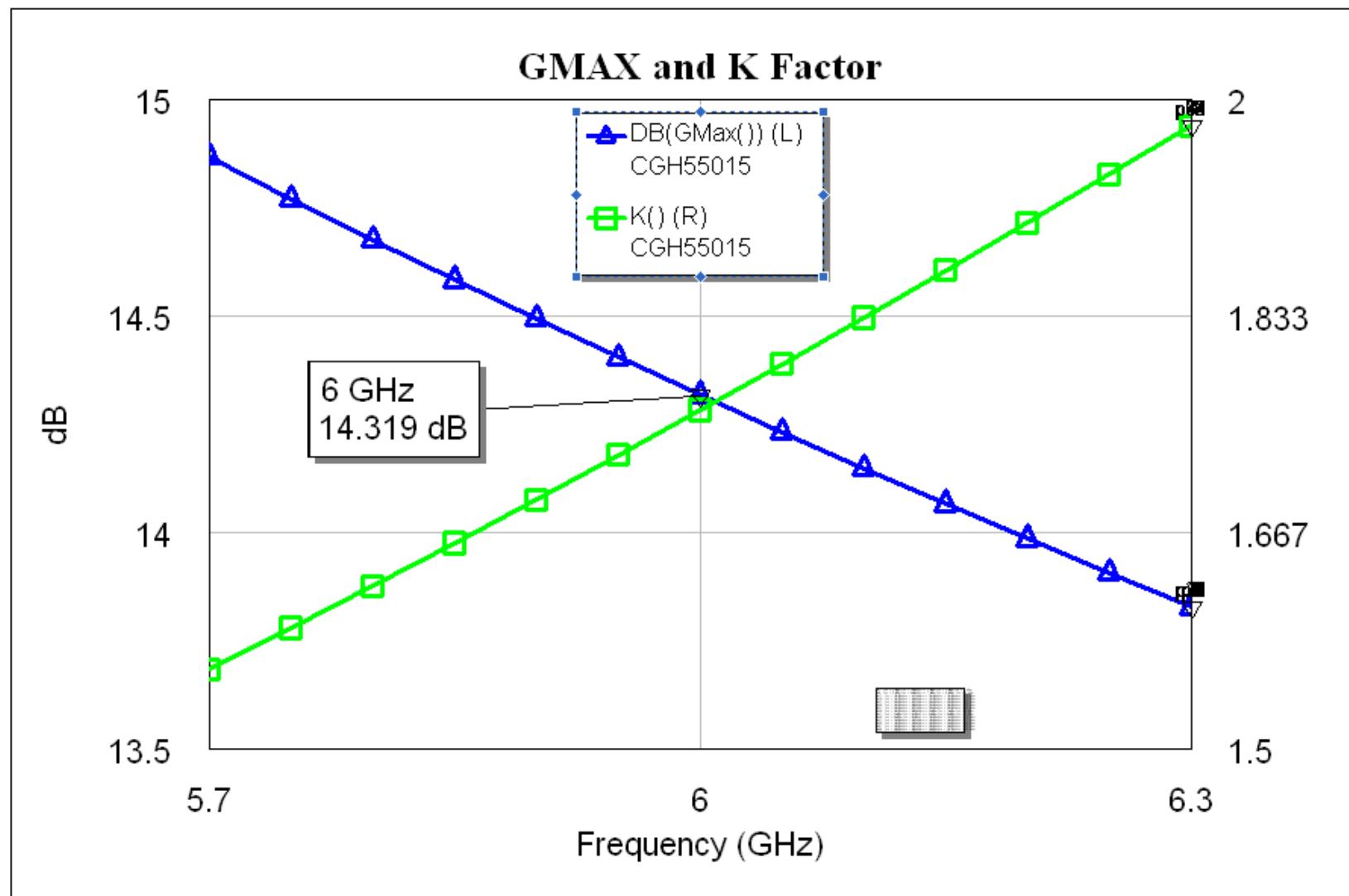


# Small-Signal Gain and Input return loss over 5.7 to 6.3 GHz


S21 and S11

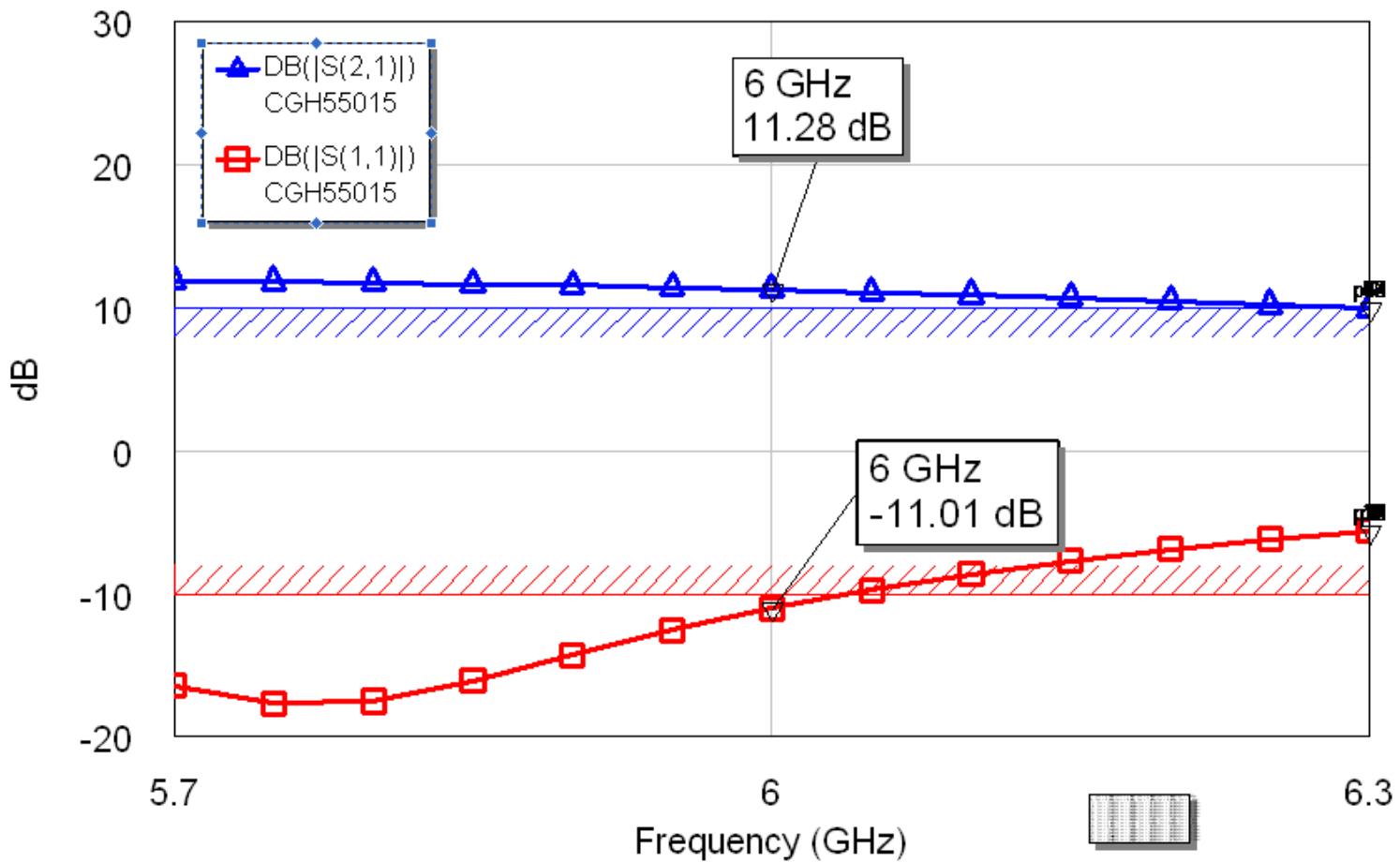
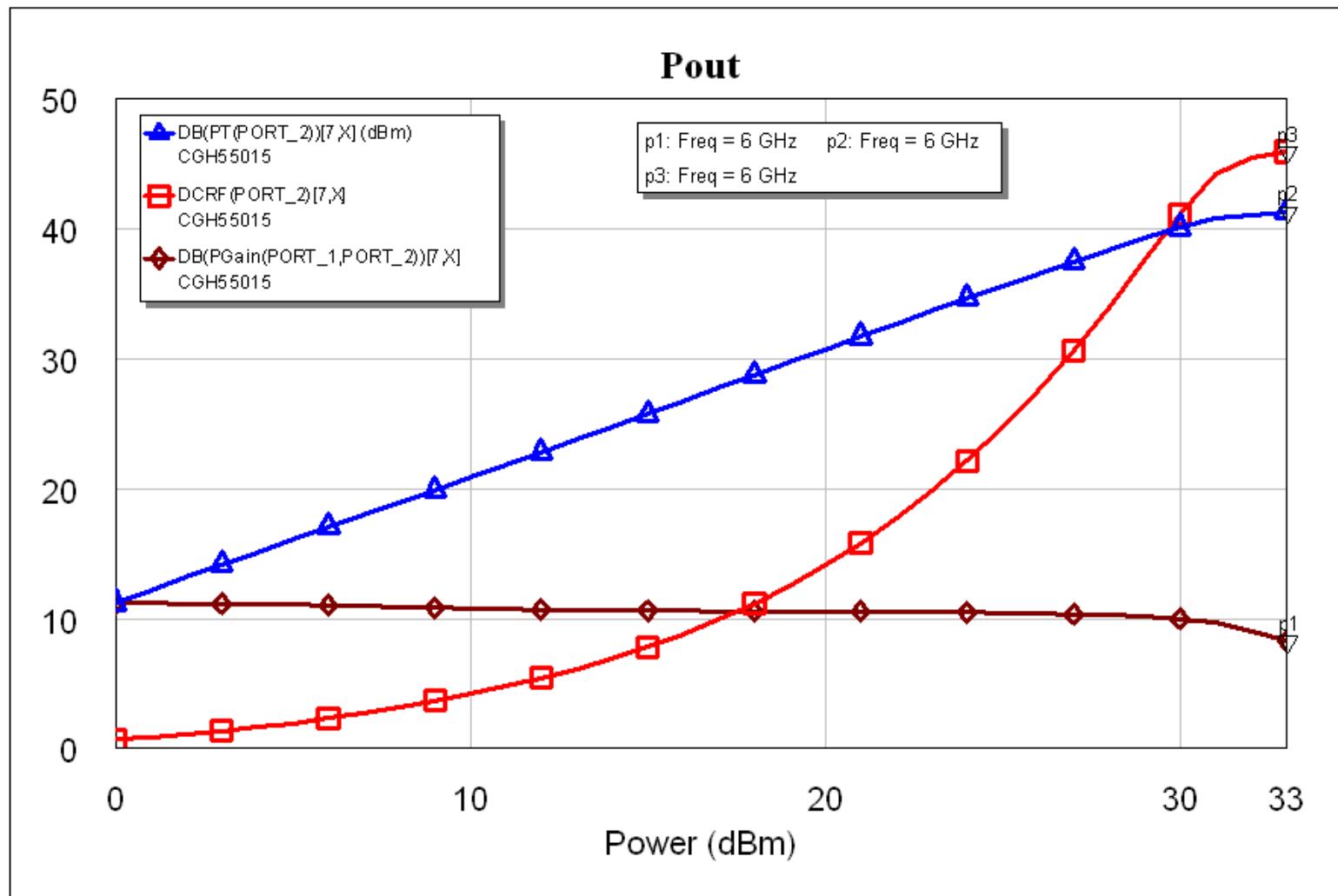
# Single-Tone CW RF Output Power, Power Gain and Drain Efficiency versus RF Input Power



# 2-Tone IM3 versus Input Power

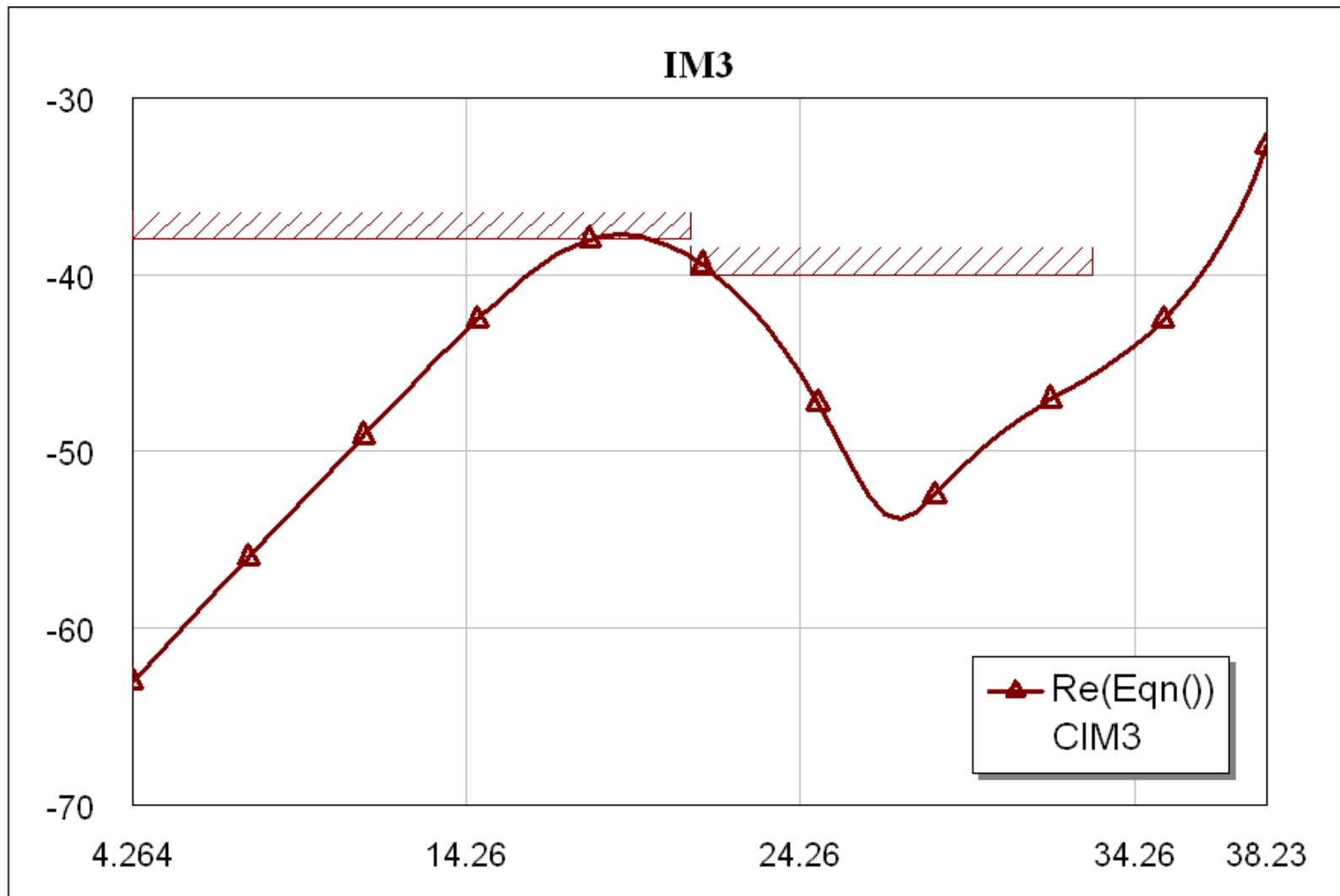


# **Example 7**

## **High Efficiency Waveform Engineered Amplifier**

# Summary

- CGH40120F operating at 28 volts
- Fundamental tuning as well as 2<sup>nd</sup> and 3<sup>rd</sup> harmonic terminations to improve efficiency
- 2.45 GHz application where high efficiency is key

# Amplifier Schematic

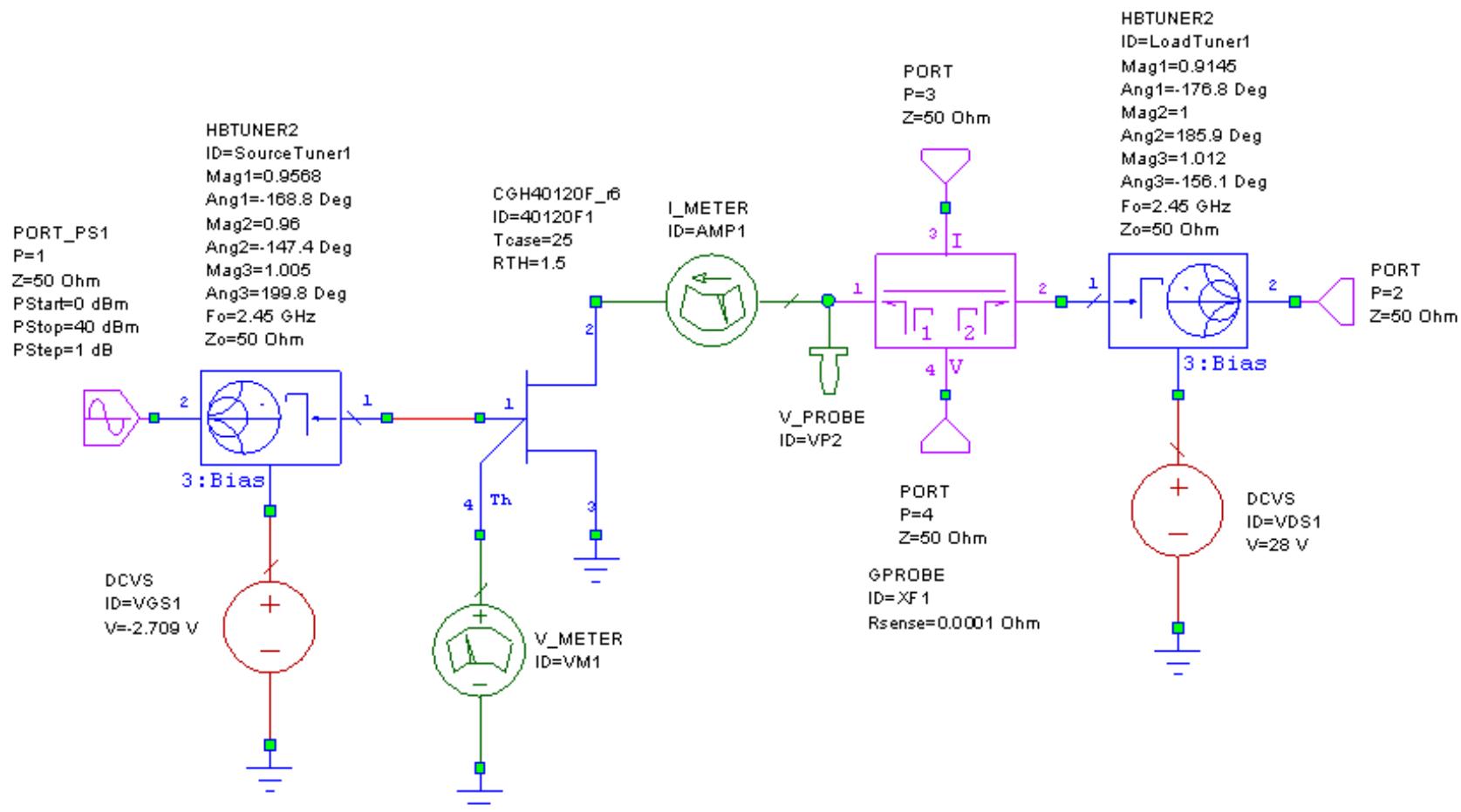


# Gate fundamental and harmonic terminations

PORT\_PS1  
P=1  
Z=50 Ohm  
PStart=0 dBm  
PStop=40 dBm  
PStep=1 dB

**HBTUNER2**  
ID=SourceTuner1  
Mag1=0.9568  
Ang1=-168.8 Deg  
Mag2=0.96  
Ang2=-147.4 Deg  
Mag3=1.005  
Ang3=199.8 Deg  
Fo=2.45 GHz  
Zo=50 Ohm

CGH40:  
ID=401:  
Tcase=2  
RTH=1.


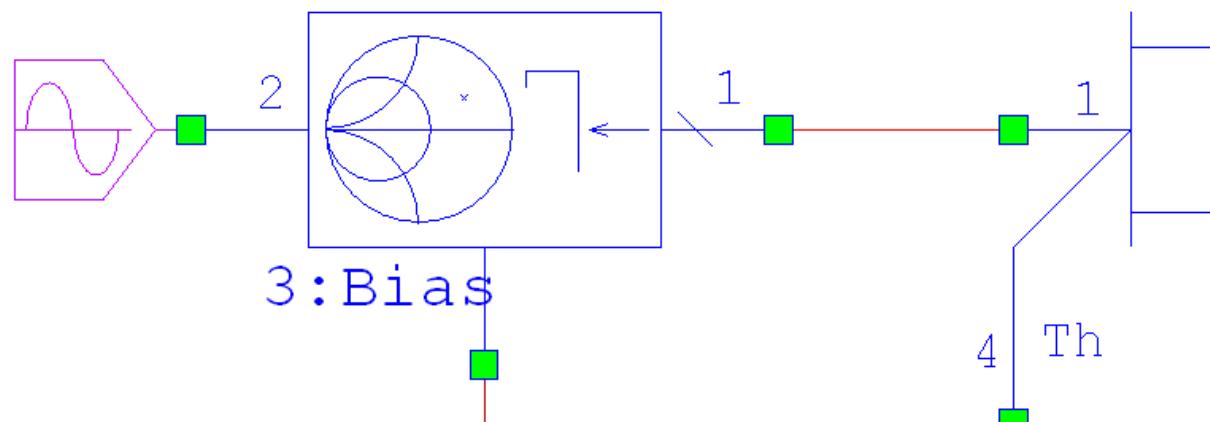


# Drain fundamental and harmonic terminations

RT

3

50 Ohm

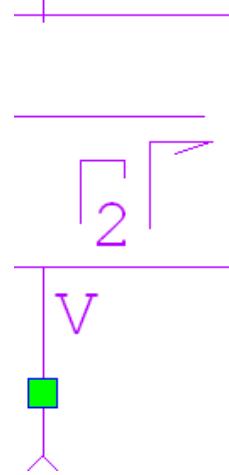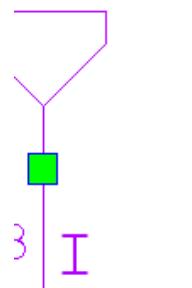

HBTUNER2

ID=LoadTuner1

Mag1=0.9145

Ang1=-176.8 Deg

Mag2=1


Ang2=185.9 Deg

Mag3=1.012

Ang3=-156.1 Deg


Fo=2.45 GHz

Zo=50 Ohm

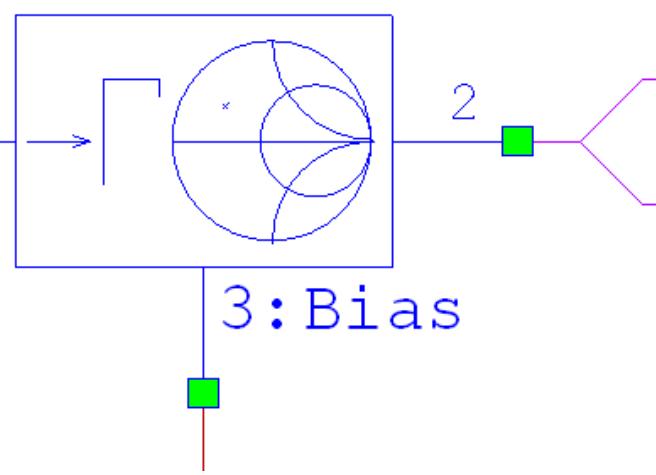


PORT  
P=2  
Z=50 Ohm
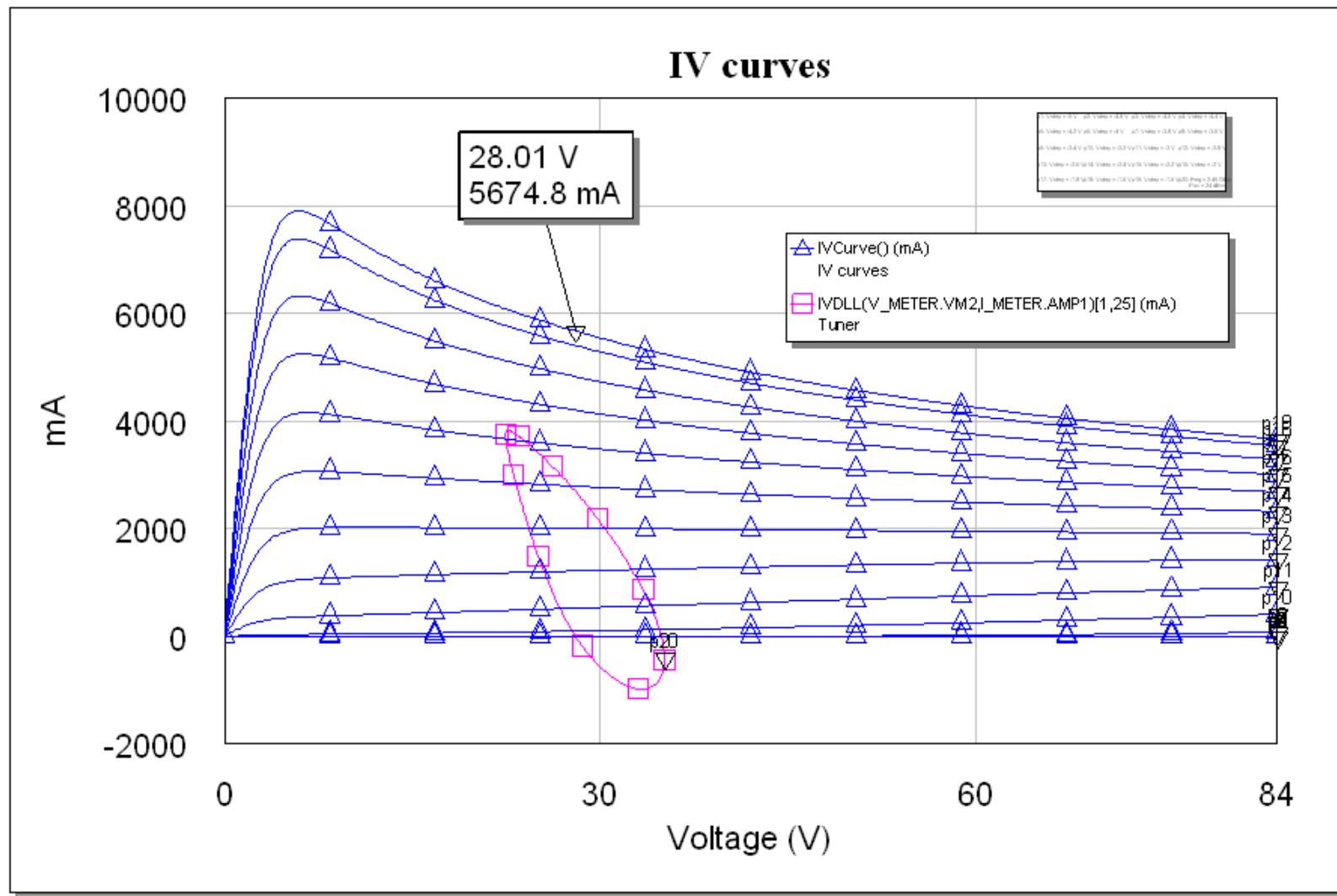
# I-V Curves showing effect of self heating (CW)




Also shown is dynamic load line

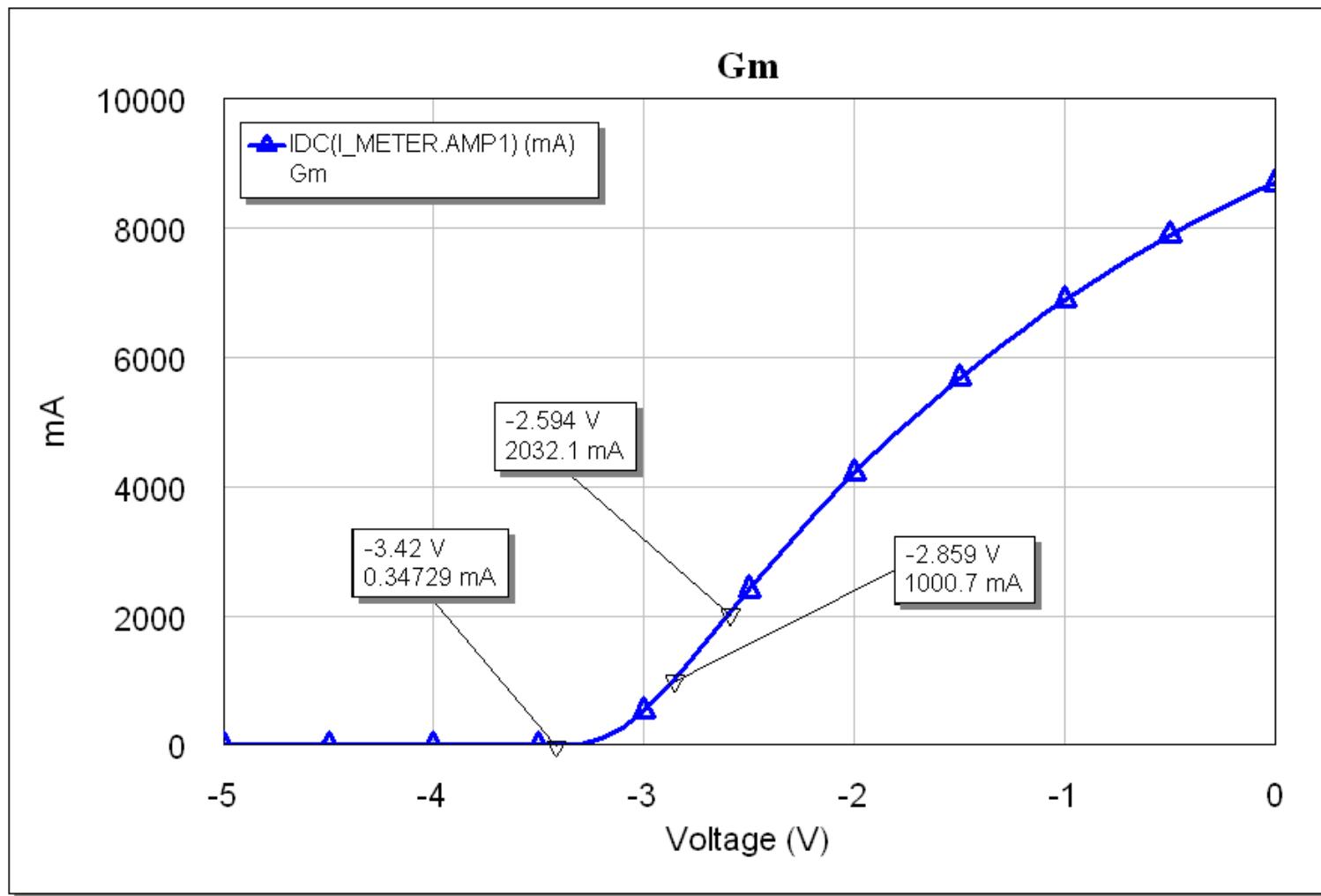
# Simulation showing pinch-off of transistor


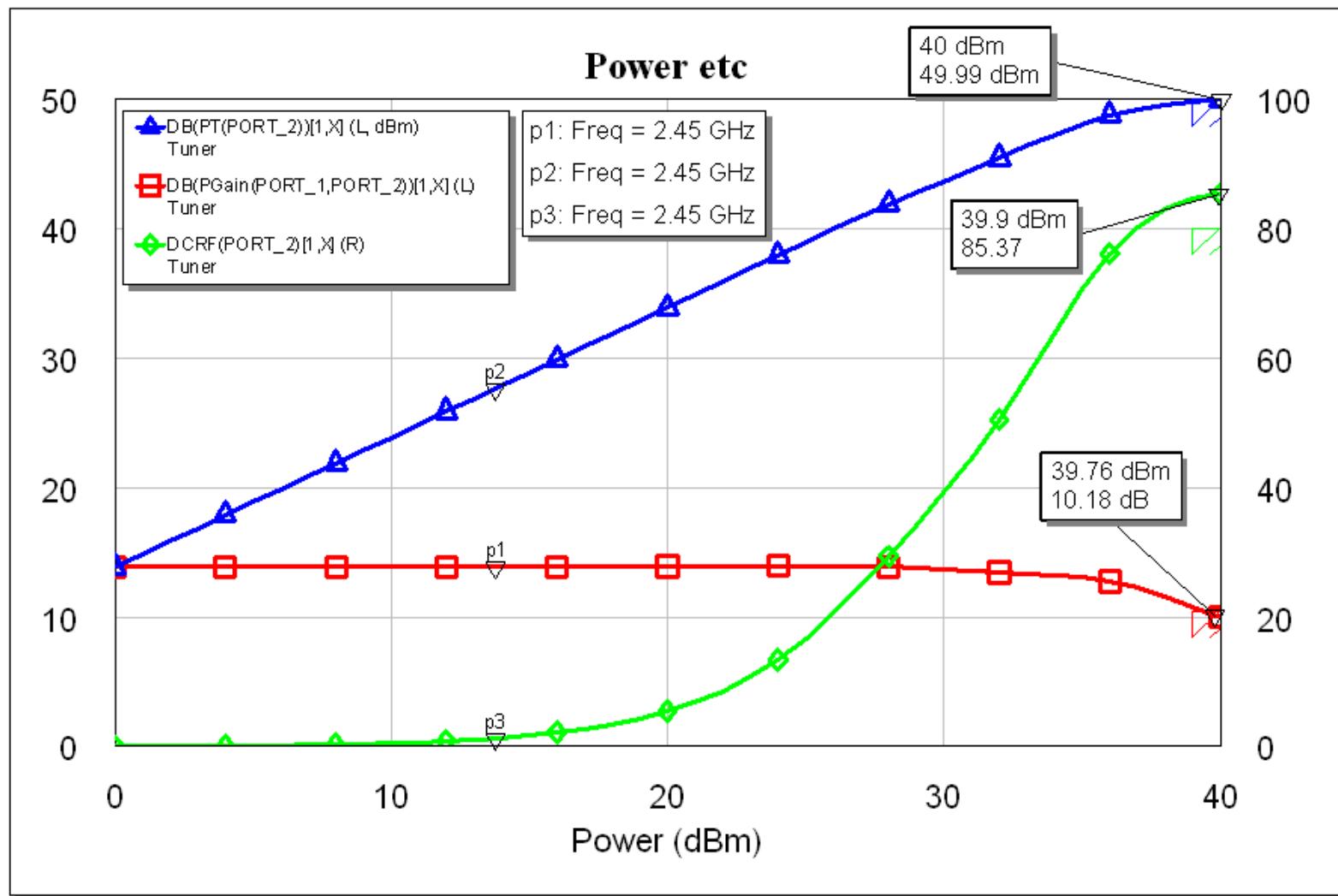
# Output Power, Power Gain and Drain Efficiency




# Drain Voltage and Current Waveforms

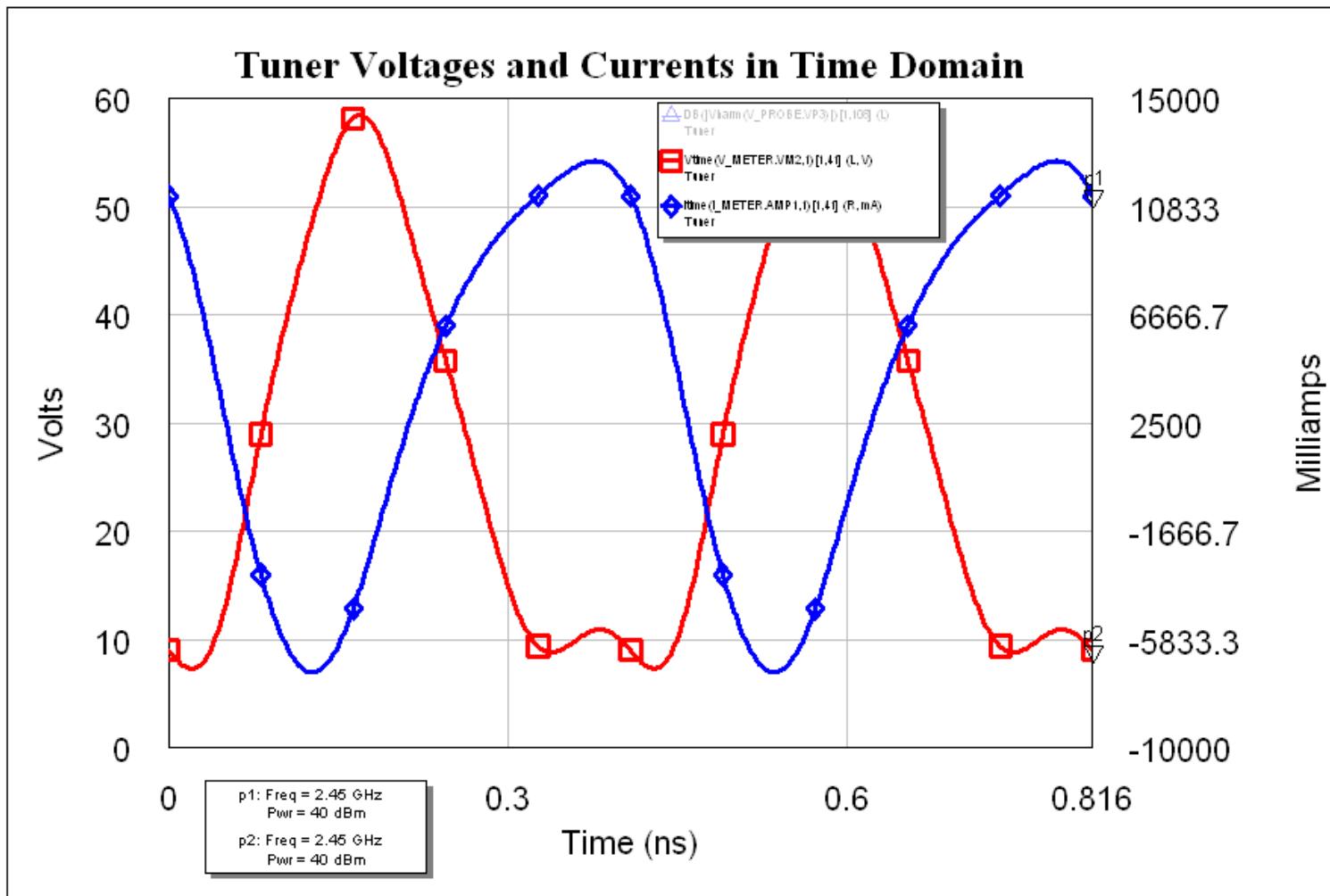

Pin = 40 dBm

# Current and Voltage harmonics at Drain – 3dB compression

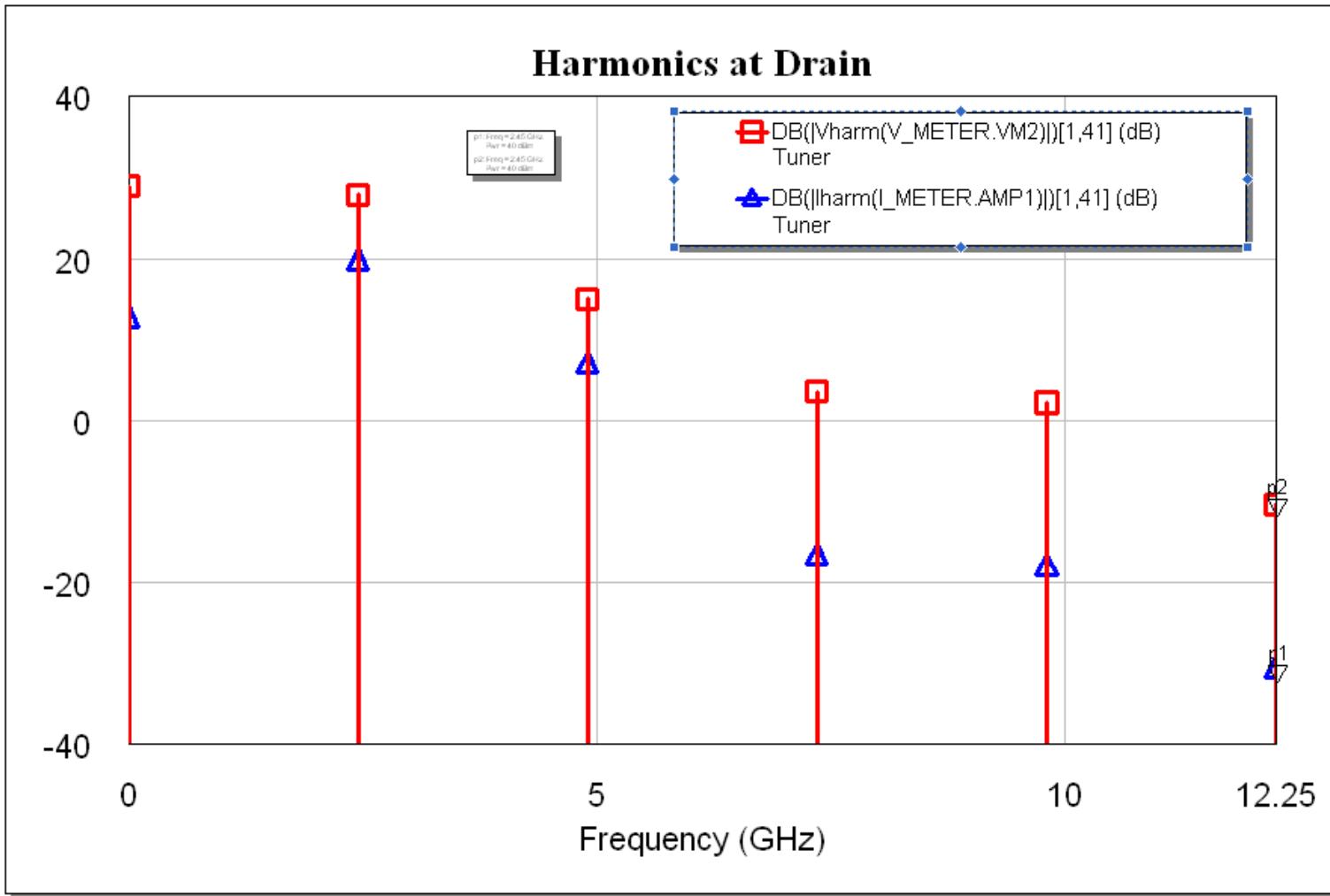

**Example 8**

**CGH27030 Linear Driver Amplifier**


**for the 1.45 to 1.492 GHz DVB-H**

**Band**

# Summary


- PCB material assumed to be 32 mil thick Rogers 4003 with dielectric constant of 3.38
- Simple design using a few transmission lines and chip components using CGH27030F GaN HEMT transistor in Cree 440166 package
- Drain voltage set at 32 volts and  $I_{dq}$  set to 100mA
- Microstrip used with finite Q capacitors and inductor in simulation
- Goals
  - $> 18$  dB stable small-signal gain
  - IM3's at Pave and back-off hill to be better than 42 dBc and 35 dBc respectively
  - $P_{sat} > 25$  watts
  - Input Return Loss  $> 15$  dB

# Schematic of Amplifier

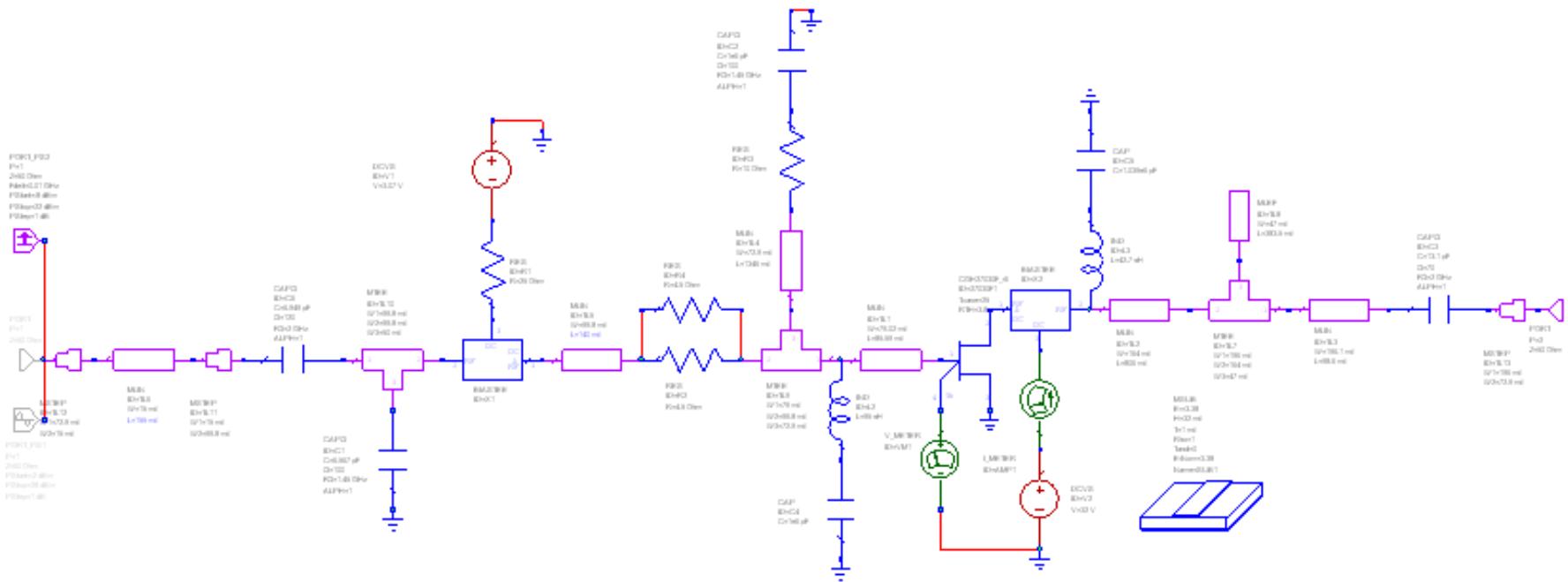


**CREE**

# Detail of Input Match

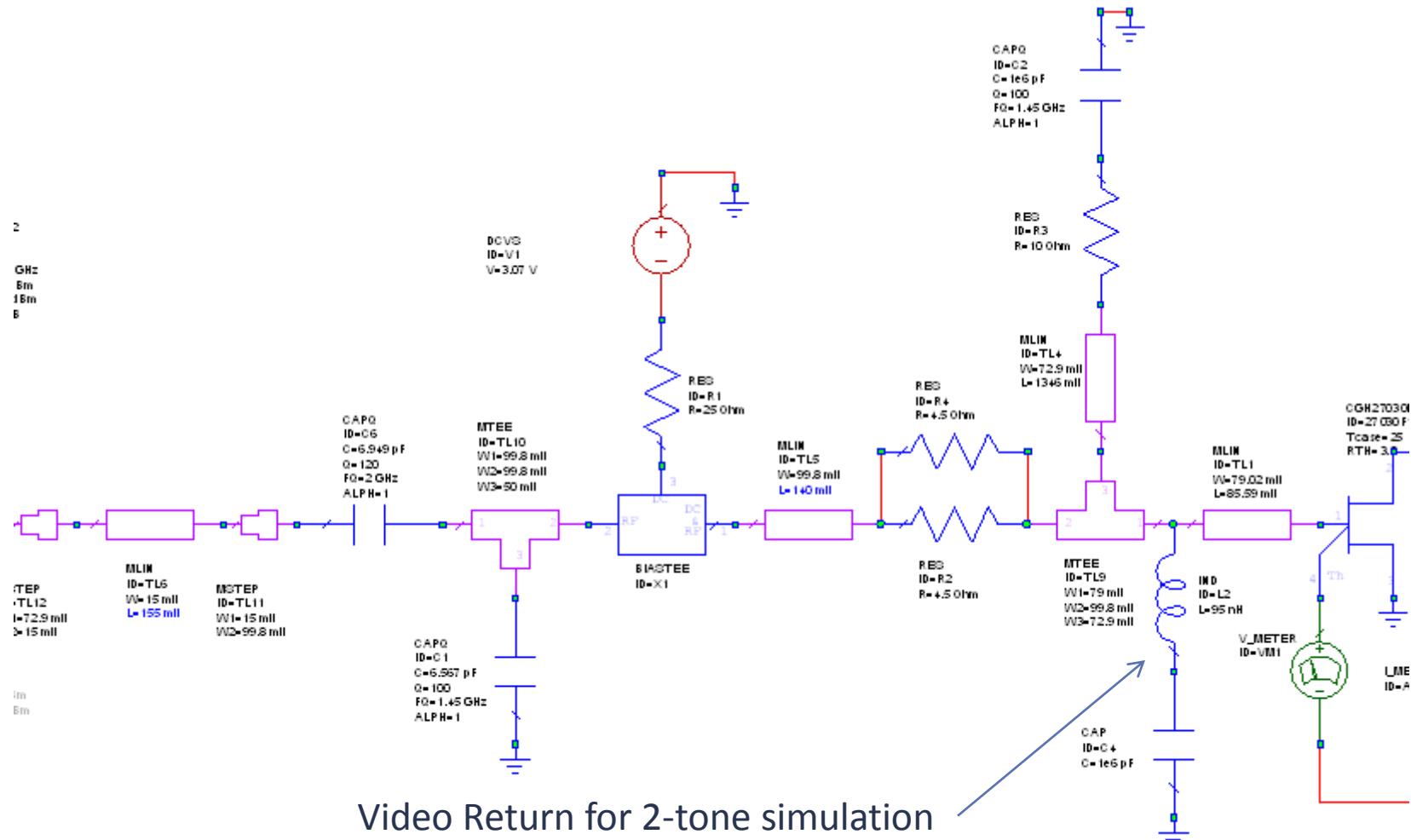


Video Return for 2-tone simulation


# Detail of Output Match

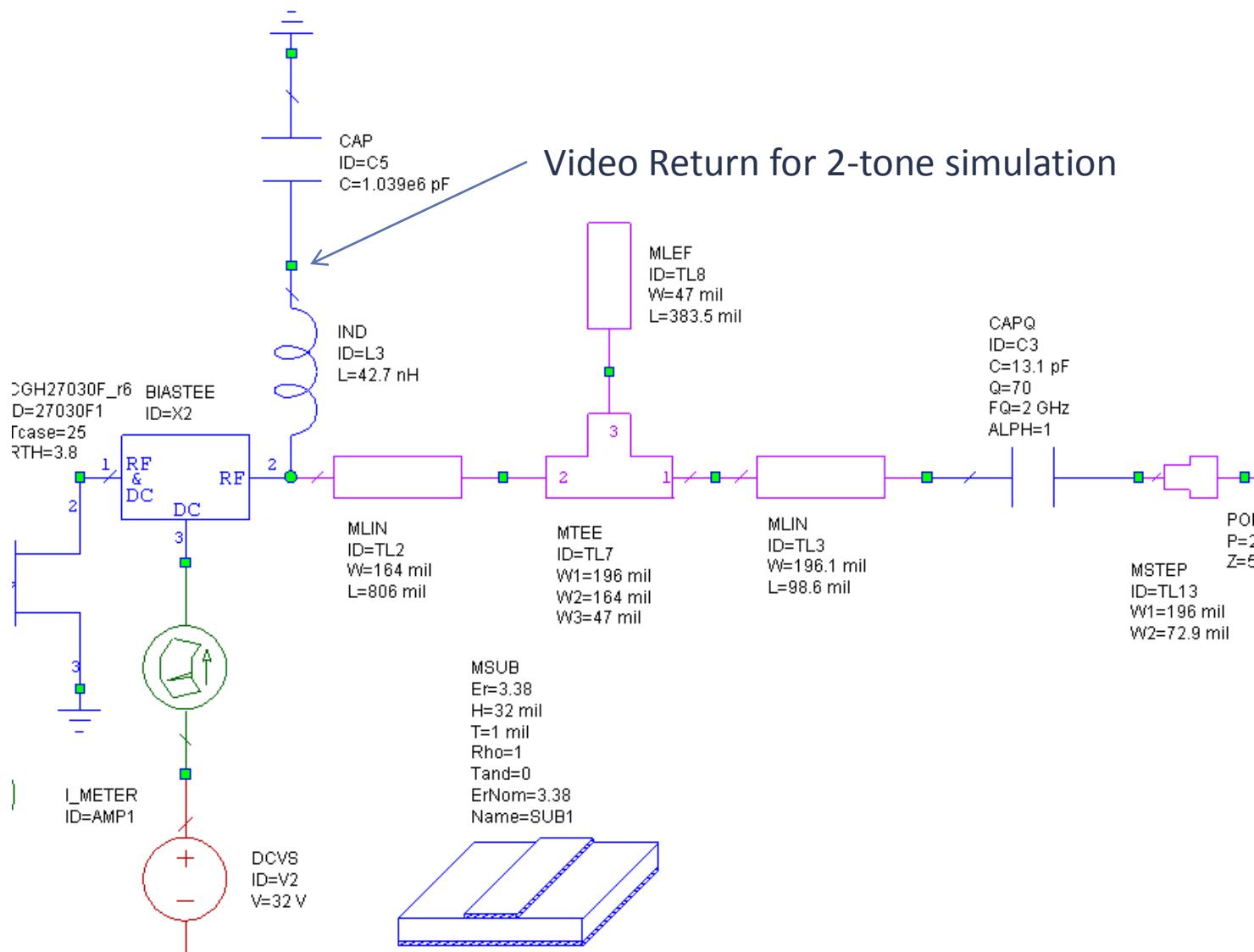


# Small Signal Characteristics

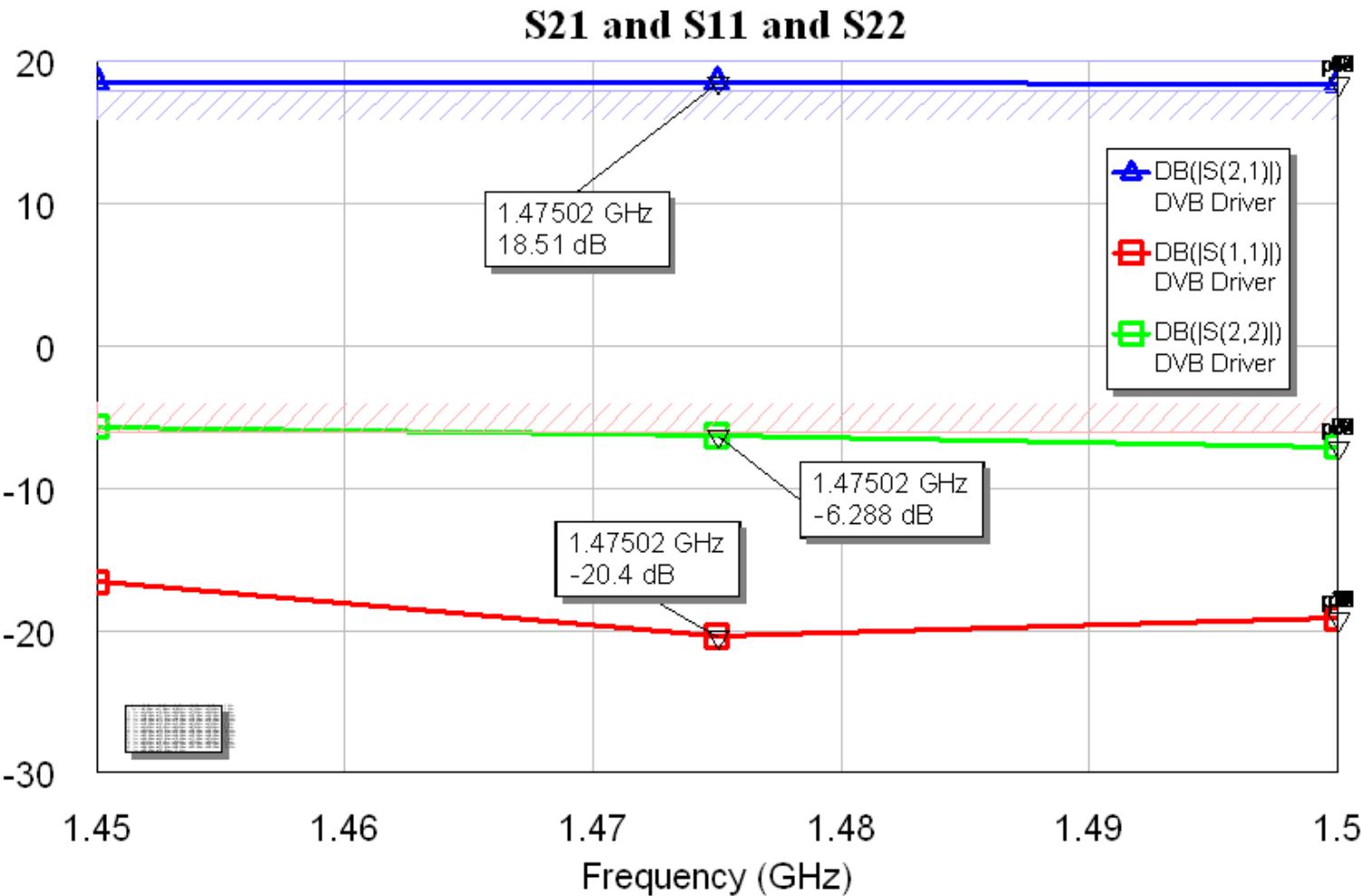


# Wideband Small Signal Characteristics

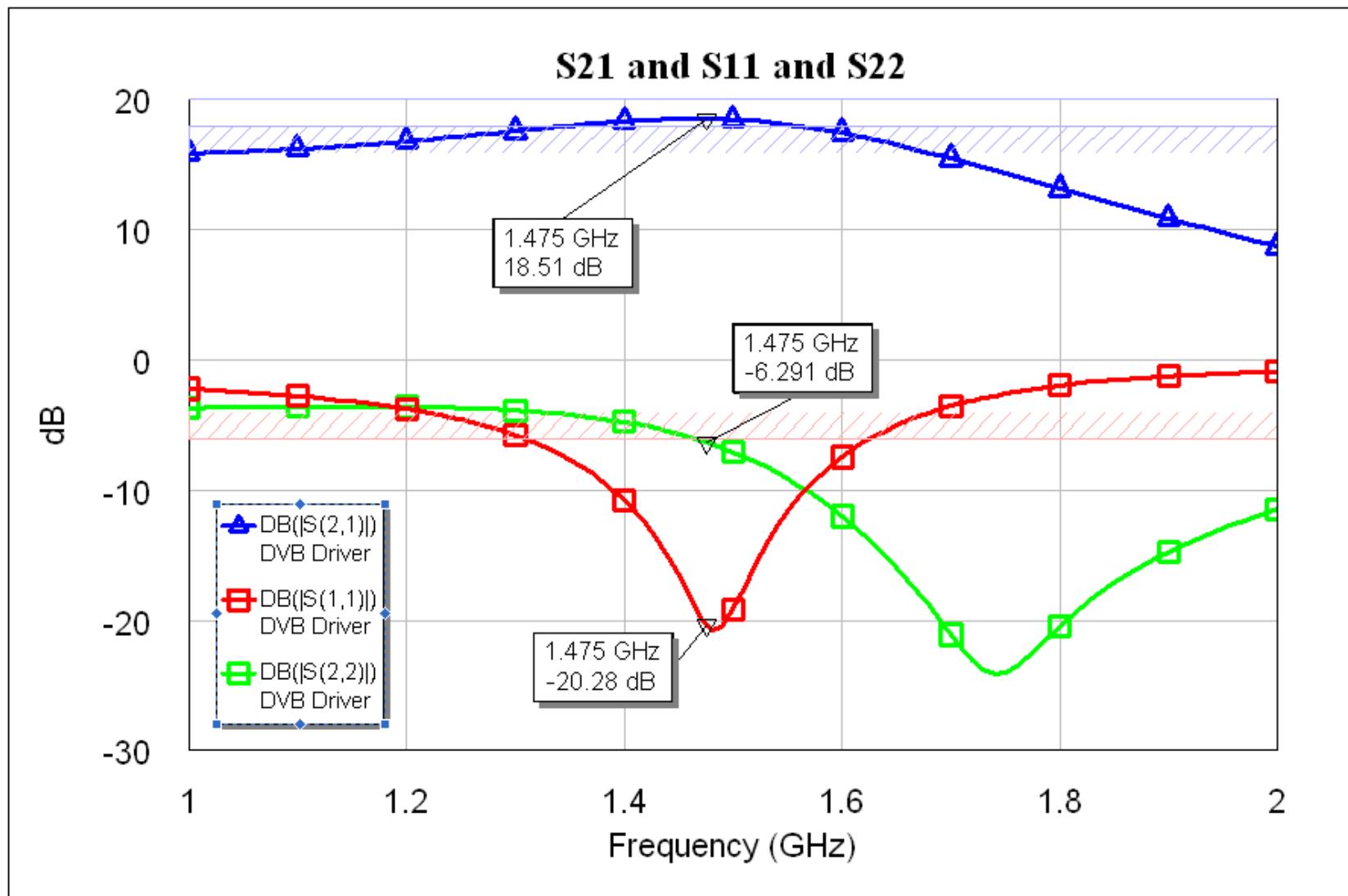


# Maximum Gain and Stability Factor K

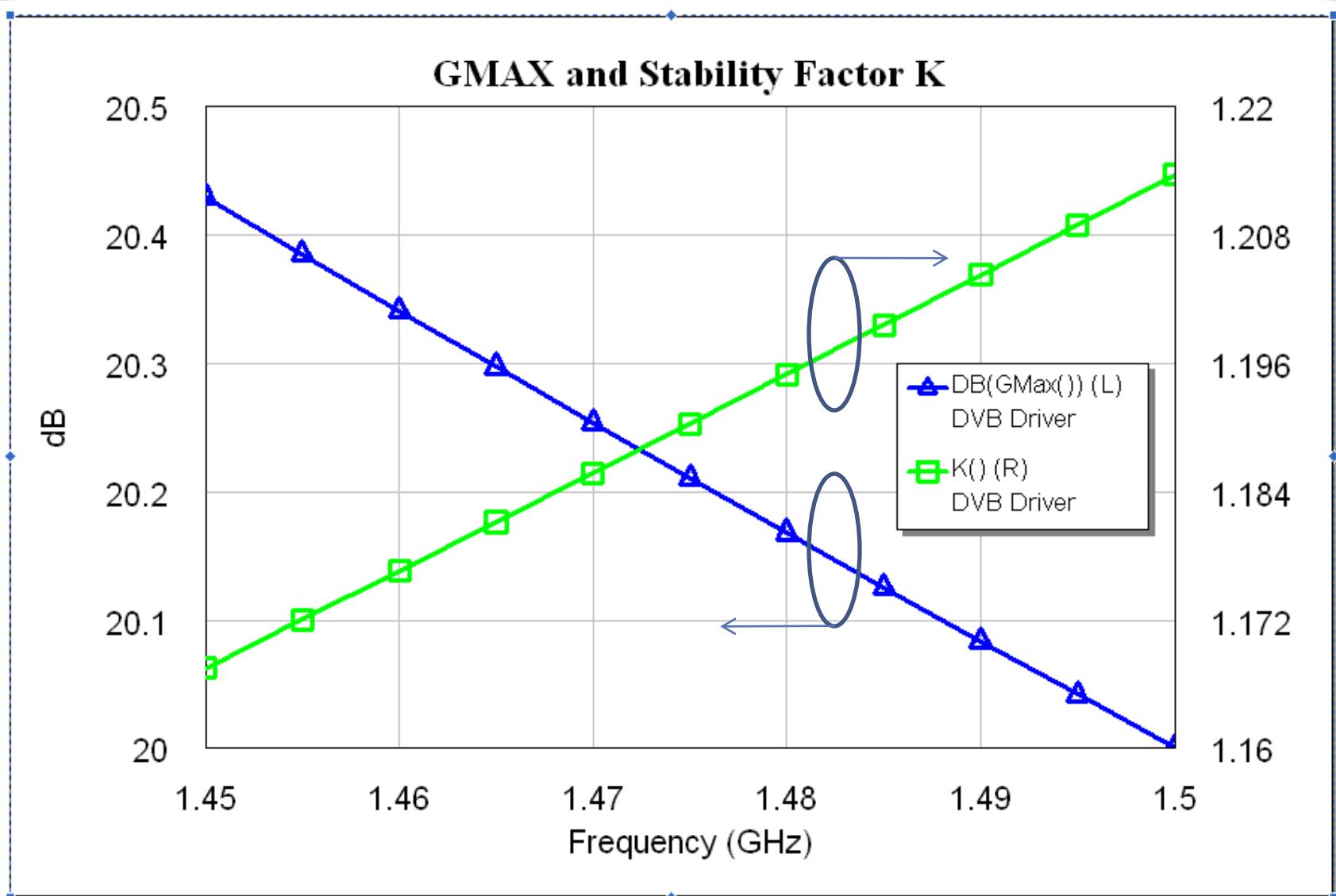


# Power Characteristics (1.475 GHz)

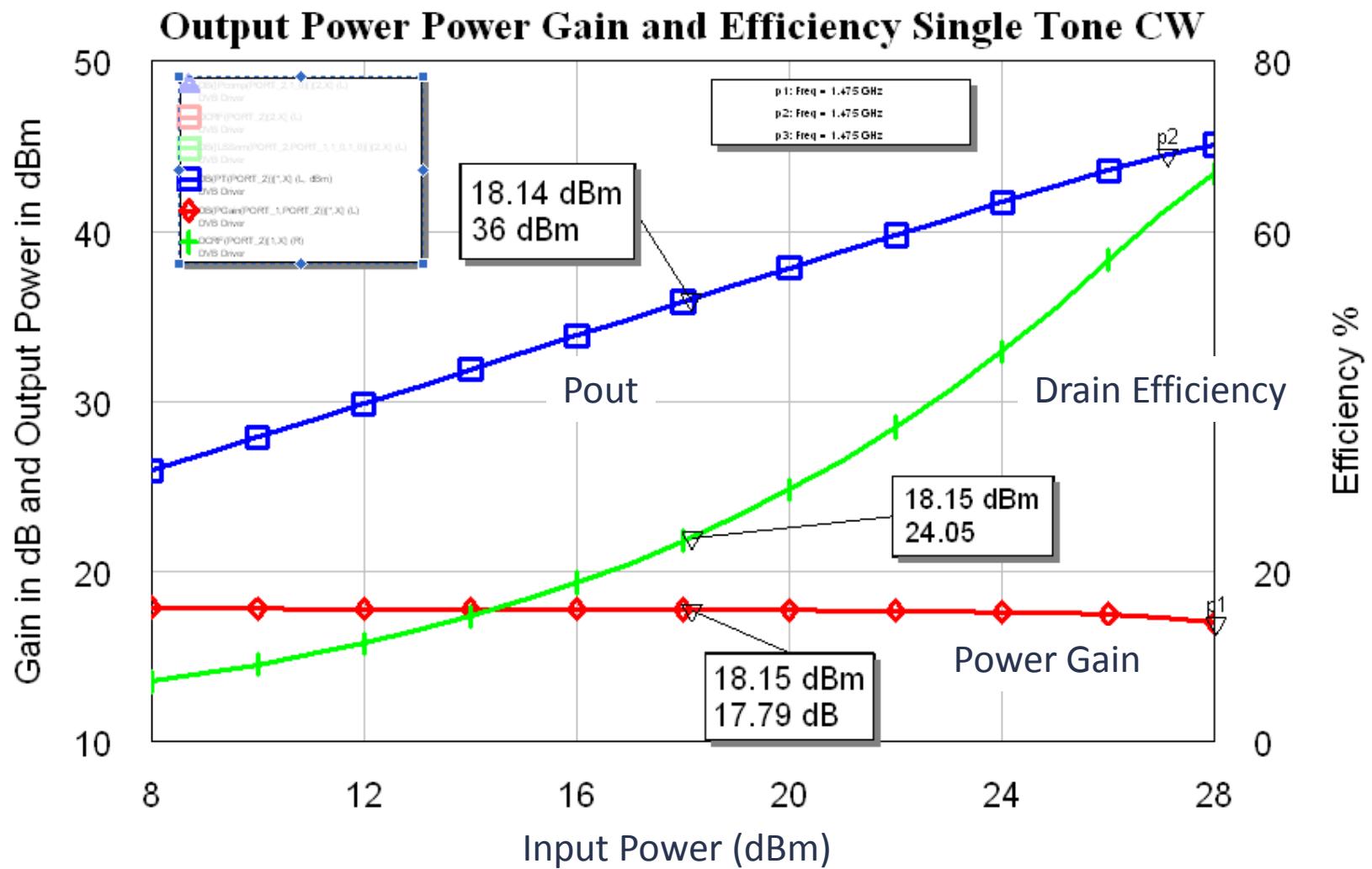

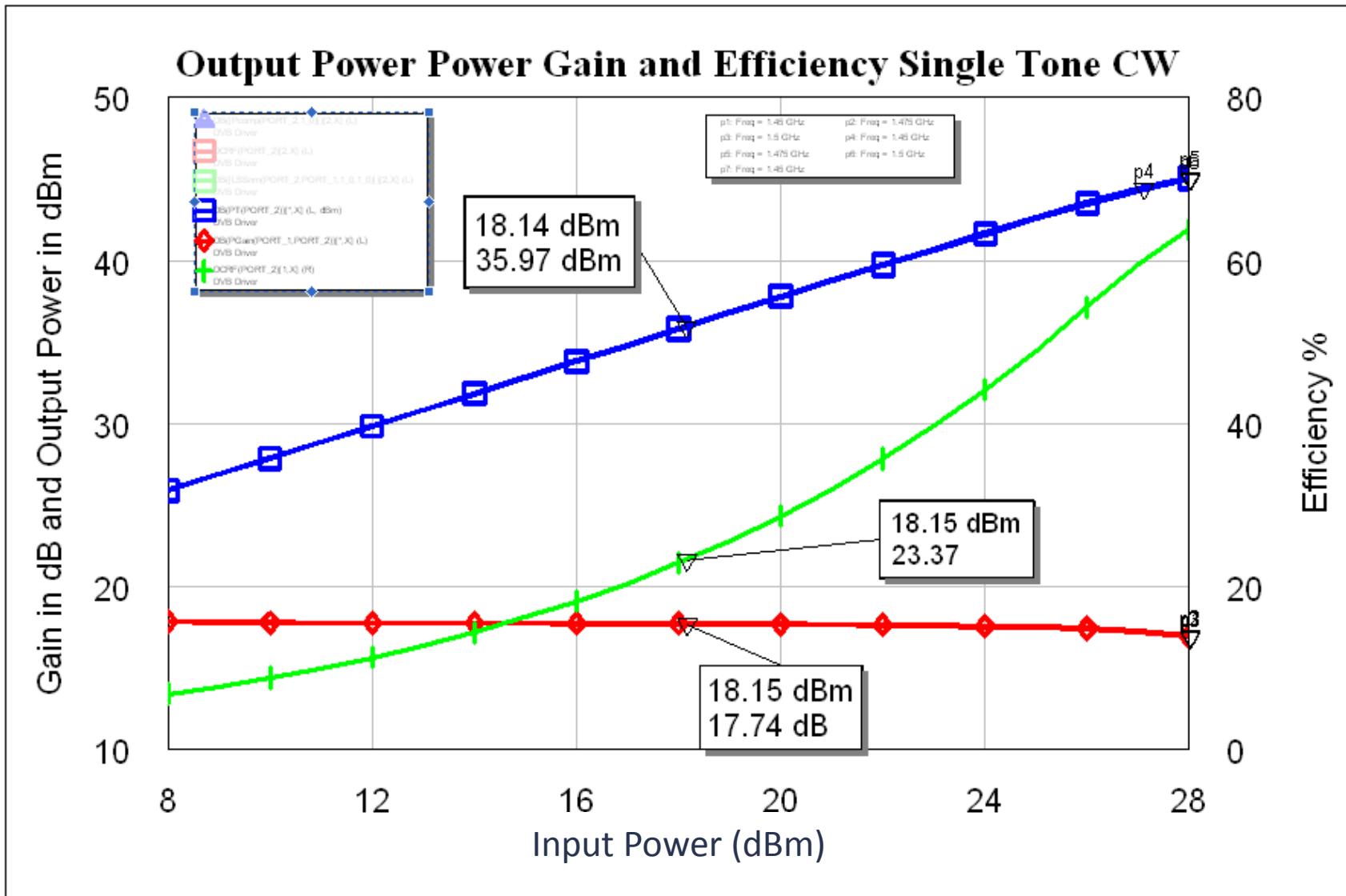
## **Power Characteristics at Band Center and Edges**



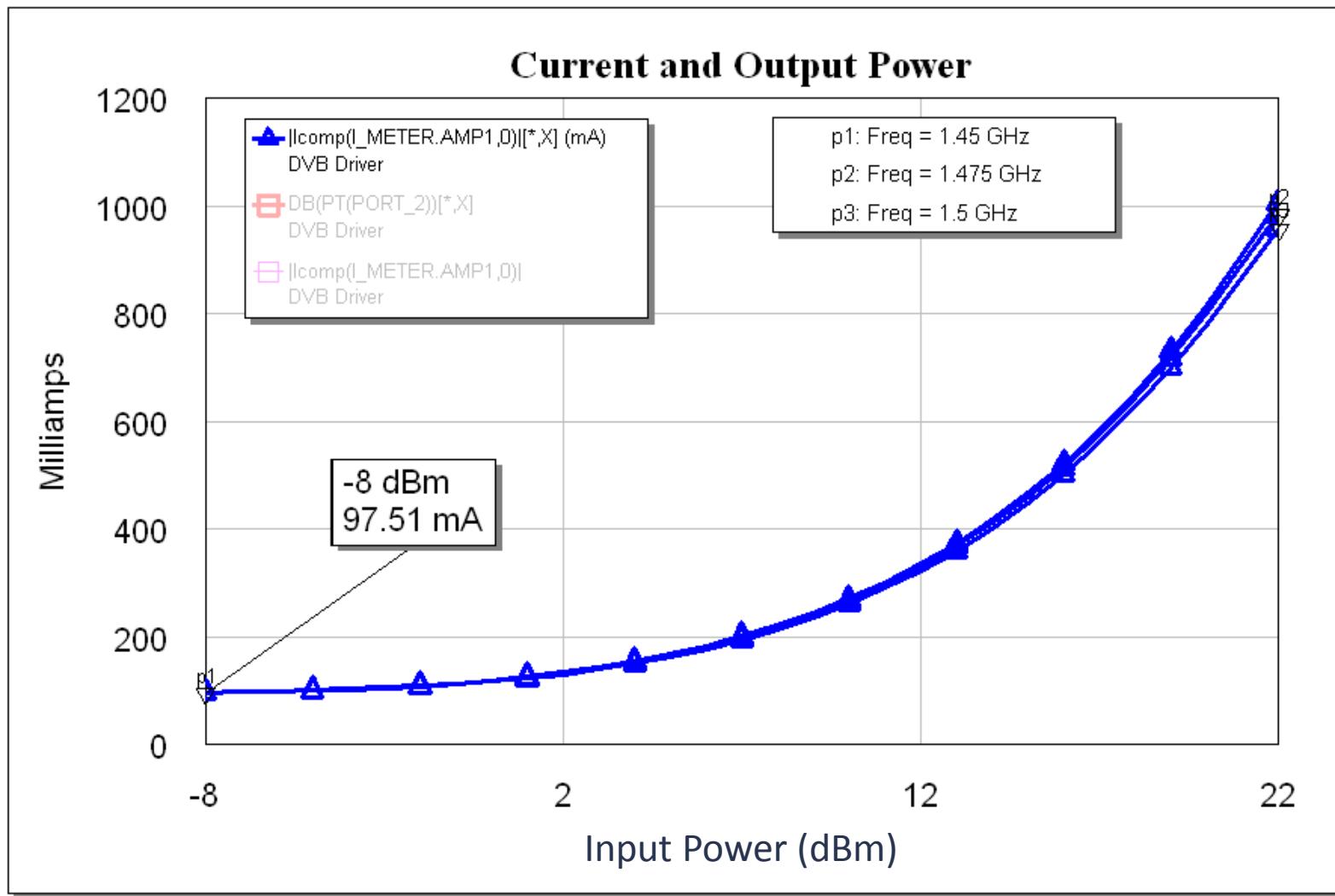
# DC Current versus RF Drive level (2-tone)


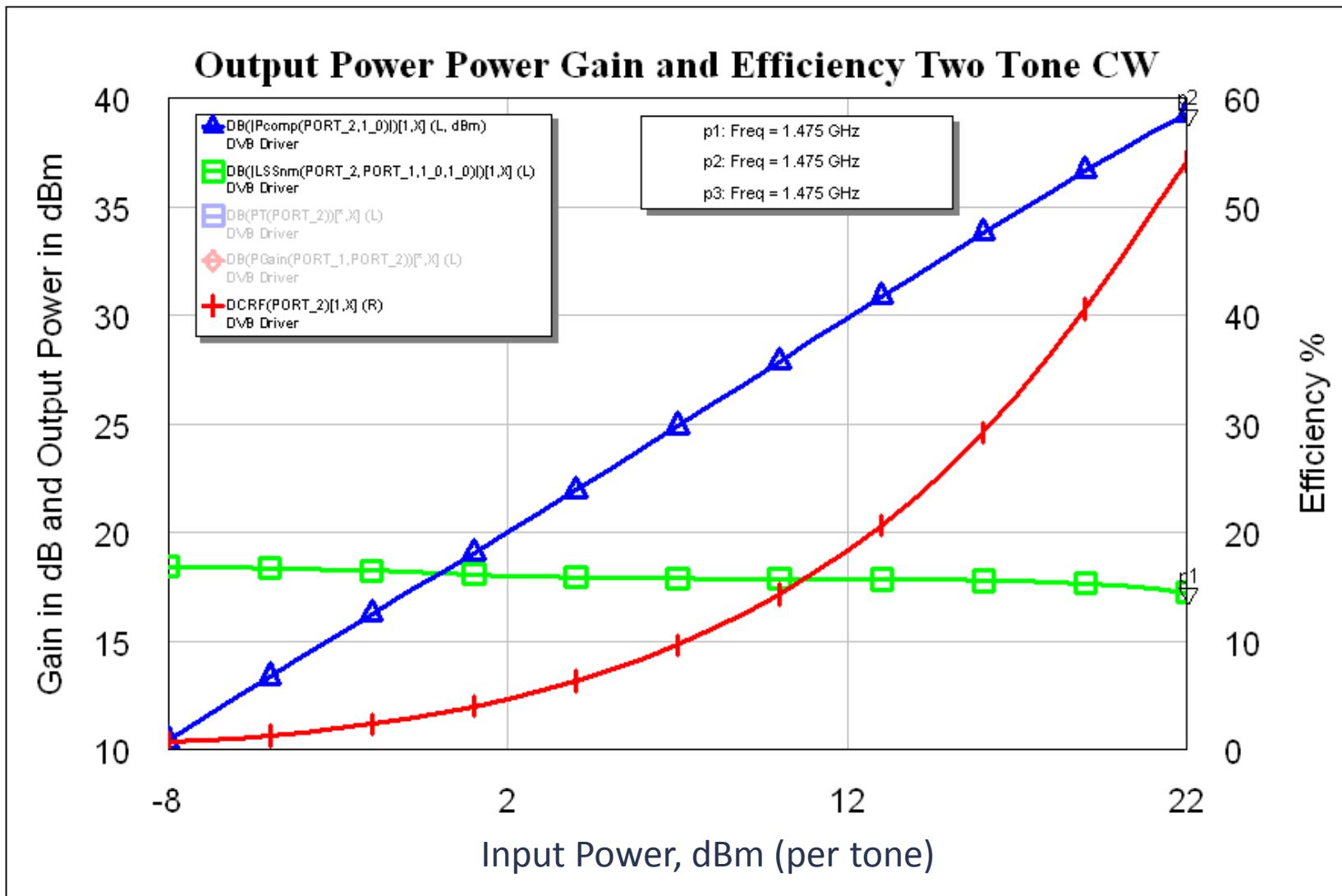
# 2 Tone Power Characteristics (1.475 GHz)



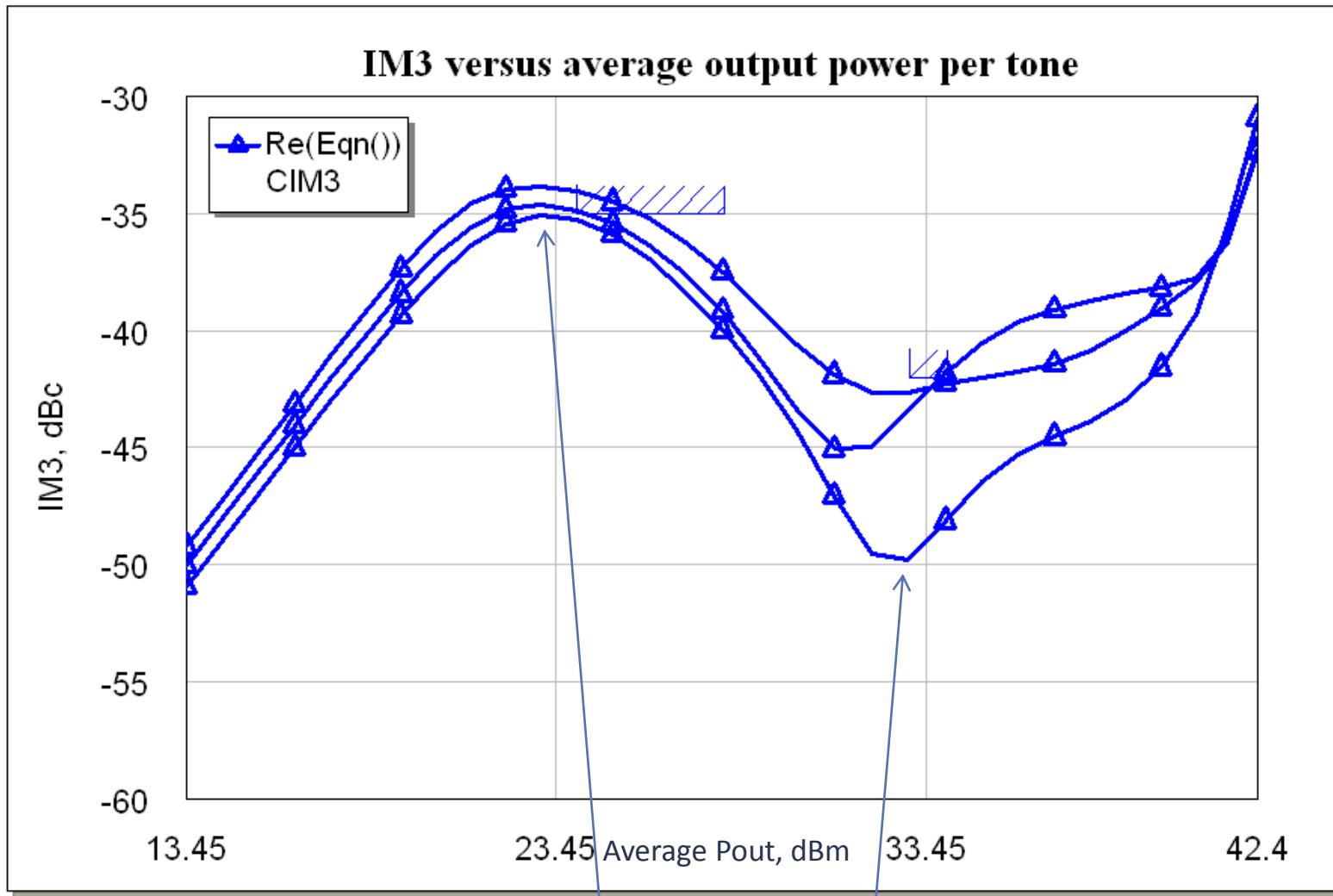
# 3<sup>rd</sup> order intermodulation products at band center and band edges



"Classic" back-off hill and sweet spot

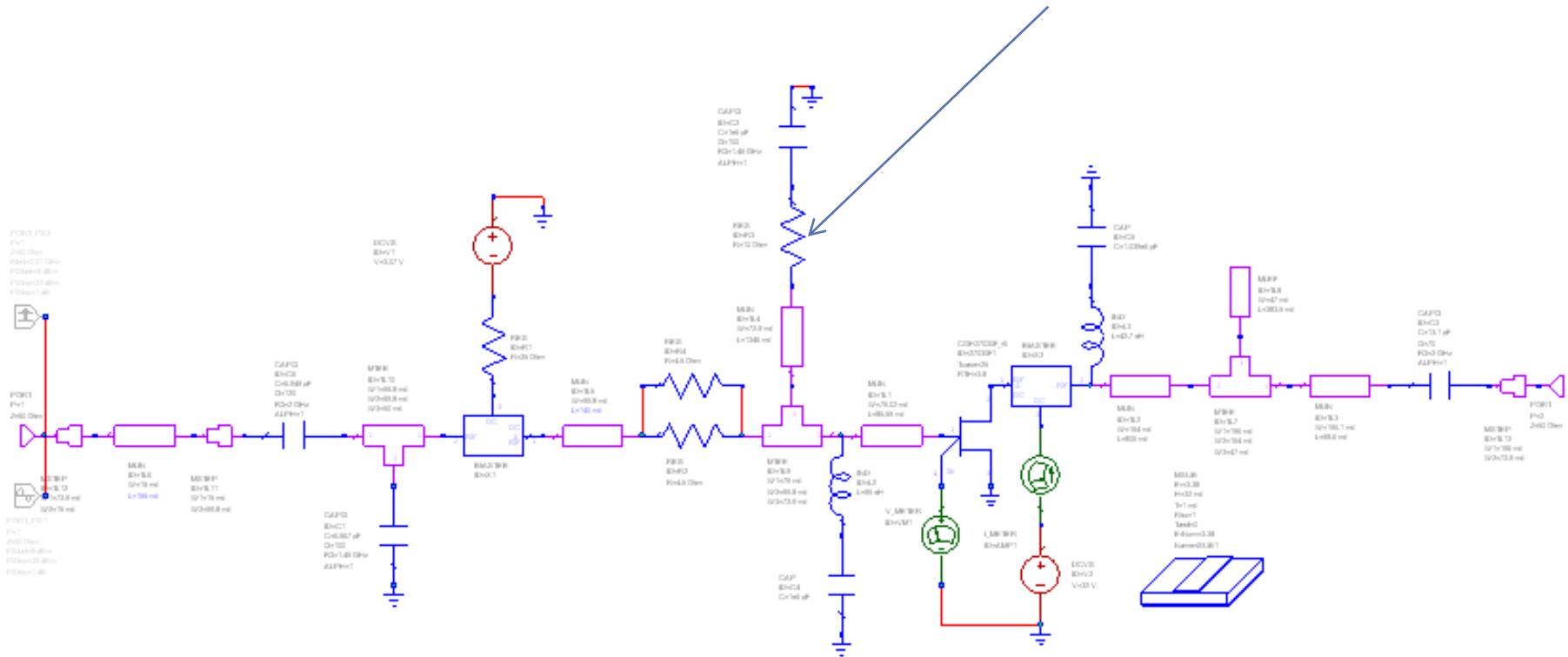
# **Very low frequency stability**

Additional 90 degree 50 ohm line at 1.45 GHz  
loaded with 10 ohm “de-Qing” resistor



**CREE**
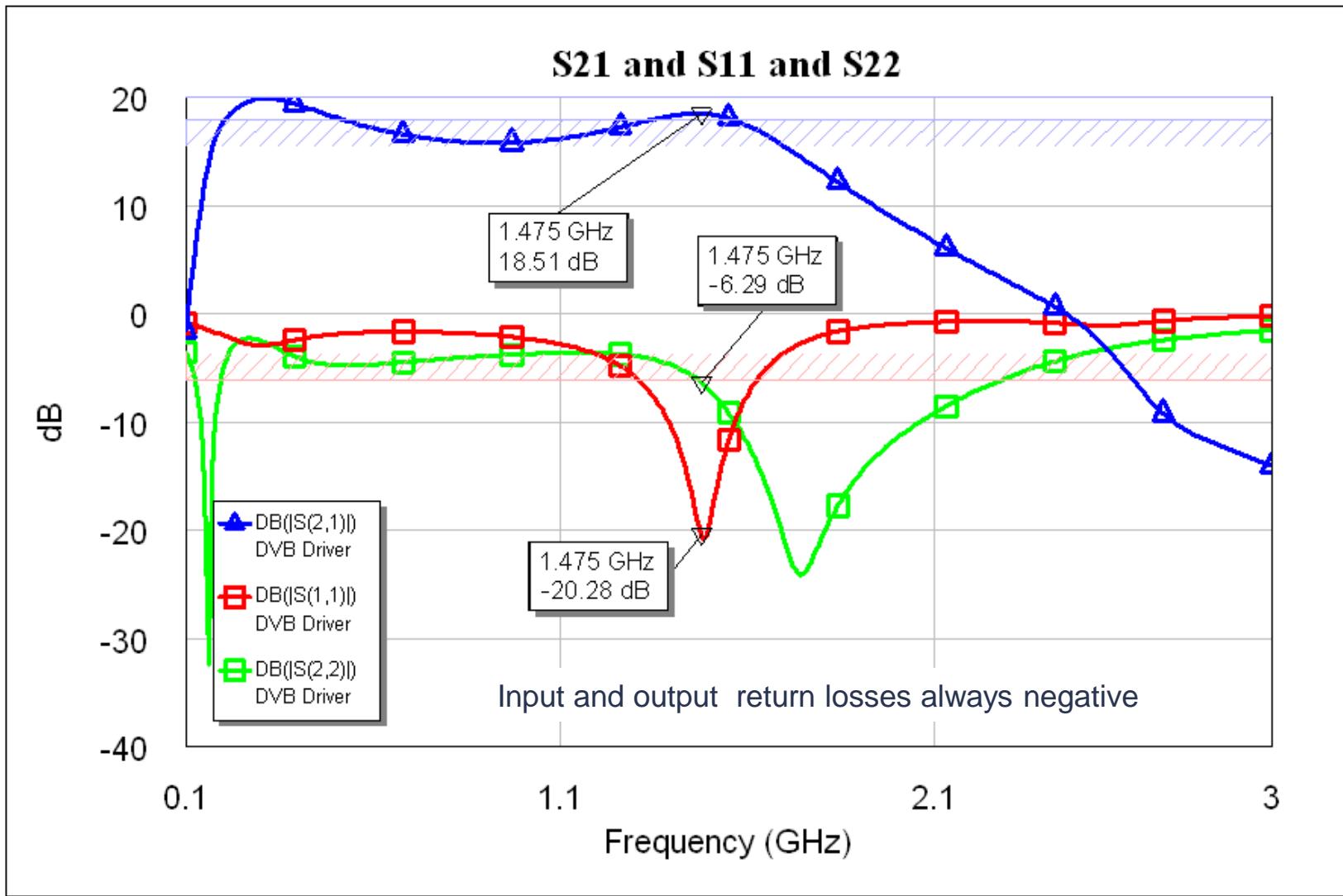
# Ultra wideband small signal characteristics



# **Example 9**


## **Doherty Amplifier Example**

### **(CDPA21480)**

# Summary

- Operating Frequency: 2.11 to 2.17 GHz (aim to have 200 MHz bandwidth)
- Modulation Signal: 3 GPP W-CDMA
- Gain: > 14 dB
- Peak Output Power: 480 Watts
- Average Output Power: 80 Watts
- Drain Efficiency at  $P_{AVE}$ : 50%
- DPD Corrected ACLR1: -50 dBc
- Operating Voltage: 28 volts
- Uses 2 x CGH21240F pre-matched transistors
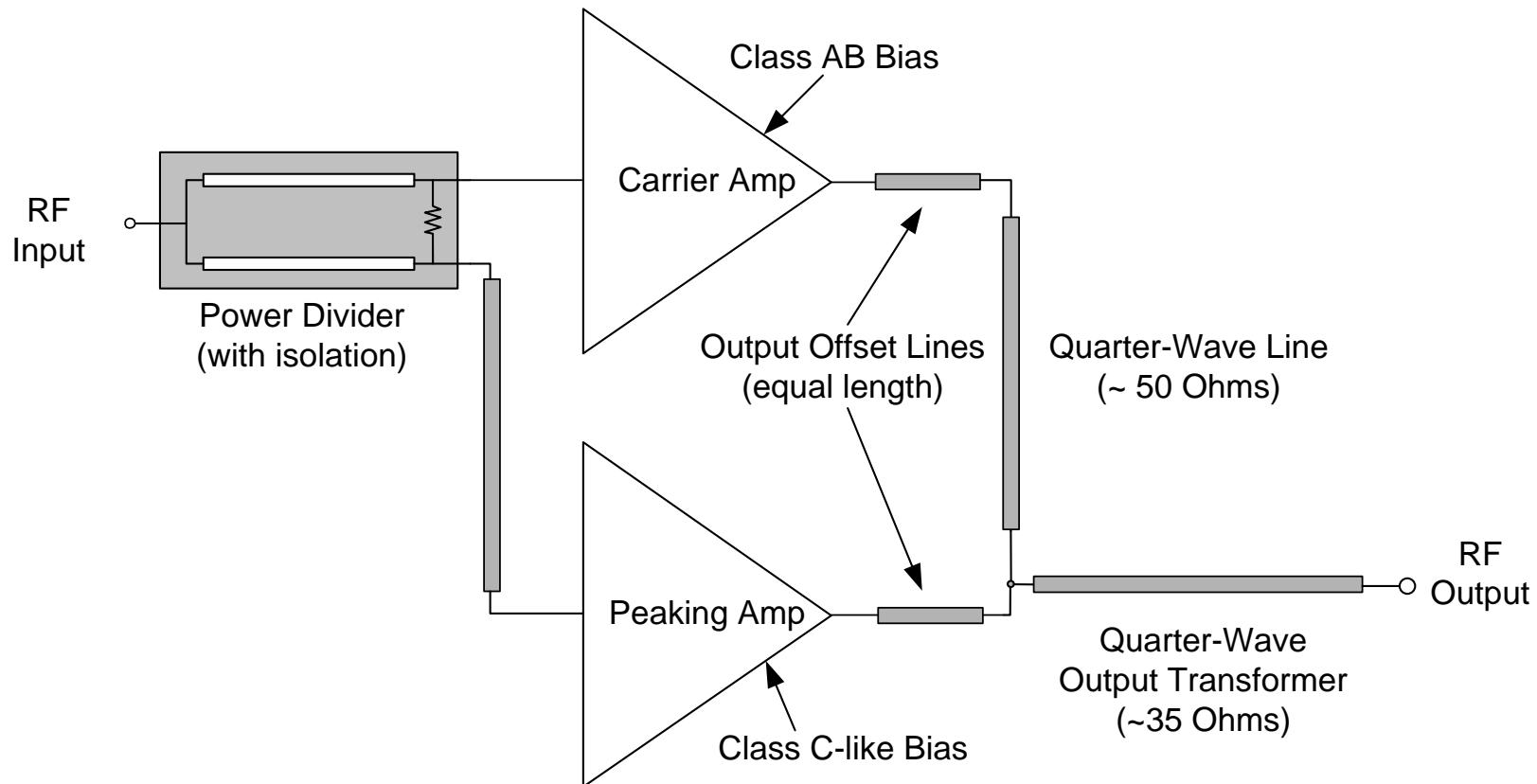
# Two-way Doherty Amplifier Block Diagram




# Design Considerations



- Doherty Amplifier Design has many design aspects:
  - Input divider coupling ratio
  - Source impedances for carrier and peaking amplifiers (including harmonics)
  - Load impedances for carrier and peaking amplifiers (including harmonics)
  - Output offset line lengths
  - “Quarter wave” input and output line lengths
  - Output transformer impedance
  - Carrier and peaking amplifier quiescent bias levels
- 2-tone intermodulation products need to be < -25 to -30 dBc to meet SEM requirements after DPD
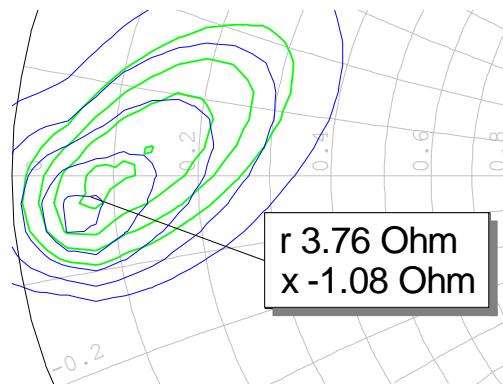
# Simulations of Doherty Amplifier 2-tone Intermodulation rejection



Source Pull of Peaking Amplifier at  $P_{IN}=37$  dBm



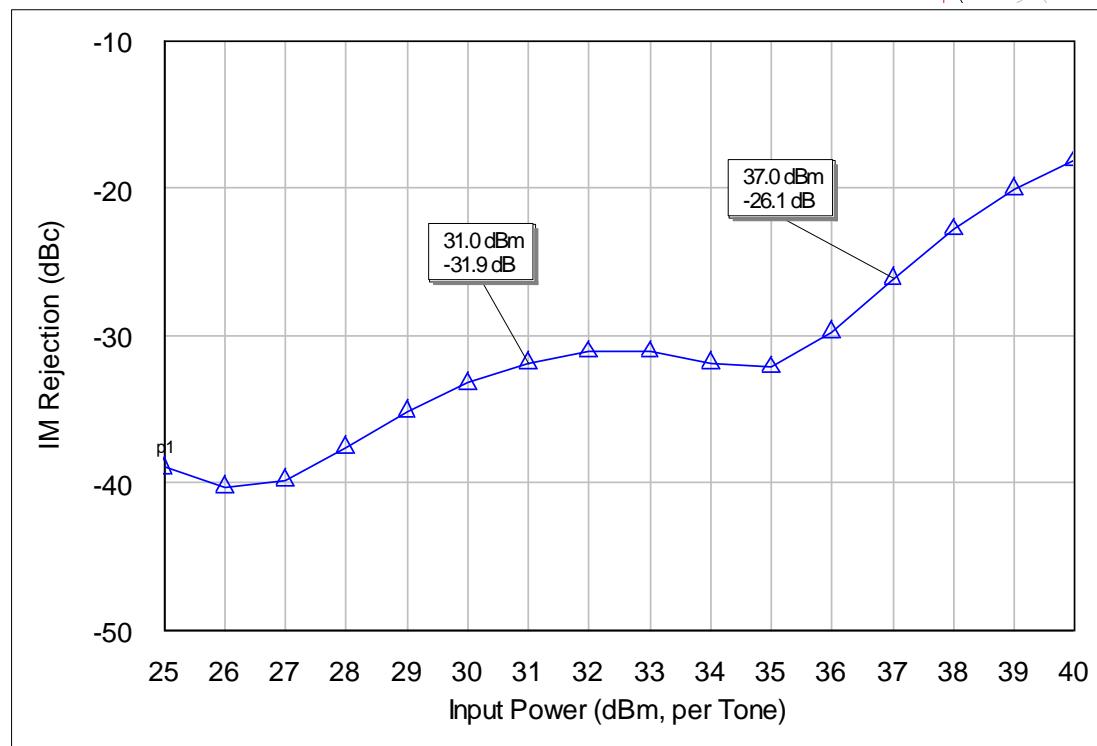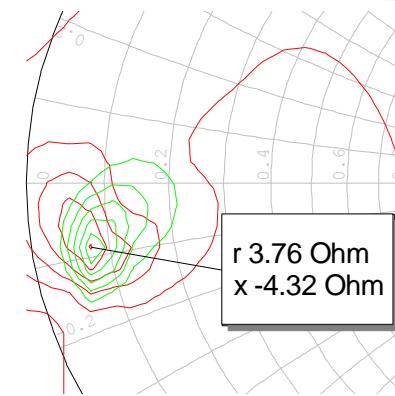
Source Pull of Peaking Amplifier at  $P_{IN}=31$  dBm



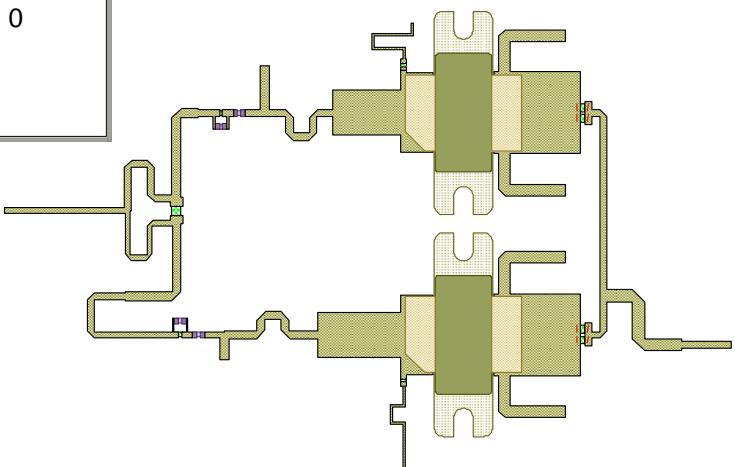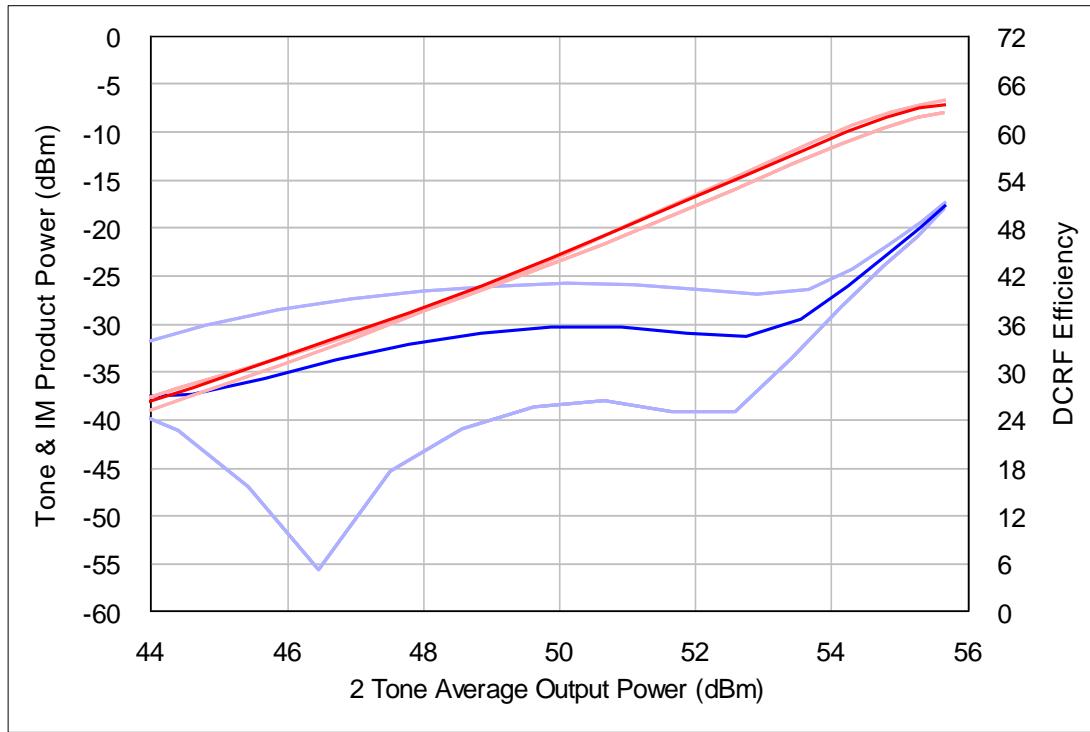
# Further simulation of Doherty 2-tone IM rejection and Efficiency versus lengths of output offset lines



# UMTS 480 watt peak power DPA hardware

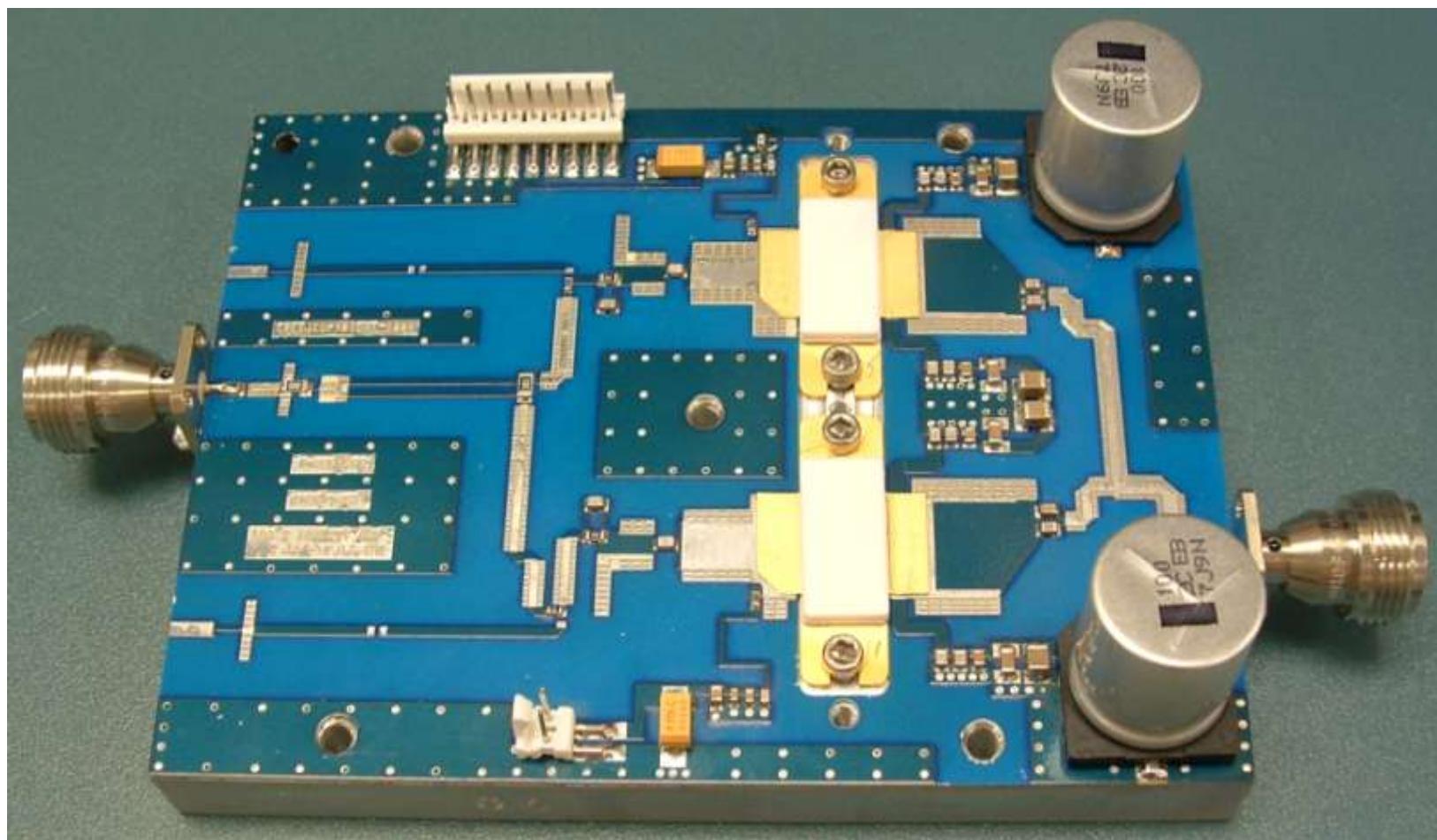

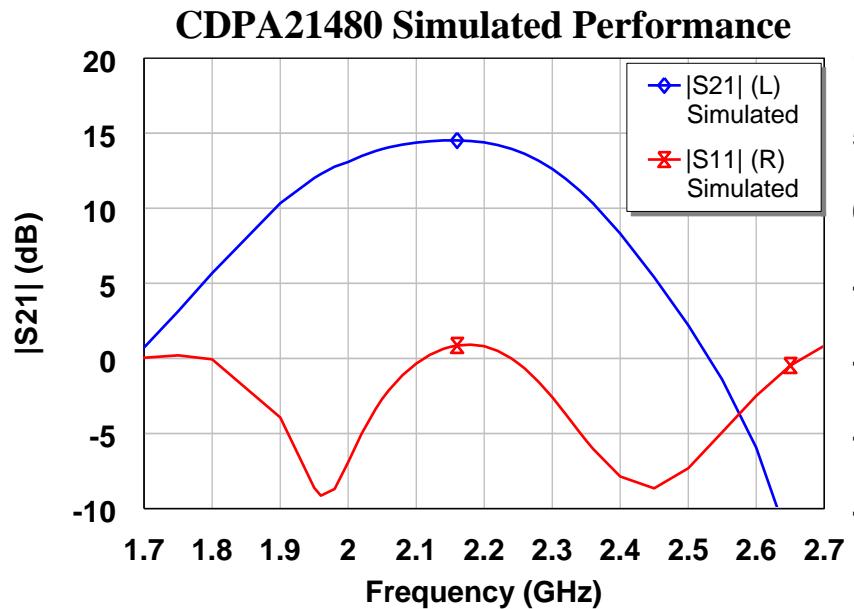
# Simulated and Measured Performance of CDPA21480



Measured W-CDMA Transfer Curves

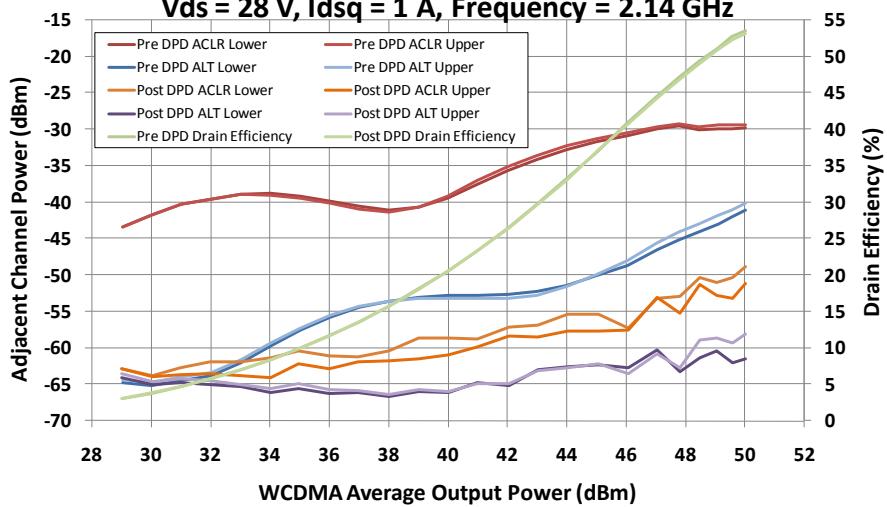
## Simulated Small Signal Response

**CDPA21480 WCDMA Transfer with and without DPD**  
**Single Channel WCDMA, 6.5 dB PAR with CFR**  
**V<sub>ds</sub> = 28 V, I<sub>dsq</sub> = 1 A, Frequency = 2.14 GHz**



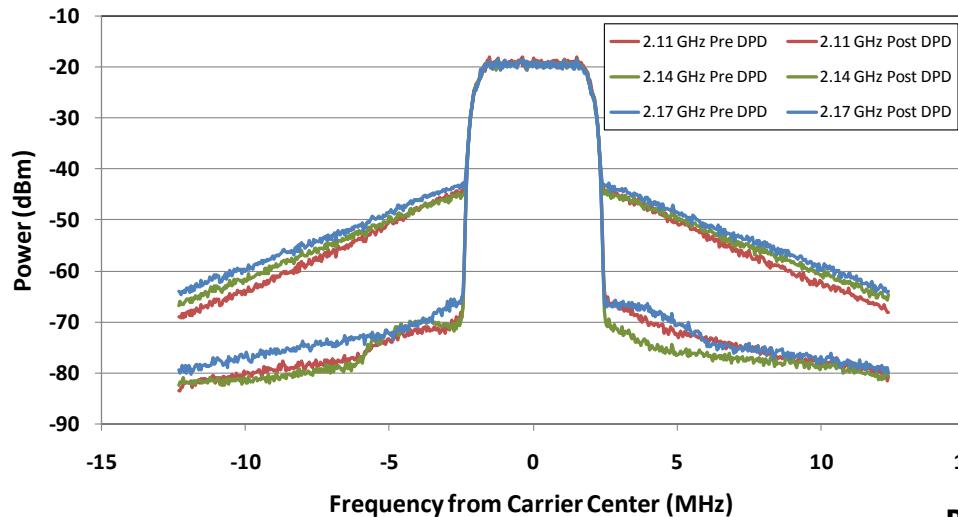
# Single and 2 carrier W-CDMA Output Spectra (with and without DPD)

CDPA21480 Spectrum at 2.11, 2.14 & 2.17 GHz  
 $P_{AVE} = 49$  dBm 1c WCDMA PAR = 6.5 dB with CFR



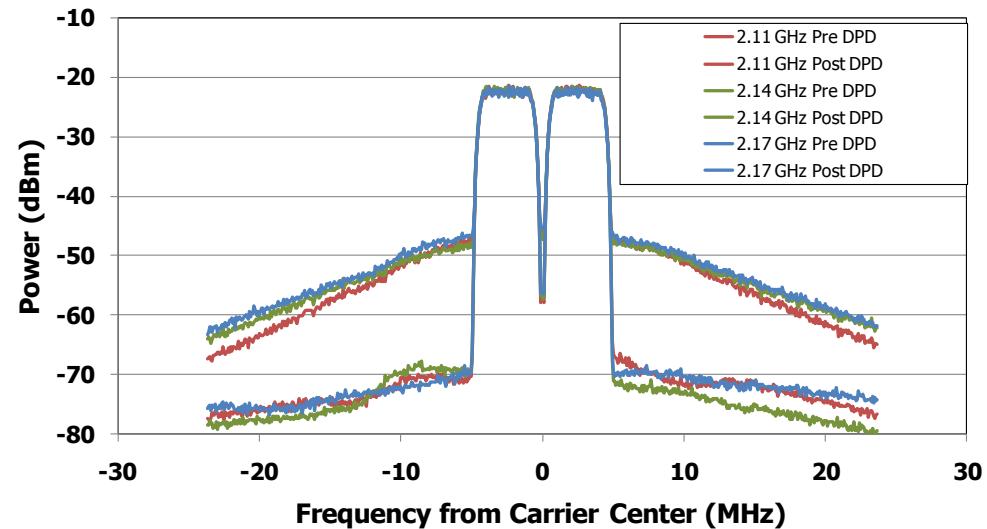CDPA21480 Spectrum at 2.11, 2.14 & 2.17 GHz  
 $P_{AVE} = 49$  dBm 2c WCDMA PAR = 7.5 dB with CFR



# **Example 10**


## **Comparing Balanced Amplifier and Doherty Performances**

# Summary



- CGH09120F transistor used in single-ended PA design
  - That design applied to a balanced amplifier as well as a Doherty amplifier to compare back-off efficiencies

Single-ended amplifier performance:


Parameter	
Operating Frequency	700 to 950 MHz
Modulation signal (for testing purposes)	2 carrier W-CDMA with 10 MHz bandwidth and PAR of 7.5 dB
Output Power (average)	20 Watts
Drain efficiency	35%
DPD corrected ACLR1	-50 dBc
Operating Voltage	28 volts

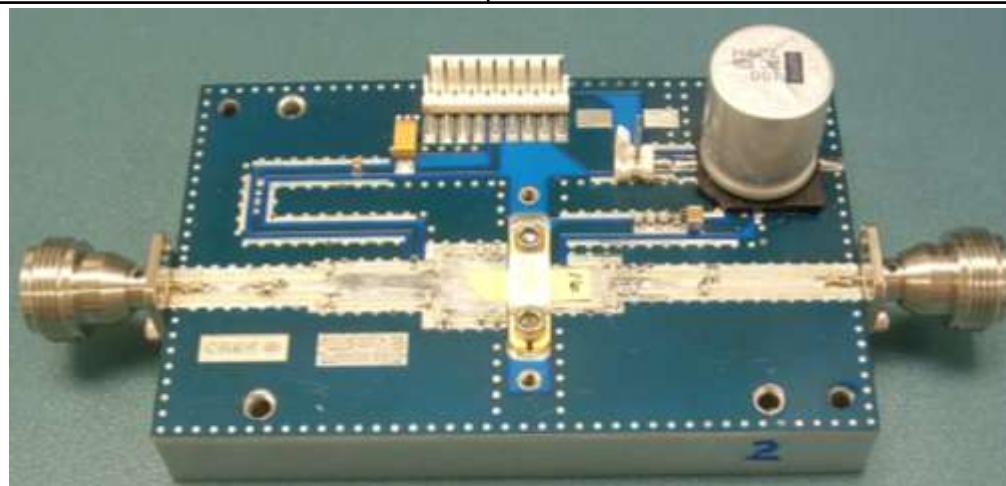

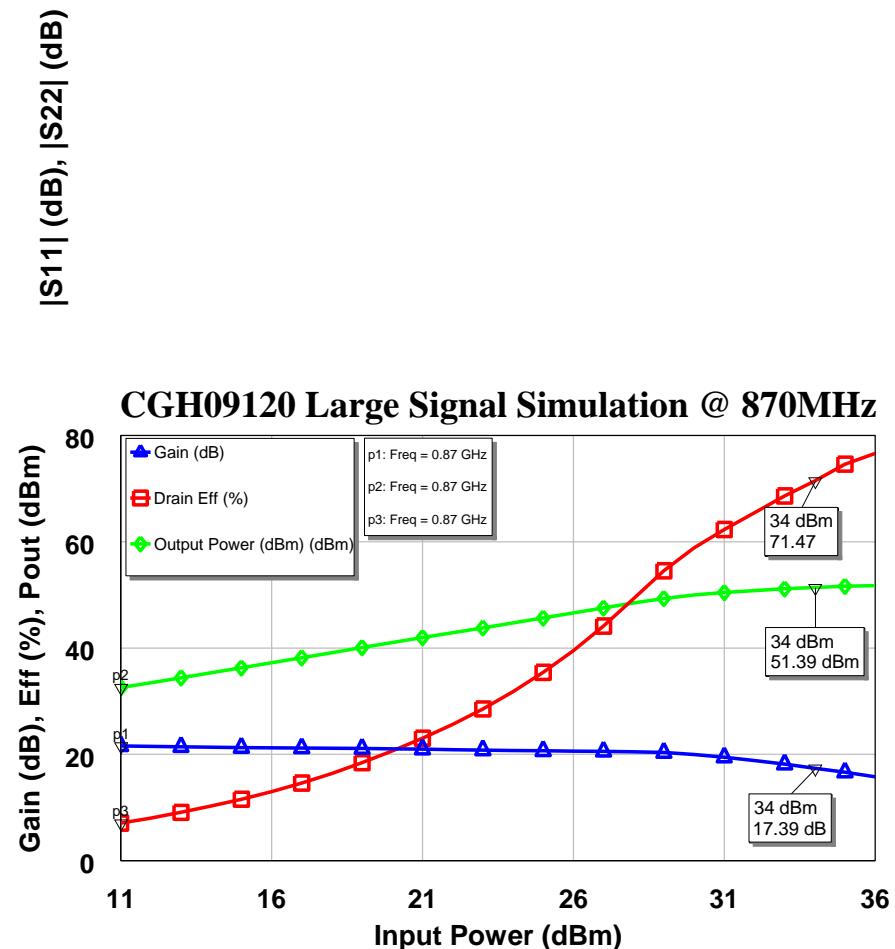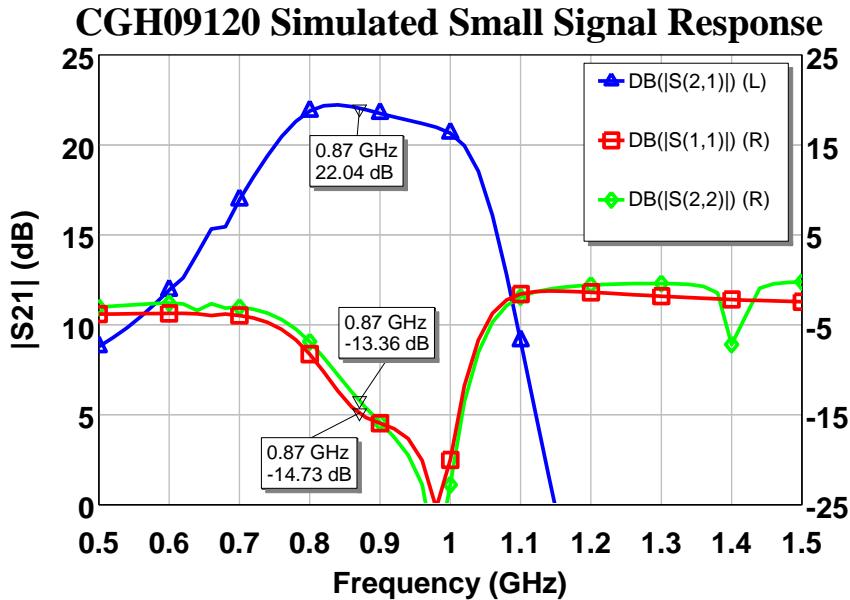
# Simulated Small and Large signal performance of CGH09120F demonstration amplifier



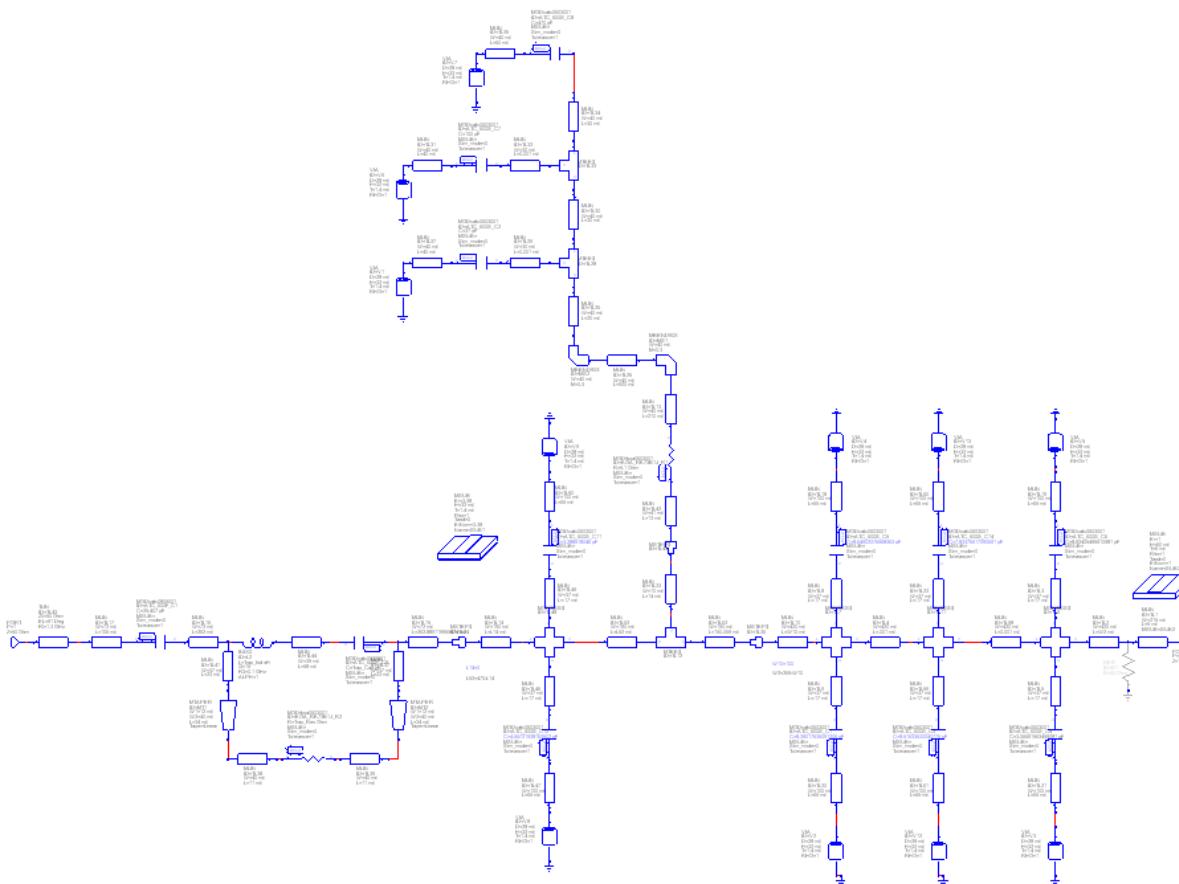
# Input Matching Network of Single-Ended PA



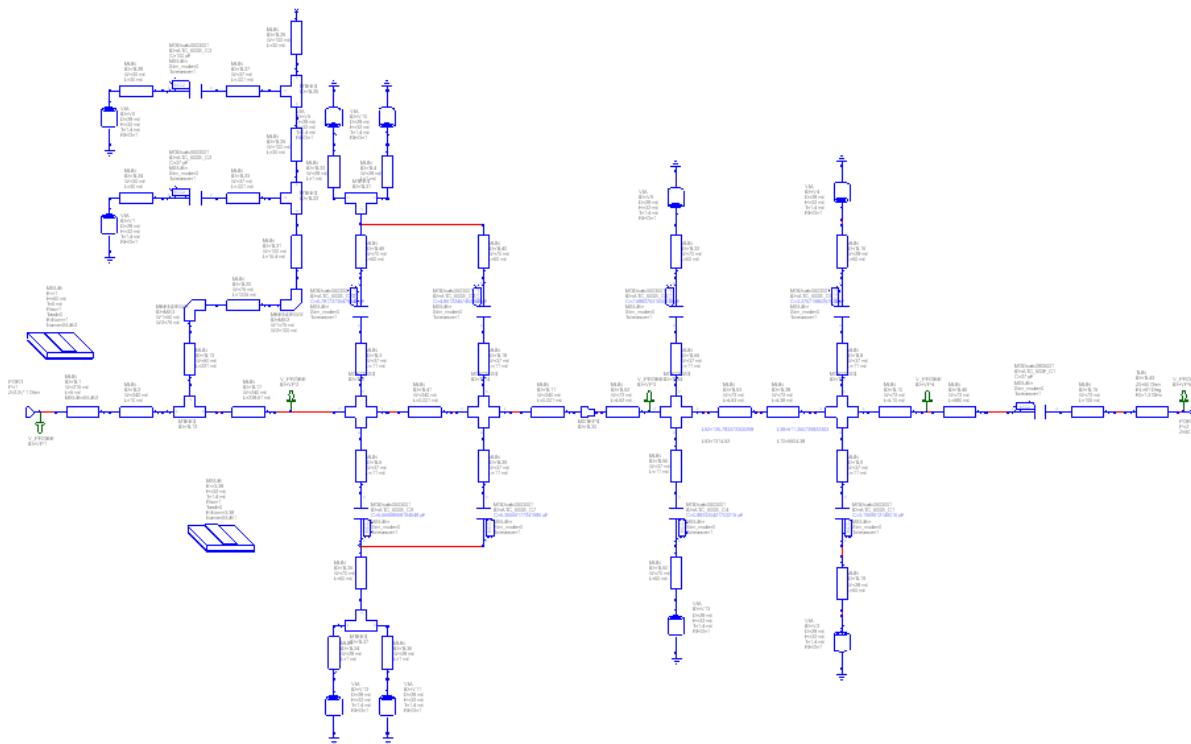
# Output Matching Network of Single-Ended PA


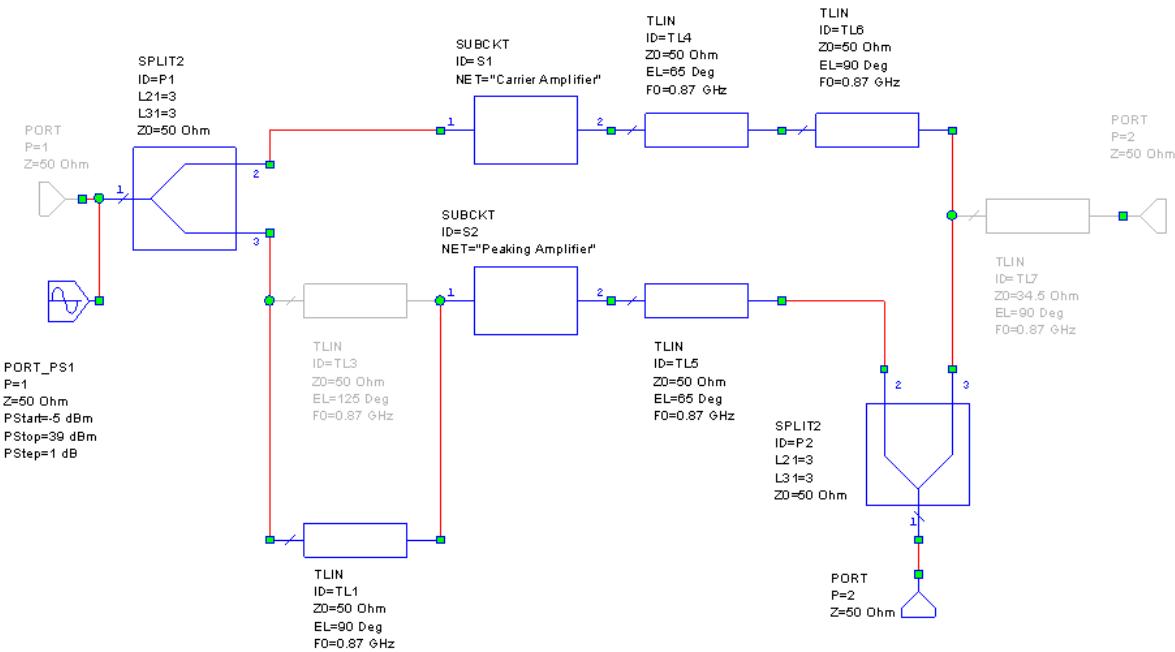
# Top Level Schematic set up as balanced PA



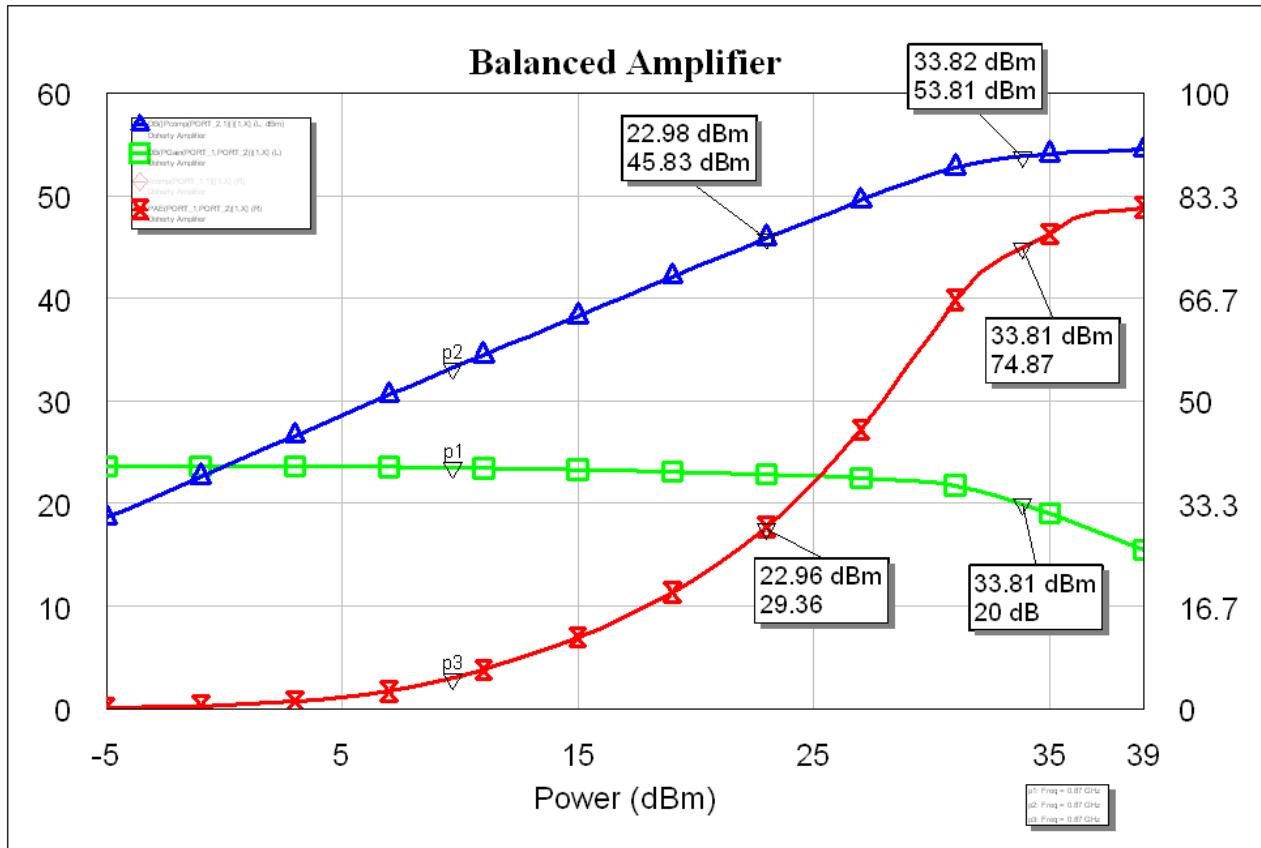
# Simulation of Large-Signal Performance of Balanced Amplifier




Note the marker values at Peak Power and 8 dB Back-off
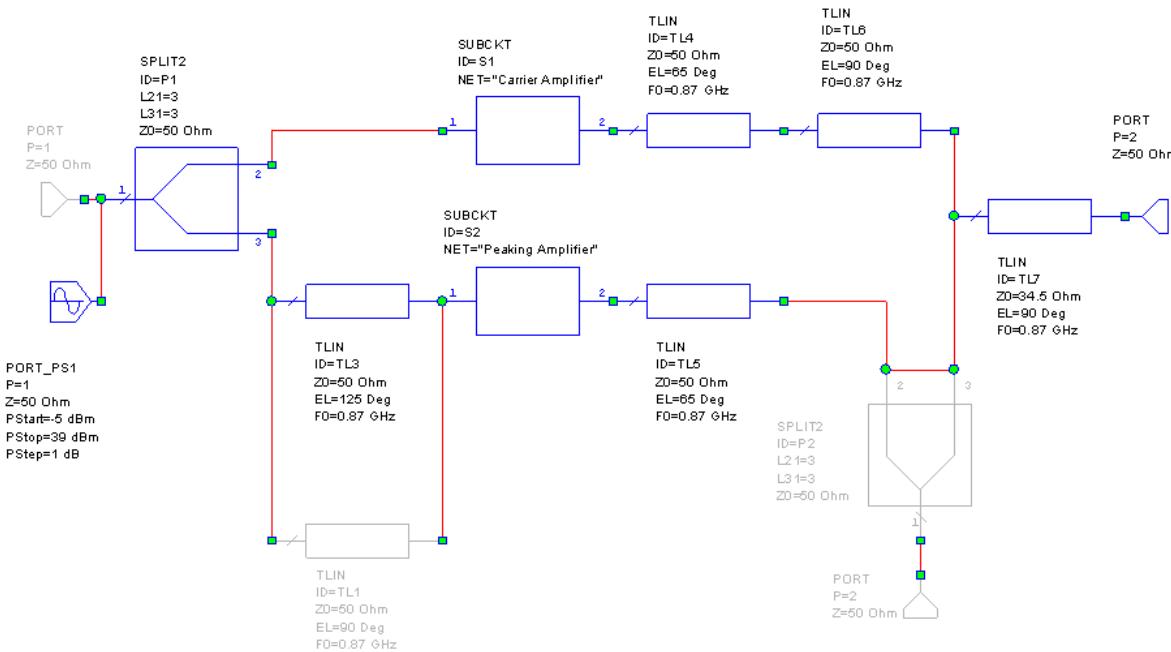
# Top level schematic set up as Doherty PA


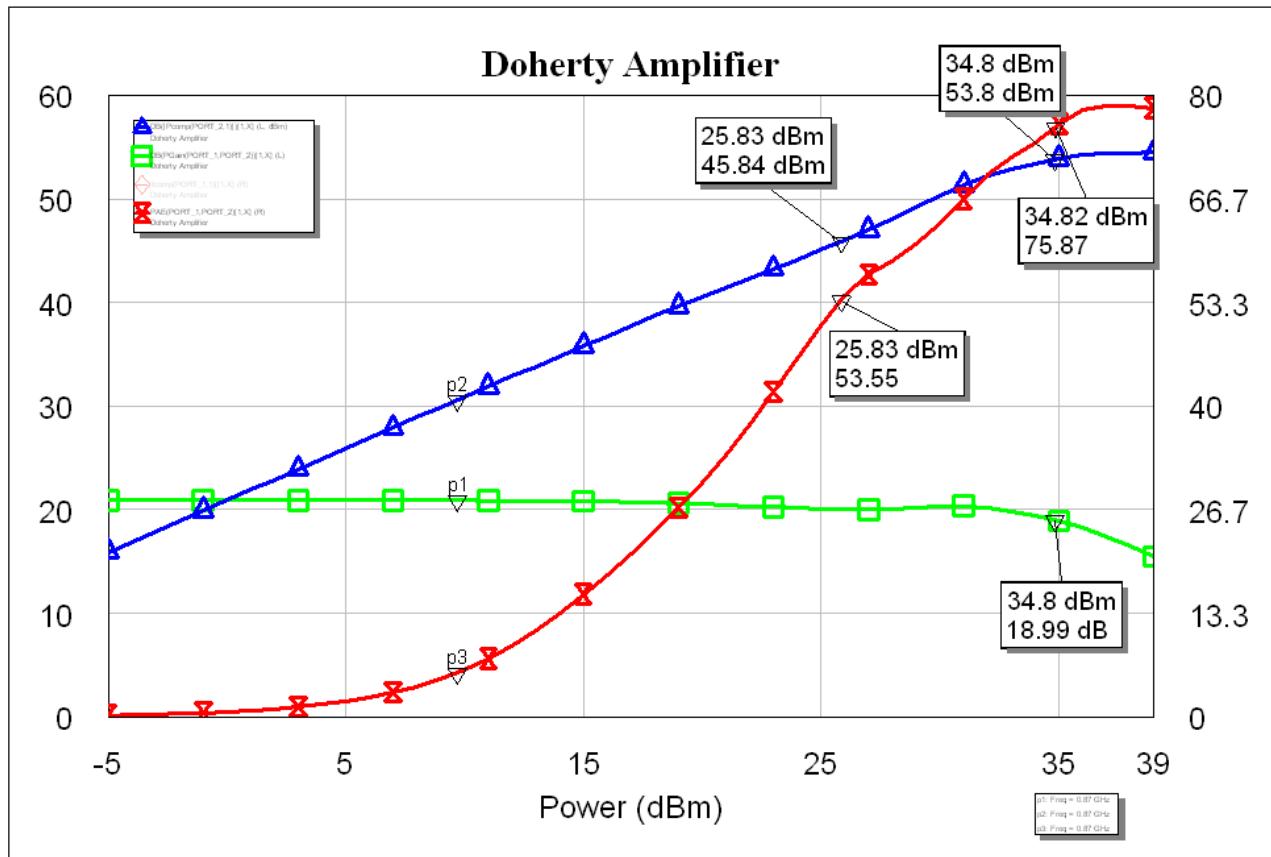
# Simulation of Large-Signal Performance of Doherty Amplifier



Note the marker values at Peak Power and 8 dB Back-off


## **Example 11**

# **Using the CGH4006P over 20 to 520 MHz**


# Summary

- The CGH40006P consists of a 2.16mm GaN HEMT in a small ceramic/metal pill package. The device is capable of providing 8 watts CW power
  - Microwave Office has been used to design a gate-to-drain feedback amplifier with additional reactive matching provided by lumped elements in a 50 ohm characteristic impedance;
  - Drain voltage set at 28 Volts; Idq for the transistor set at 65 mA
- Drain Efficiencies between 42 and 66% at Psat of 8 watts over 20 MHz to 520 MHz obtained
- Noise Figure Analysis of the PA also performed


# Schematic of PA

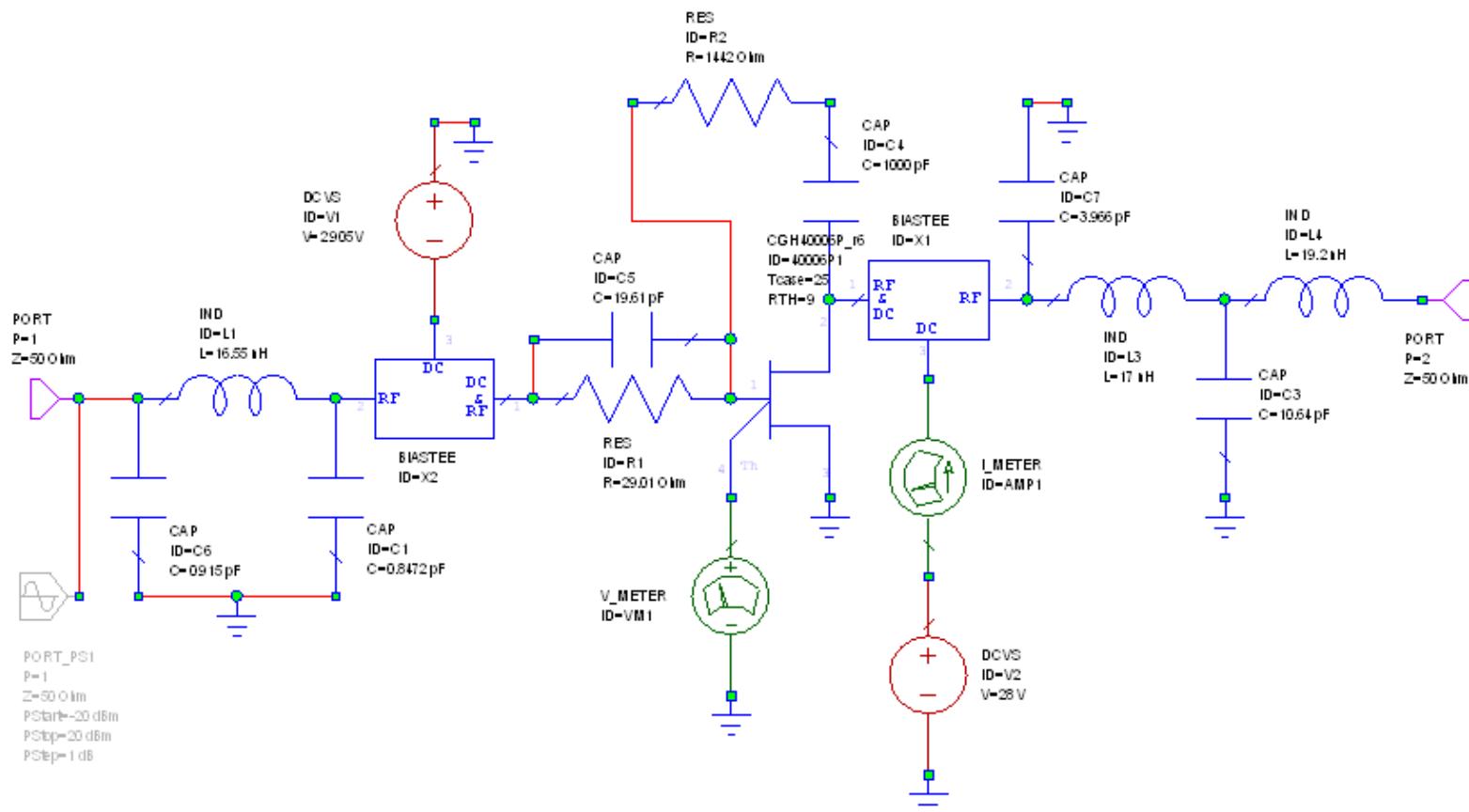


# Input Matching Network

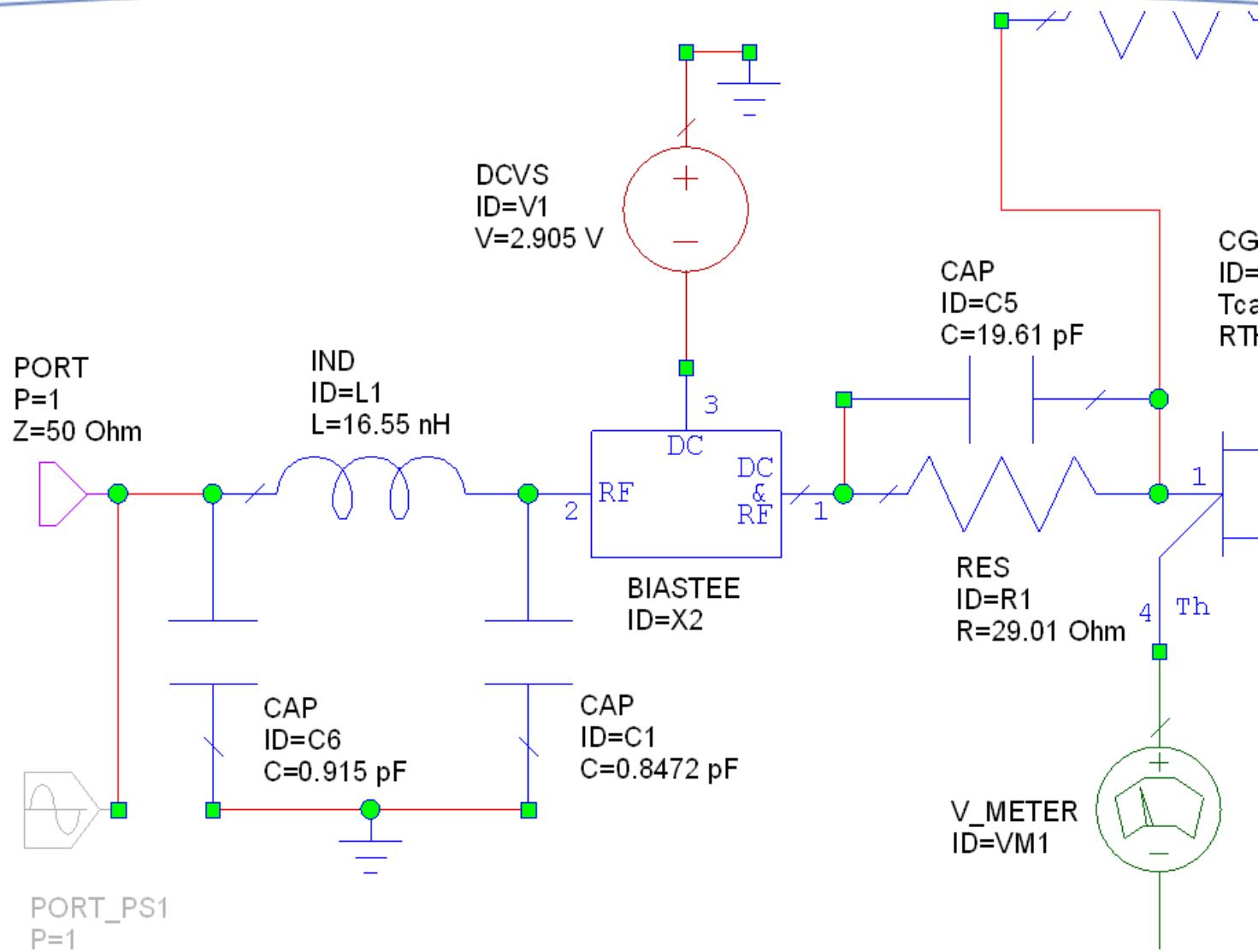


# Feedback Network

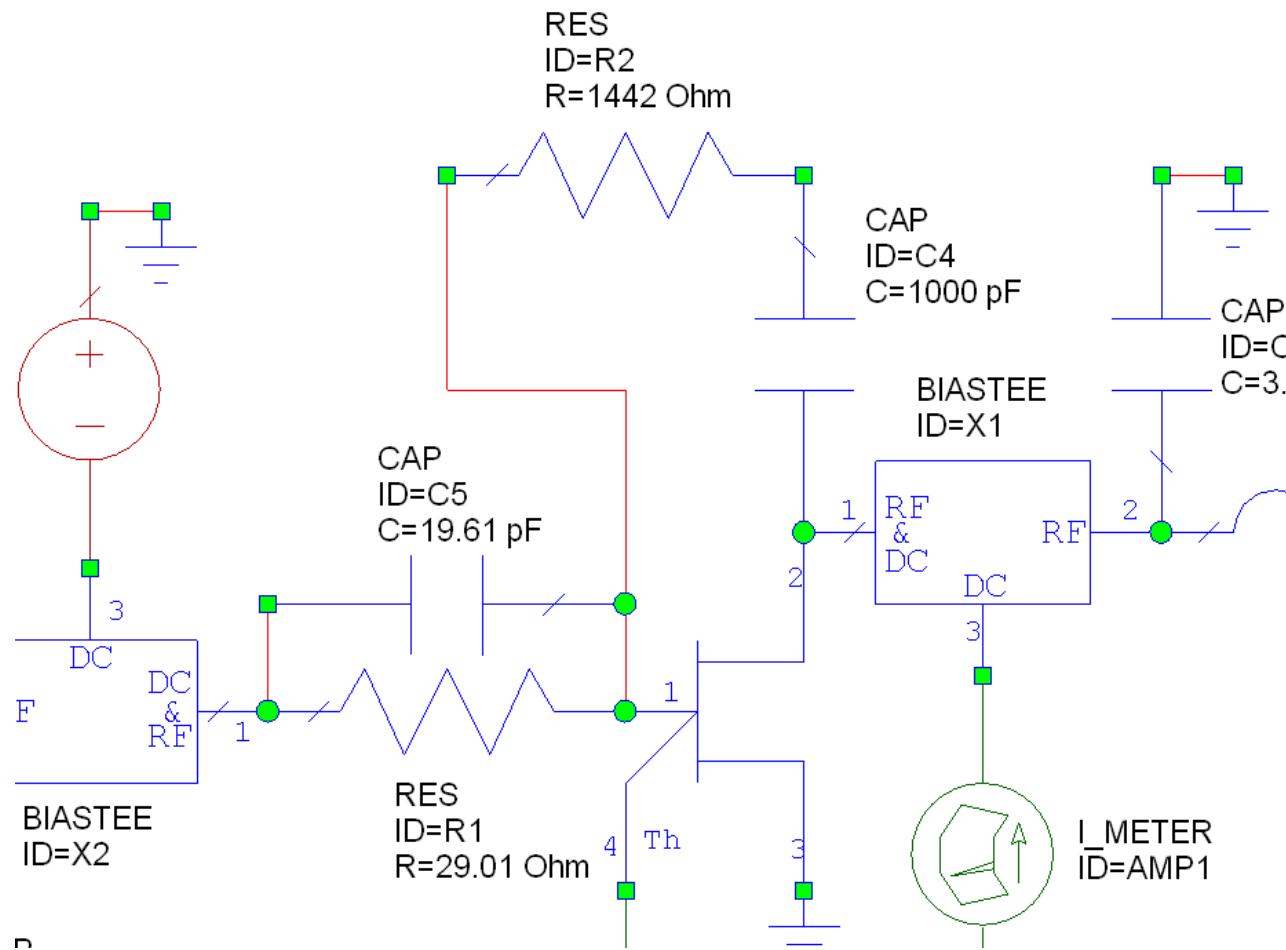


# Output Matching Network

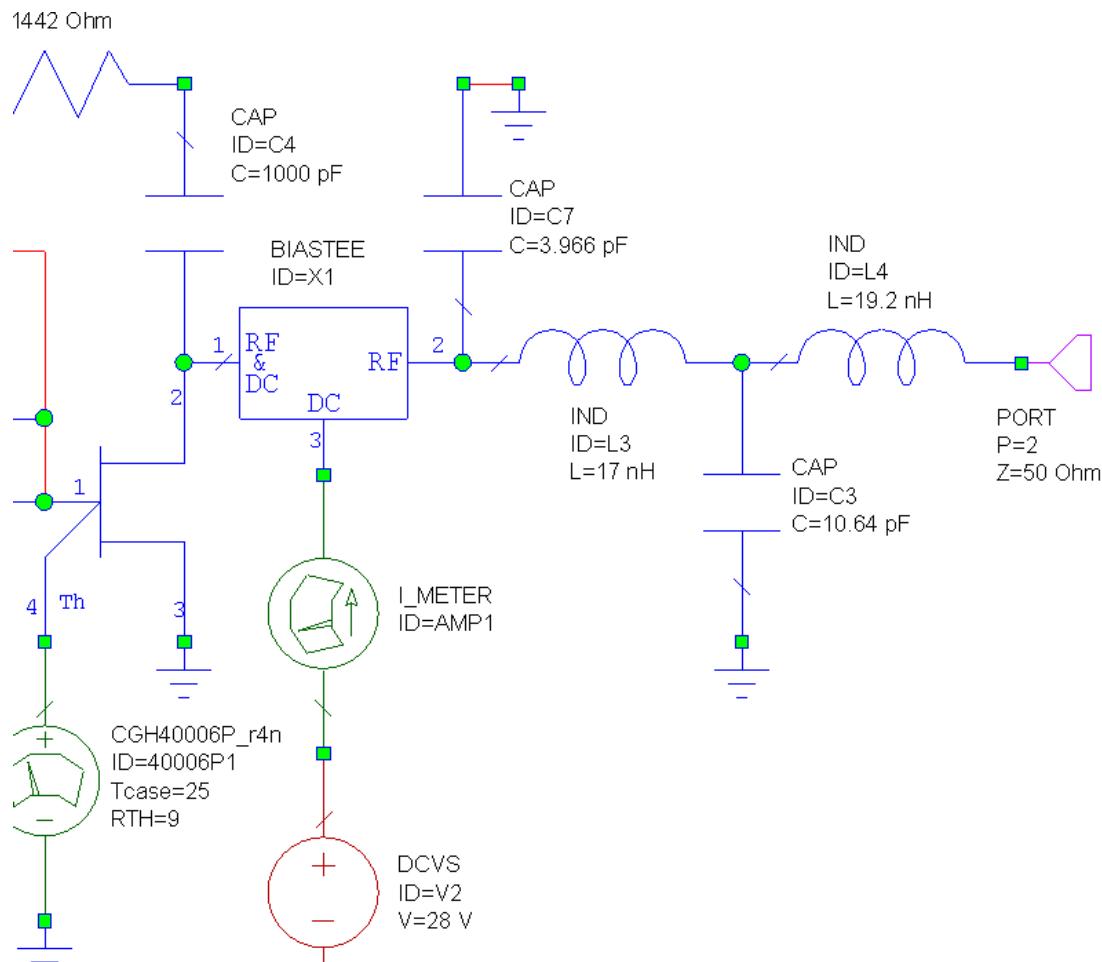

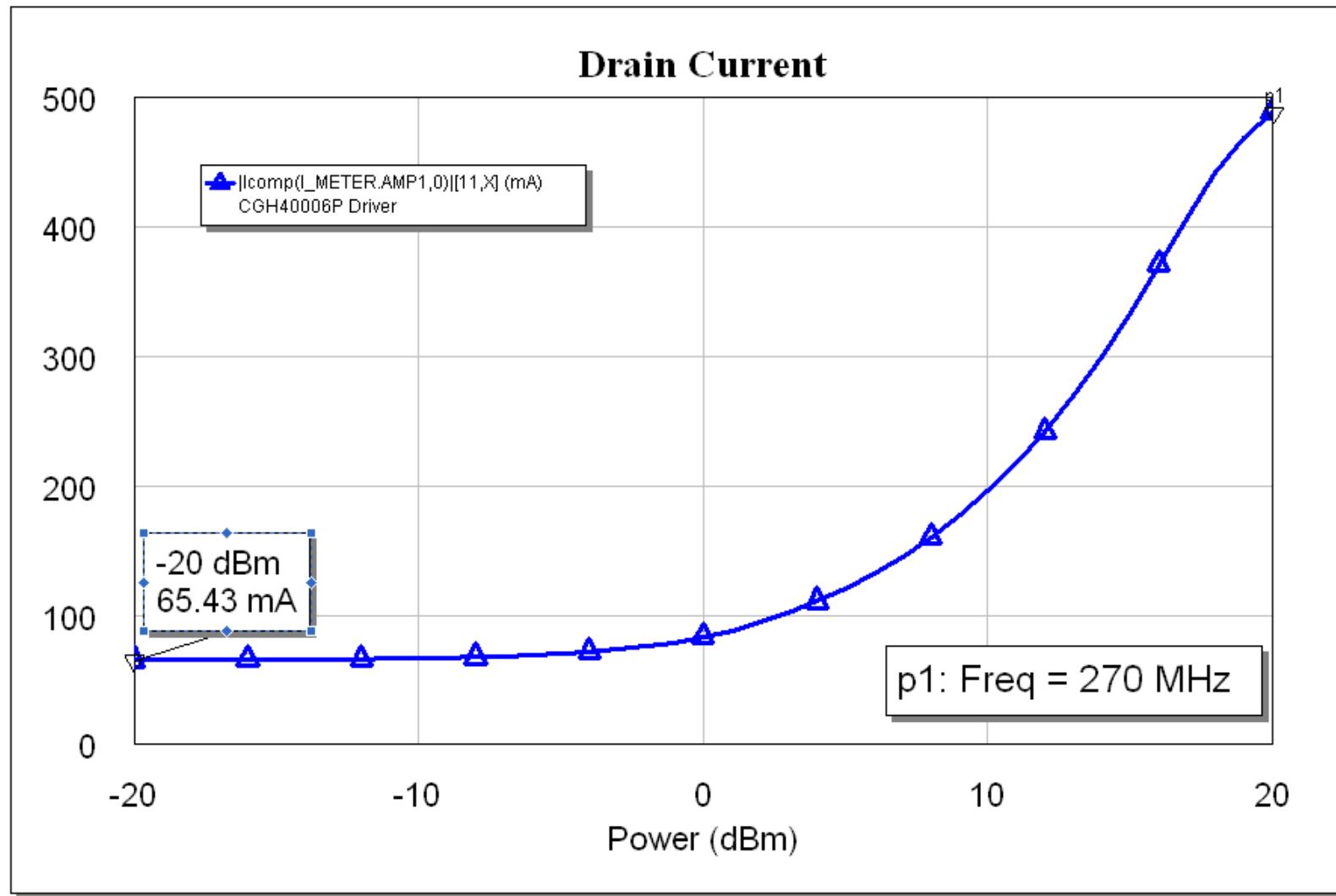
# Typical Drain Current versus Input Power



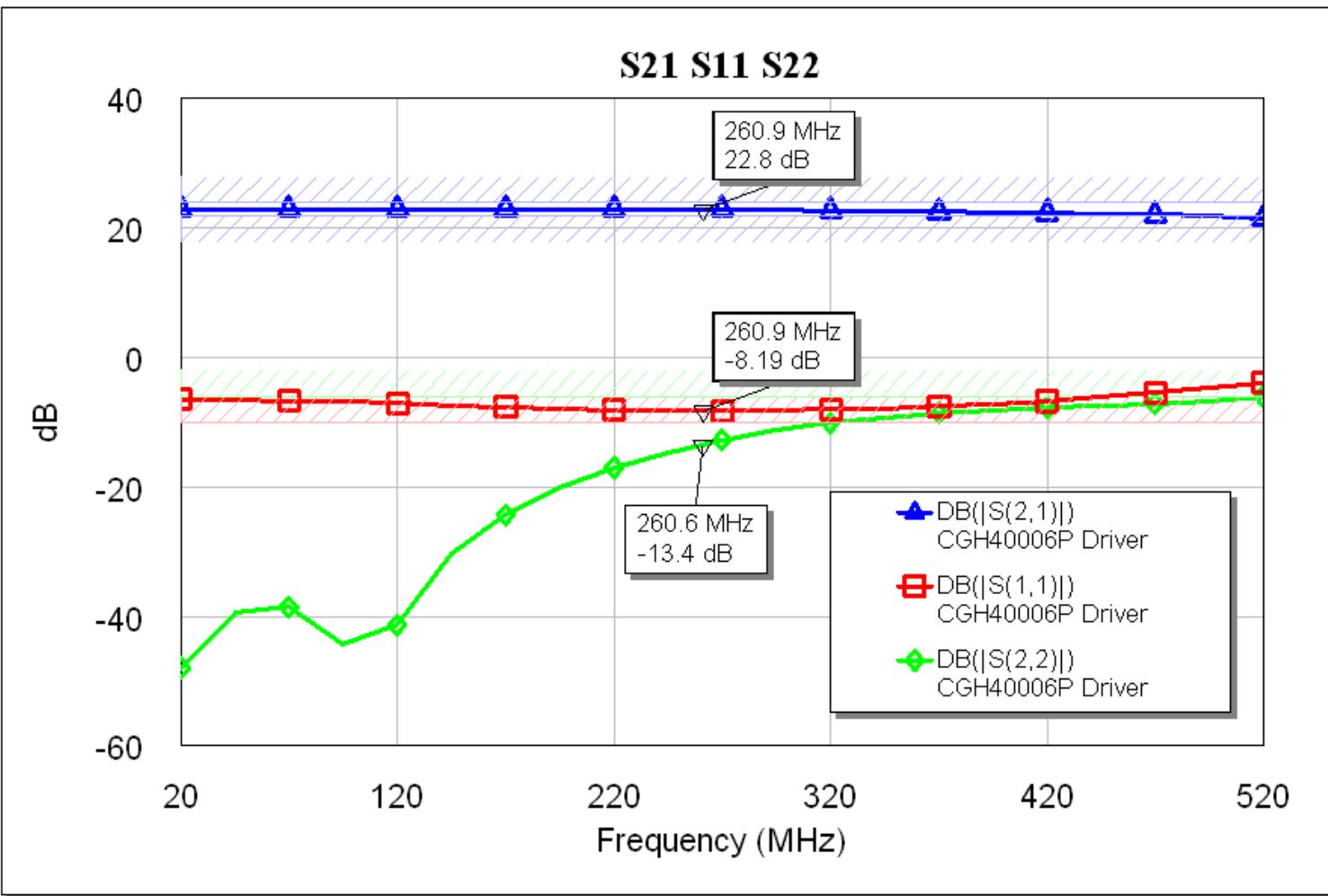
# Small signal gain, input and output return losses



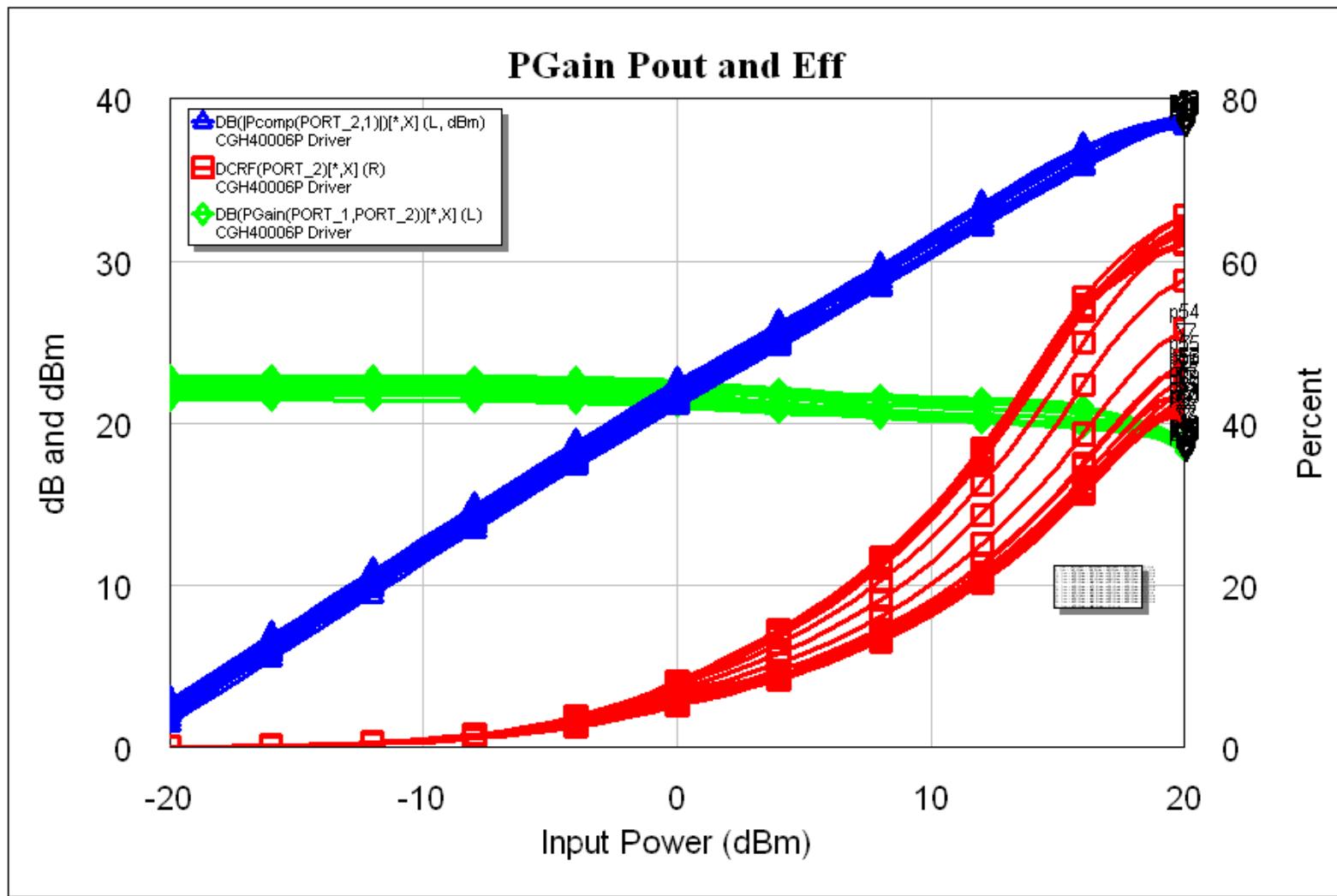
# Gain, Drain Efficiency and Output Power versus Input Power



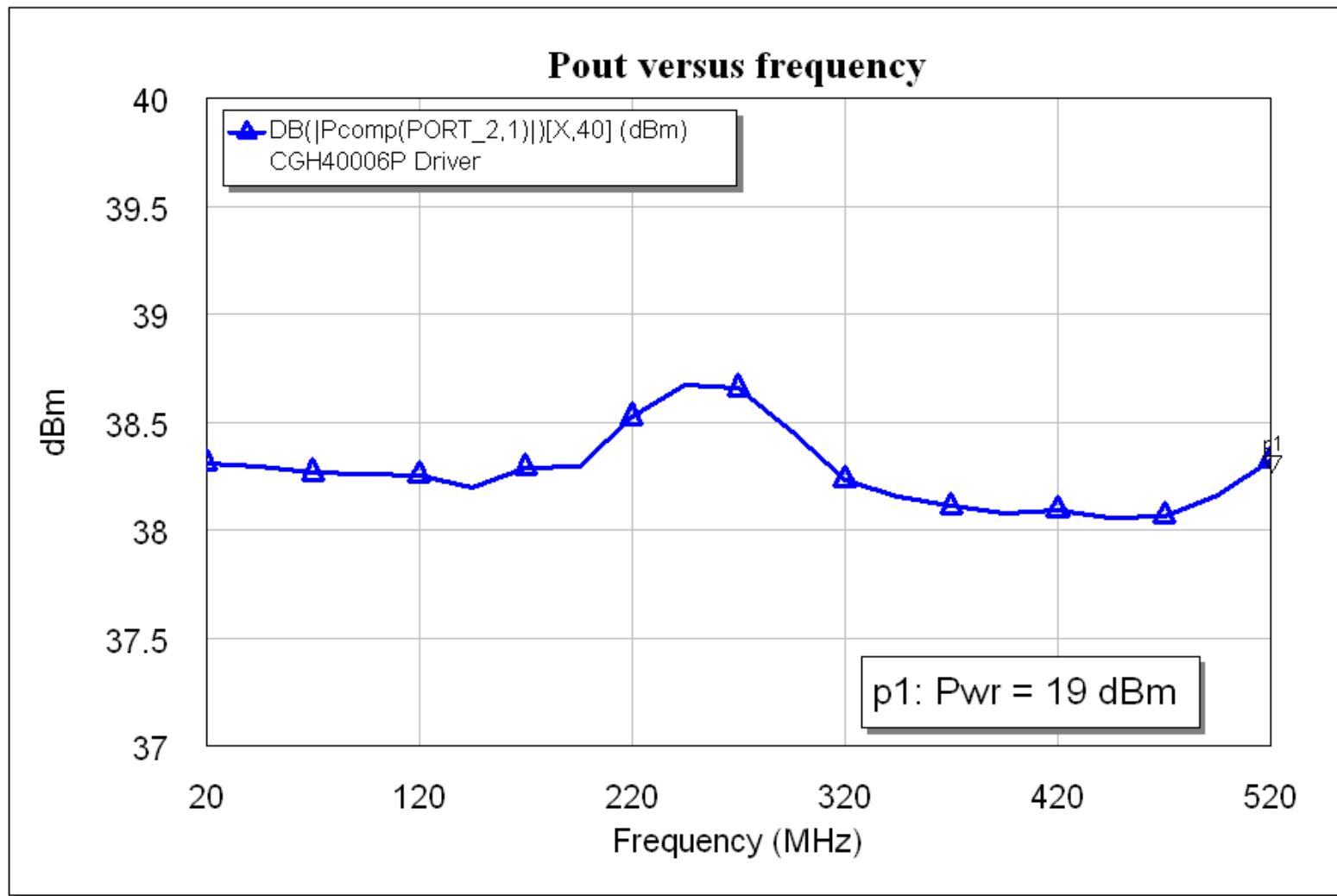
# Output Power versus Frequency at Pin=19 dBm



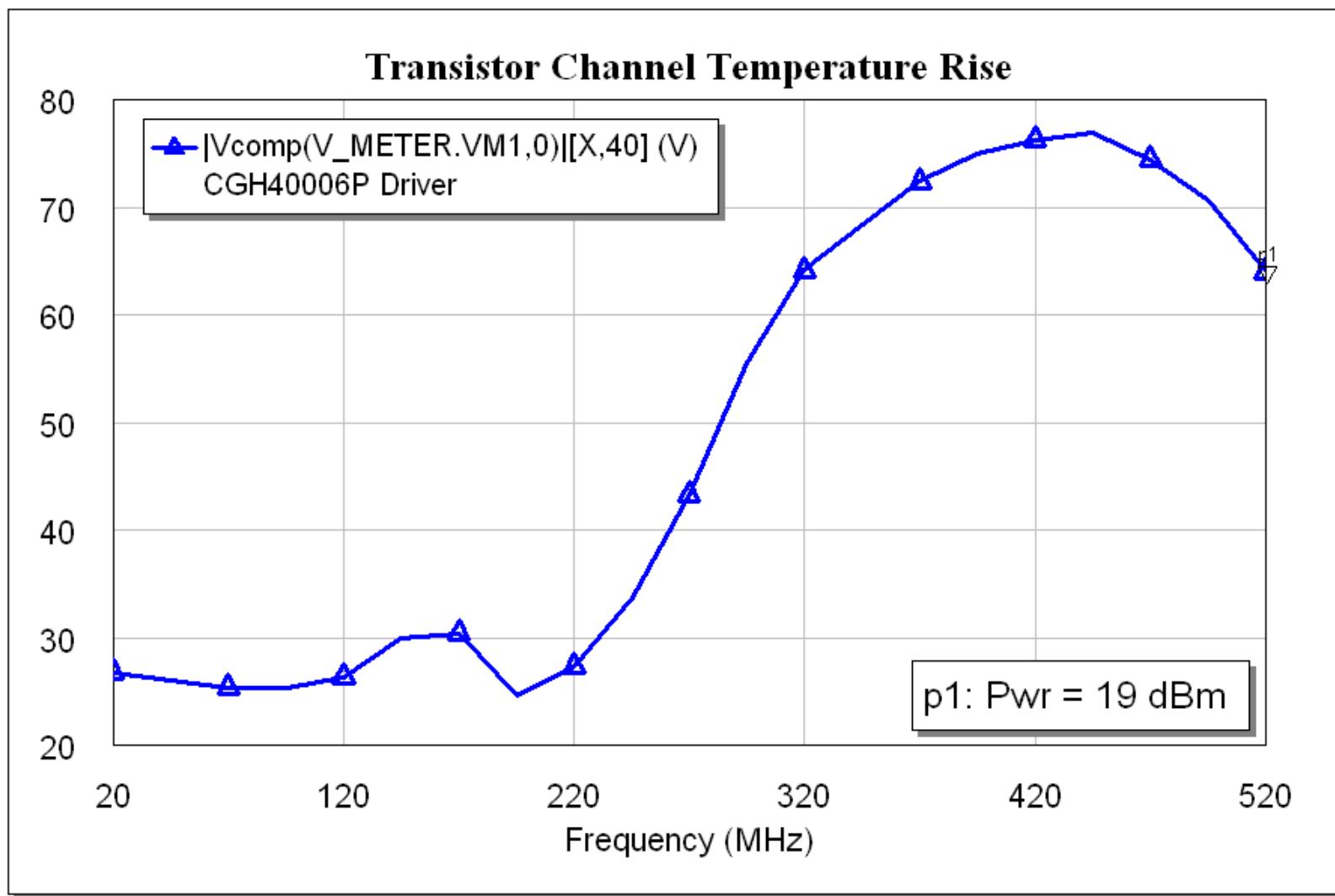
# Transistor Temperature Rise at Pin= 19dBm



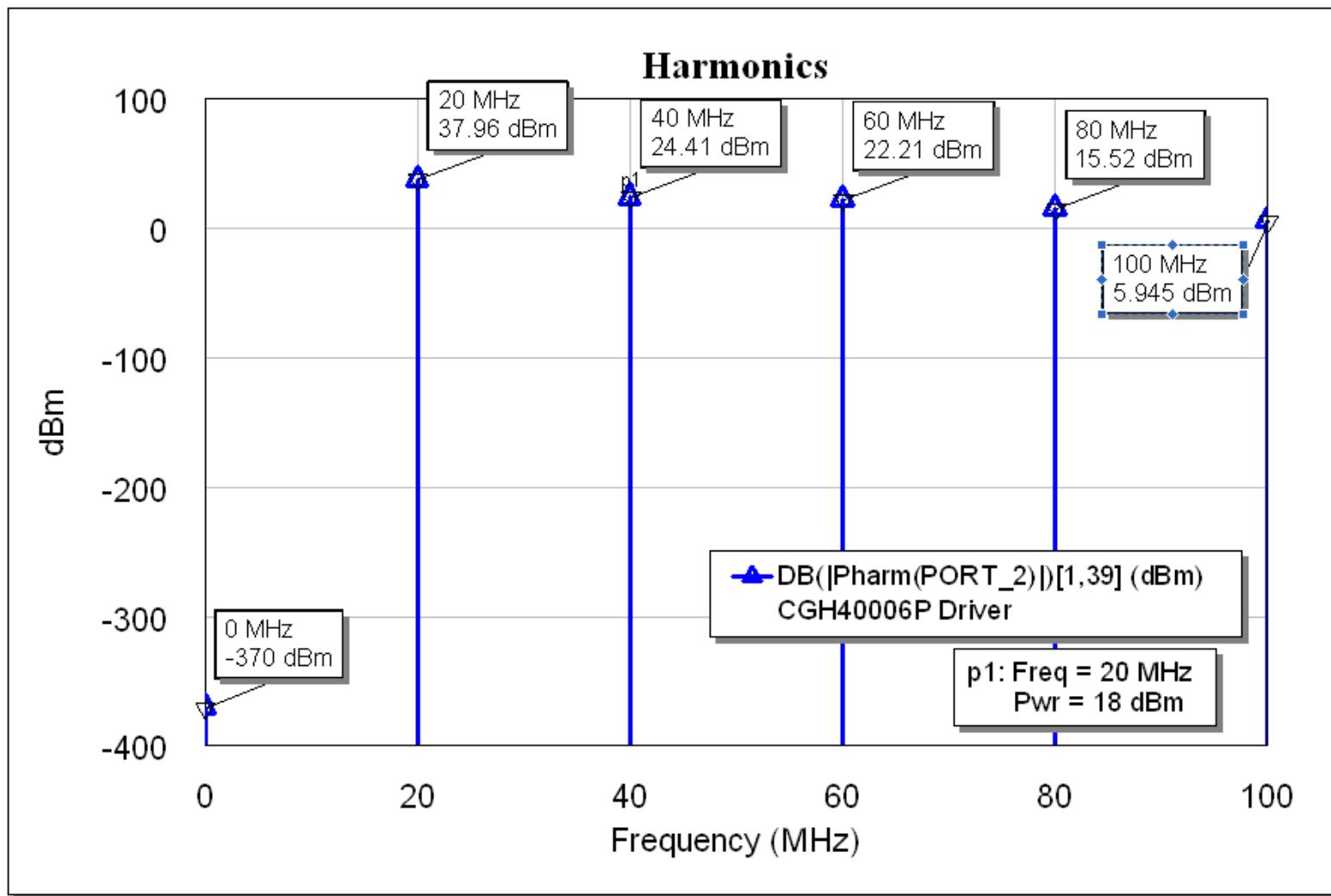
# Harmonics of PA (f=20 MHz) at Pin=18 dBm



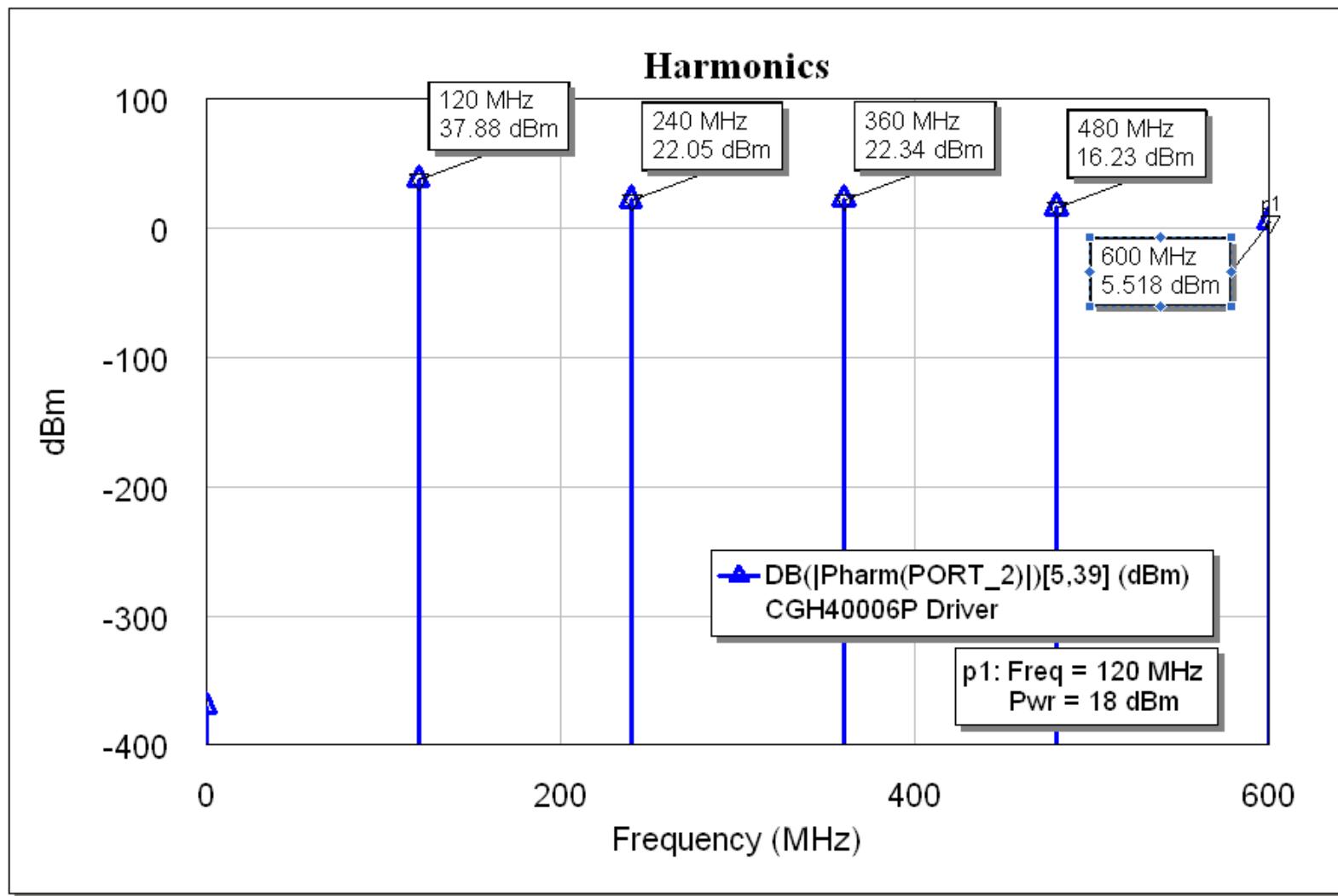
# Harmonics of PA (f=120 MHz) at Pin = 18 dBm



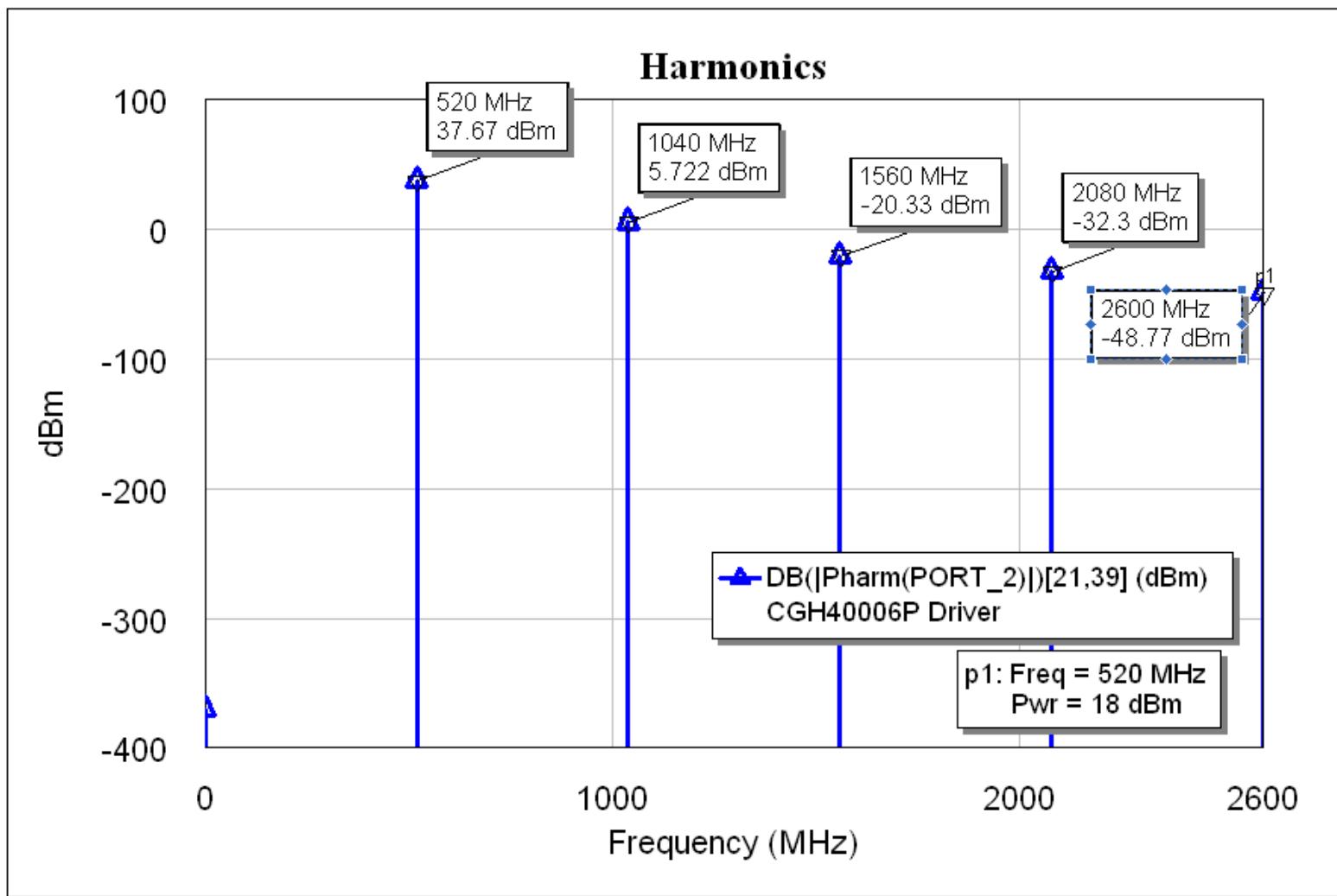
# Harmonics of PA (f=520 MHz) at Pin=18 dBm




# Noise Figure of PA

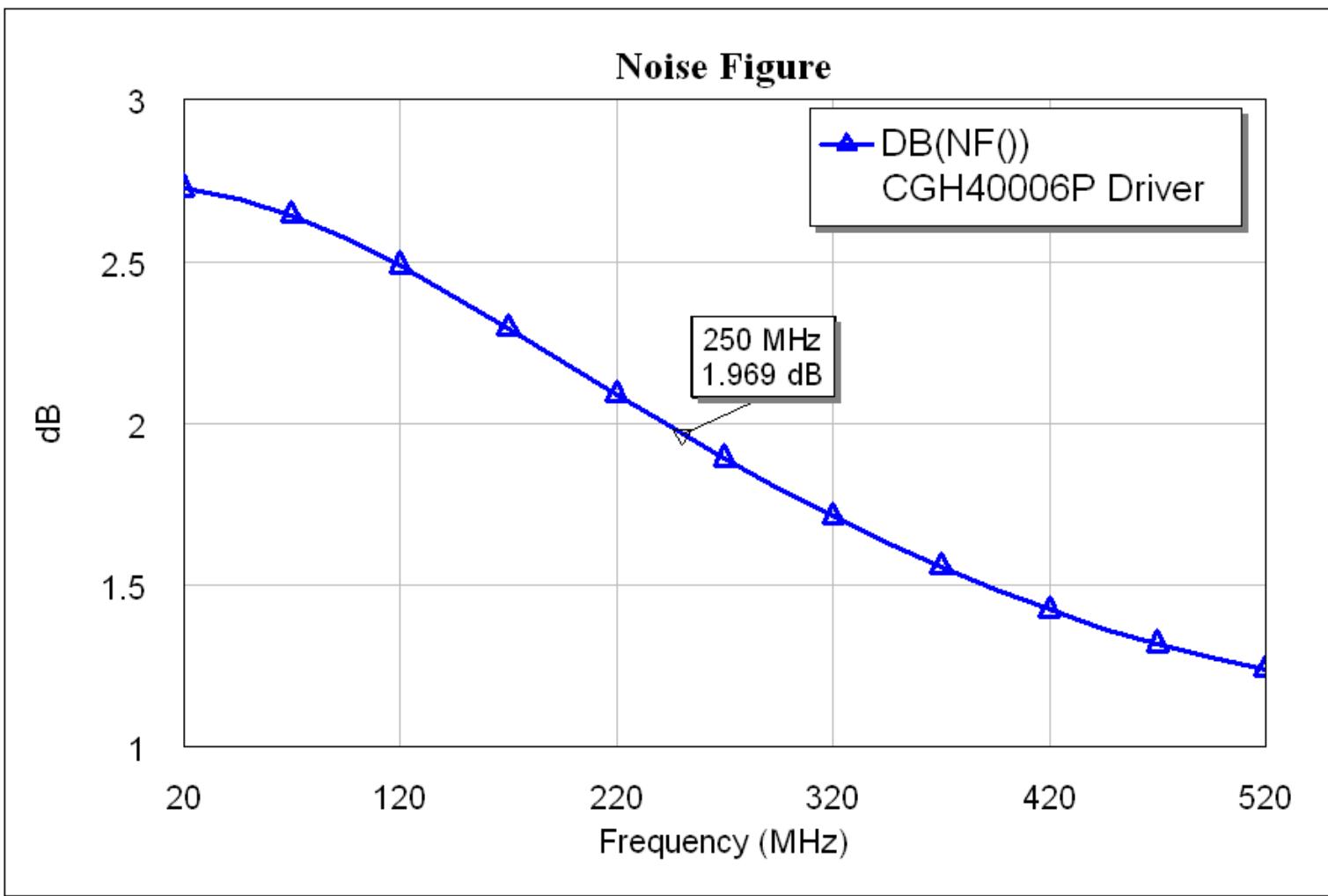

# Ultra-Broadband Performance of PA

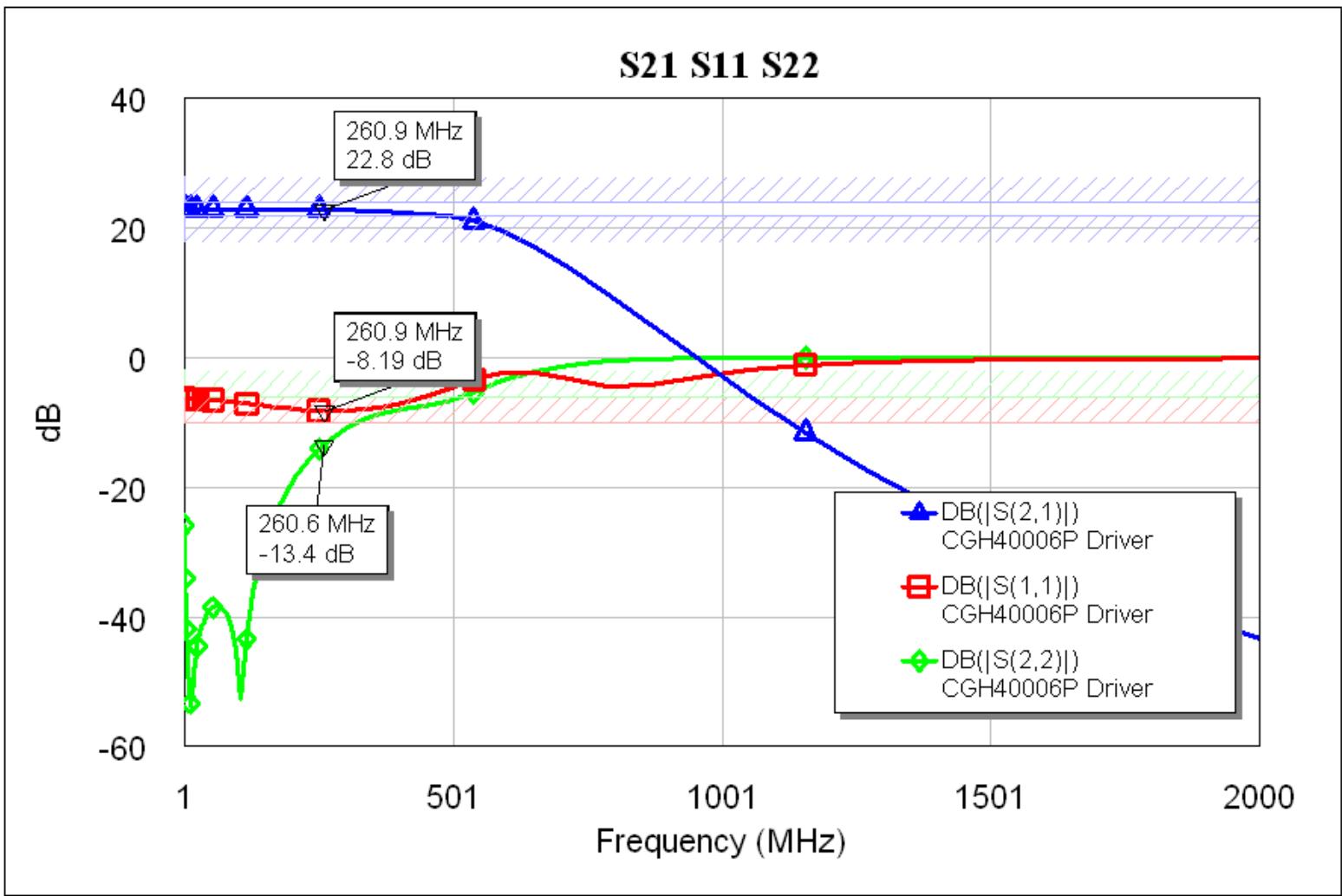
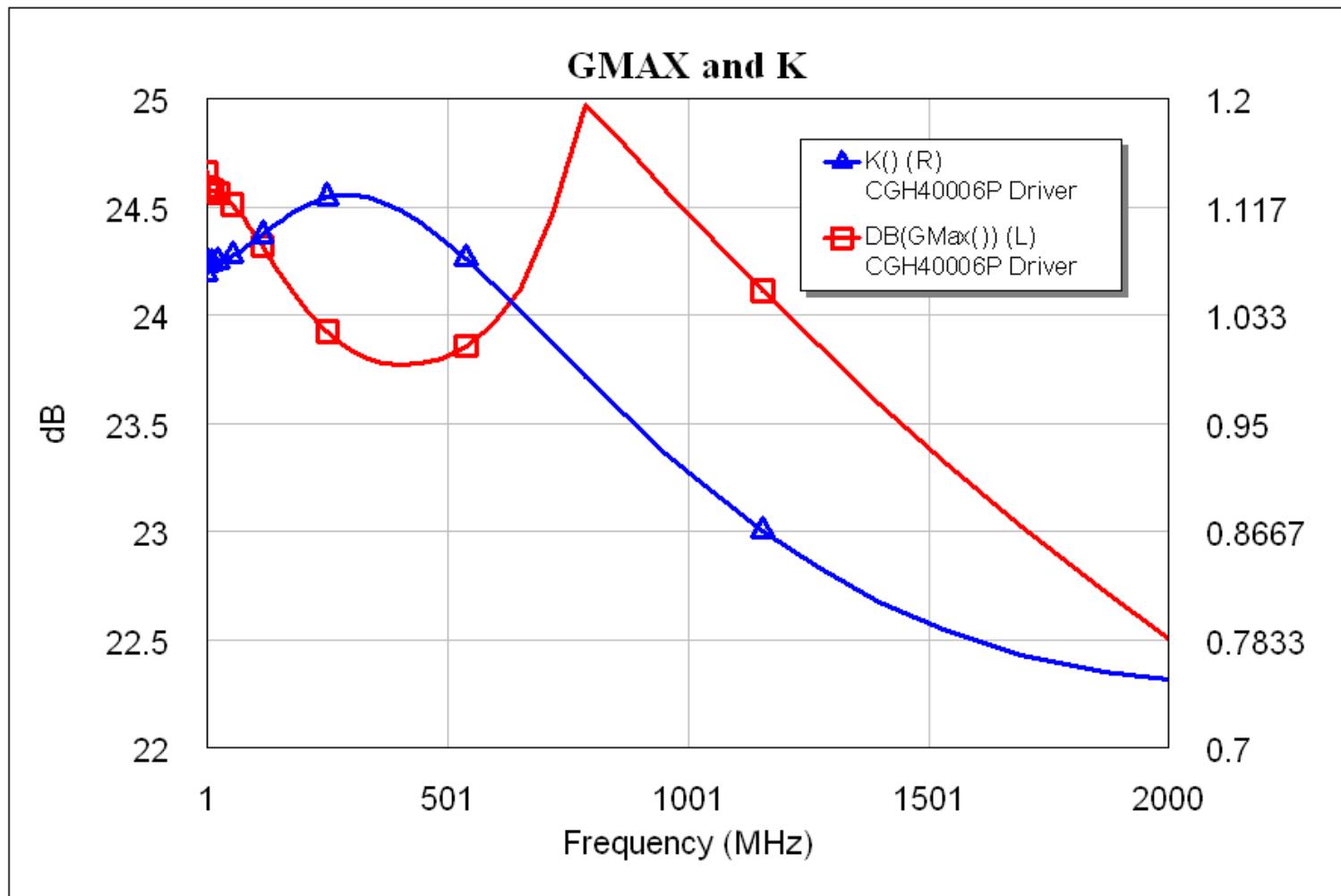
# Ultra-Broadband GMAX and K Factor of PA



# Further Reading

1. J.M. Tirado et al "Trapping effects in the transient response of AlGaN/GaN HEMT devices", *IEEE Trans. on Electron Devices, Vol. 54, No. 3, March 2007*
2. Y.F.Wu, A. Saxler,M. Moore, R. P. Smith, S. Sheppard, P. M. Chavarkar, T.Wisleder, U. K. Mishra, P. Parikh, "30-W/mm GaN HEMTs by field plate optimization," *IEEE Electron Device Lett., vol. 25, no. 11*, pp. 117-119, Nov. 2004.
3. D. Farrell, J. Milligan, B. Million, R. Pengelly, C. Platis, B. Pribble, P. Smith, S. Wood, "Tracking Advances In High-Power GaN HEMTs," *Microwaves and RF*, Feb 2009.
4. S. Wood, R. Pengelly, and Jim Crescenzi, "A High Efficiency Doherty Amplifier with Digital Predistortion for WiMAX," *High Frequency Electronics, Dec 2008*.
5. S. C. Cripps, *RF Power Amplifiers for Wireless Communications*, 2nd ed., Artech House, 2006, pp. 68-73, 122-124
6. R.S. Pengelly, "N-way RF power amplifier with increased back-off power and power added efficiency," U.S. Patent 6,700,444, Mar. 2, 2004.
7. R.S. Pengelly and S.M. Wood, "N-way RF power amplifier circuit with increased back-off capability and power-added efficiency using unequal input power division," U.S. Patent 6,737,922, May 18, 2004.
8. R.S. Pengelly and S.M. Wood, "N-way RF power amplifier circuit with increased back-off capability and power-added efficiency using selected phase lengths and output impedances," U.S. Patent 6,791,417, Sep. 14, 2004.
9. M. Iwamoto, A. Williams, P.-F Chen, Andre G. Metzger, Lawrence E. Larson, Peter M. Asbeck, "An Extended Doherty Amplifier With High Efficiency Over a Wide Power Range," *IEEE MTT, vol. 49 no. 12 pp. 2472-2479*, Dec 2001.

# Further Reading

10. Y. Tajima, "100 Watt GaN HEMT Modeling" *Microwave Journal, May 2007*
11. R. Pengelly et al, "Application of Non-Linear Models to a range of challenging GaN HEMT power amplifier designs" *Workshop WMF, IEEE MTT-S IMS 2008;*  
[http://www.cree.com/products/pdf/App\\_of\\_Non-linear\\_Models\\_for\\_GaN\\_HEMT\\_PA\\_Design.pdf](http://www.cree.com/products/pdf/App_of_Non-linear_Models_for_GaN_HEMT_PA_Design.pdf)
12. M.J. Pelk et al, "A High-Efficiency 100-W GaN Three-Way Doherty Amplifier for Base-Station Applications" *IEEE Transactions on Microwave Theory and Techniques;*  
[http://www.cree.com/products/pdf/High\\_Efficiency\\_100W\\_GaN\\_3-Way\\_Doherty\\_Amp\\_Base\\_Station\\_Apps.pdf](http://www.cree.com/products/pdf/High_Efficiency_100W_GaN_3-Way_Doherty_Amp_Base_Station_Apps.pdf)
13. J. Kim et al, "A Saturated PA with High Efficiency" *IEEE Microwave Magazine, February 2009;* [http://www.cree.com/products/pdf/A\\_Saturated\\_PA\\_with\\_High\\_Efficiency-Student\\_Comp-08.pdf](http://www.cree.com/products/pdf/A_Saturated_PA_with_High_Efficiency-Student_Comp-08.pdf)
14. B. Millon et al, "Design of GaN HEMT Transistor Based Amplifiers for 5 - 6 GHz WiMAX Applications" *Proceedings of 2008 European Microwave Conference;*  
[http://www.cree.com/products/pdf/Design\\_GaN\\_HEMT\\_Transistor\\_Based\\_Amplifiers\\_for\\_5-6GHz\\_WiMAX.pdf](http://www.cree.com/products/pdf/Design_GaN_HEMT_Transistor_Based_Amplifiers_for_5-6GHz_WiMAX.pdf)
15. D. Schmelzer et al, "A GaN HEMT Class F Amplifier at 2 GHz with > 80 % PAE" , *2006 IEEE Compound Semiconductor IC Symposium;*  
[http://www.cree.com/products/pdf/GaN\\_HEMT\\_Class\\_F\\_Amplifier\\_at\\_2\\_GHz\\_with\\_80\\_PAE.pdf](http://www.cree.com/products/pdf/GaN_HEMT_Class_F_Amplifier_at_2_GHz_with_80_PAE.pdf)
16. M. Berroth et al, "Non-linear GaN HEMT modeling including thermal effects", *2<sup>nd</sup> joint symposium on opto- and microelectronic devices and circuits, 2002 pp. 236-239*

# Further Reading

17. F. Kharabi, M.J. Poulton, et al, "A Classic Nonlinear FET Model for GaN HEMT Devices", *IEEE Compound Semiconductor Integrated Circuit Symposium, 2007, 14-17 Oct. 2007 pp. 1-4*
18. Huq, H et al, "Analytical model, simulation, and parameter extraction of AlGaN/ GaN HEMT for microwave circuit applications" *Gallium Nitride Materials and Devices II. Edited by Morkoc, Hadis; Litton, Cole W.. Proceedings of the SPIE, Volume 6473, pp. 64731N (2007)*.
19. E.S. Mengistu et al "A Large-Signal Model of GaN HEMTs for Linear High Power Amplifier Design", *European Microwave Integrated Circuits Conference, 2006, 10-13 Sept. 2006 pp. 292 – 295*
20. E.S. Mengistu, "Large-signal Modeling of GaN HEMTs for Linear Power Amplifier Design" *Published by Kassel University Press GmbH, 2008, ISBN 3899583817, 9783899583816*
21. S. Chalermwisutkul "Large Signal Modeling of GaN HEMTs for UMTS Base Station Power Amplifier Design Taking into Account Memory Effects"; [http://darwin.bth.rwth-aachen.de/opus3/volltexte/2007/1843/pdf/Chalermwisutkul\\_Suramate.pdf](http://darwin.bth.rwth-aachen.de/opus3/volltexte/2007/1843/pdf/Chalermwisutkul_Suramate.pdf)
22. E. Kohn et al, "Transient characteristics of GaN-based heterostructure field-effect transistors" *IEEE Transactions on Microwave Theory and Techniques, vol. 51, no. 2, pp. 634 –642, 2003*
23. P. McGovern, J. Benedikt, P.J.Tasker et al.: "Analysis of DC-RF dispersion in AlGaN/GaN HFETs using pulsed I-V and time-domain waveform measurements" *Microwave Symposium Digest, 2005 IEEE MTT-S International, 2005, pp. 503–506*
24. R.J. Trew, G.L. Bilbro, W. Kuang, Y. Liu, H. Yin, "Microwave Al-GaN/GaN HFETs" *IEEE Microwave Magazine, vol. 6, 2005, pp. 56–66*