

Semester project

TTT4201 - Radio System Design and
RF/Microwave Measurement Techniques

Design of a RF power amplifier

- Discrete transistor by MACOM (Wolfspeed/Cree)
- Part1: Design of the RF power amplifier with the help of Advanced Design Systems (ADS)
- Part2: Measurements of your designed RF power amplifier at the department's microwave laboratory
- Part3: Hand in a full report
 - The report should, as a minimum, include the design process for your design, and a comparison of your simulated and measured results, followed by a discussion and a conclusion. **The length of the report should not exceed 15 pages, including the appendix.**

Device technology and components

- The transistor you will be using in the design is a packaged, discrete transistor by MACOM, CG2H40010 (10W)
- The CAD-model for the transistor is provided in Blackboard/Teams. After installation of the CAD-model in ADS, you will find the transistor in the **Cree_Wlfspd_ADS_v2p5** library. The name of the component is **CG2H40010F**
- **Microstrip substrate**: standard FR-4 substrate with parameters as summarized in table 1. These parameters should be entered into the **MSUB** component found in the **TLines-Microstrip** library in ADS

H	Er	Mur	Cond	T	TanD
$1.52 \times 10^{-3} \text{ m}$	4.4	1.0	5.96×10^7	$35 \times 10^{-6} \text{ m}$	0.02


Passive components,

- Resistors: use the standard, ideal resistors found in the Lumped-Components library in ADS (E12-series)
- Capacitors: CAD-models provided on Blackboard, Johanson RF capacitors and Murata for decoupling.
- Inductors: Johanson library (if you need)

Table 2: Available component values for the R14S capacitors in ~~pico~~ farad.

0.3	0.5	0.8	1.0	1.2	1.5	1.8	2.2	2.7	3.3	3.6	3.9	4.7
5.6	6.8	7.5	8.2	9.1	10	12	15	18	20	22	24	27
30	33	36	39	43	47	56	68	82				

Bias network

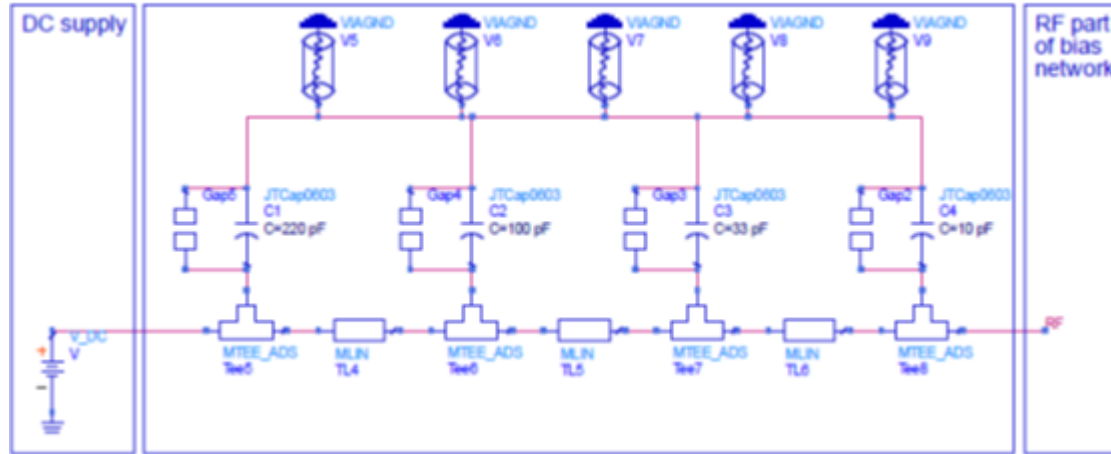

Design restrictions

- The frequency of operation (f_c) is 2.4 GHz.
- The device must be biased with a drain voltage (V_D) of 28 V.
- The drain current (I_D) should be no less than 50 mA. This implies that gate voltages (V_G) below approximately -3.0 V cannot be used.

Small-signal specifications

- The device must be unconditionally stable, e.g. the stability factor (μ) must be greater than unity for all frequencies.
- The small-signal bandwidth (f_{bw}) should be at least 100 MHz within 1dB.
- The small-signal gain (S_{21}) should be at least 14 dB throughout the bandwidth (2.35 GHz to 2.45 GHz).

Large-signal specifications


- The device should produce an output power (P_{out}) of at least 39 dBm with a maximum single-tone input power (P_{in}) of 27 dBm.
- For a two-tone peak output power of 38 dBm, the intermodulation distortion (IMD) should be as little as possible. The tone spacing should be 5 MHz for the two-tone test.

Target specifications

- Each group should target either
 - Maximum output power (maximizing P_{out} compared to the common specification) for single tone input.
 - Maximum power added efficiency (η_{PAE}) for a single-tone input, keeping the common specifications.

Layout

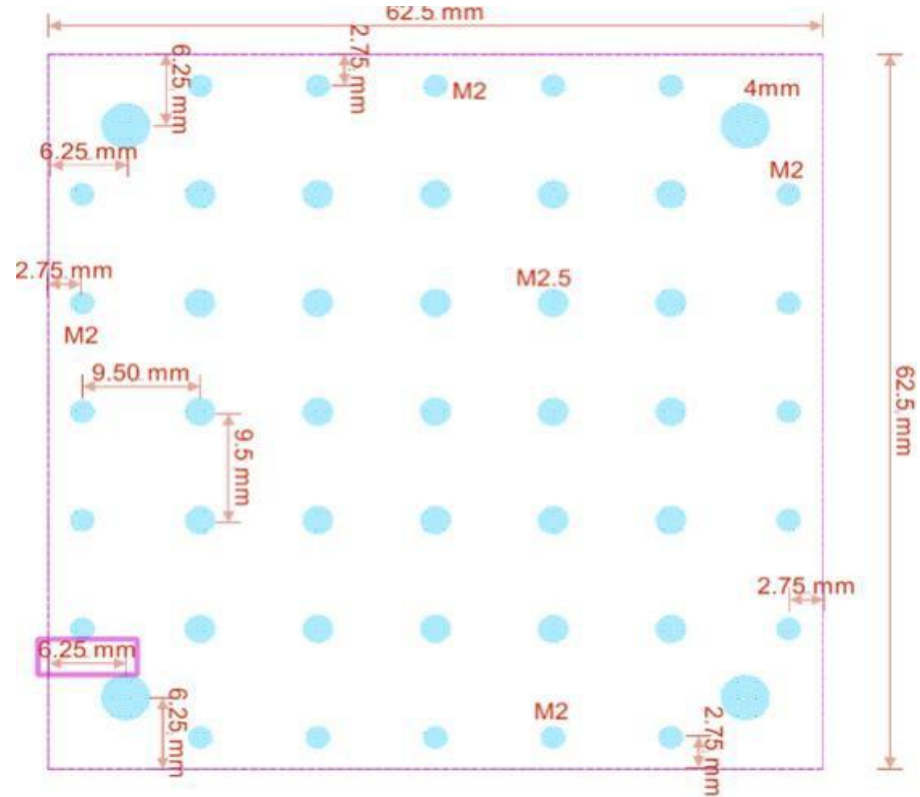- The layout should fit on a 62.5 mm-by-62.5 mm area, as depicted in the figure
- You only must adjust your layout to agree with the placement of the screw holes for the transistor.



Examples

